

# Rectifying circuits


## Annex

Analog Circuits

11/2/2012 | 23

DIODES


### Half Wave

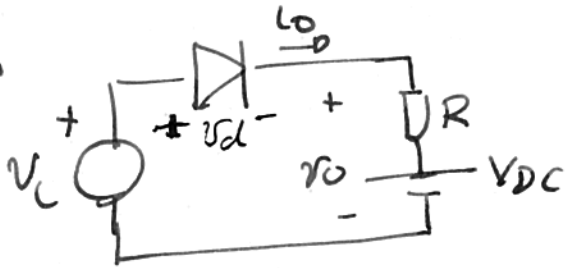

$$\begin{cases} v_i > V_{DC} \Rightarrow \text{ON} & \begin{cases} (v_o = v_i) \\ (i_L \neq 0) \end{cases} \\ v_i < V_{DC} \Rightarrow \text{OFF} & \begin{cases} (i_L = 0) \\ v_o = V_{DC} \end{cases} \end{cases}$$

$$v_i > V_{DC} \Rightarrow v_o = v_i \Rightarrow \begin{cases} i_L = \frac{v_i - V_{DC}}{R} \\ v_o = v_i \\ v_d = 0 \end{cases}$$
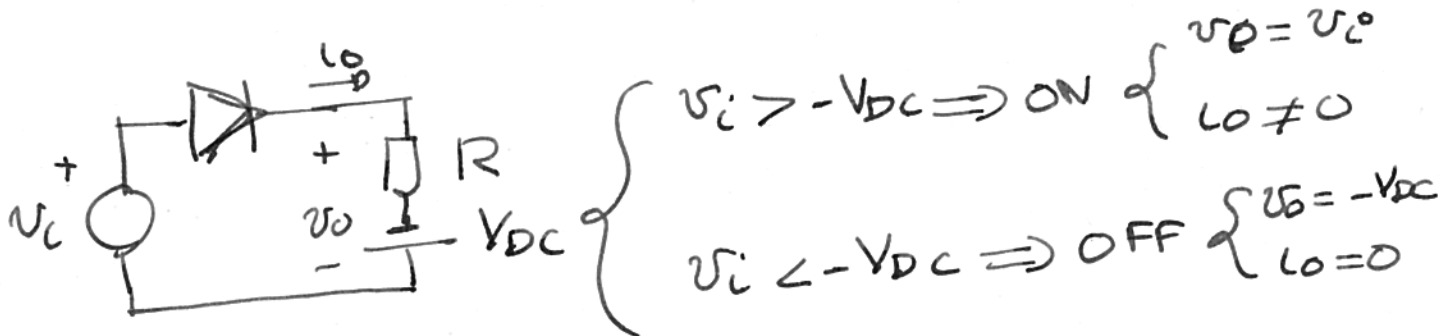
$$v_i < V_{DC} \Rightarrow v_o = V_{DC} \Rightarrow \begin{cases} i_L = 0 \\ v_d = v_i - V_{DC} \end{cases}$$




$$\begin{cases} v_i > -V_{DC} \Rightarrow \text{ON} & \begin{cases} v_o = v_i \\ i_L \neq 0 \end{cases} \\ v_i < -V_{DC} \Rightarrow \text{OFF} & \begin{cases} v_o = -V_{DC} \\ i_L = 0 \end{cases} \end{cases}$$

$$v_i > -V_{DC} \Rightarrow v_o = v_i \Rightarrow i_L = \frac{v_i + V_{DC}}{R}$$


$$v_i < -V_{DC} \Rightarrow v_o = -V_{DC} \Rightarrow i_L = 0$$

# Full wave

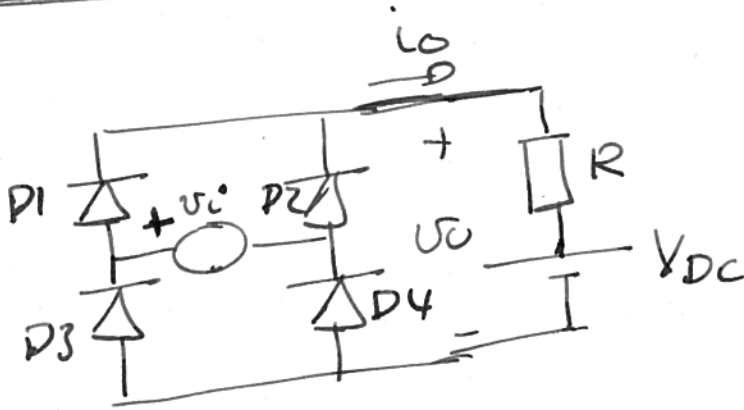


$$\left\{ \begin{array}{l} |v_i| > V_{DC} \Rightarrow \text{ON} \\ |v_i| < V_{DC} \Rightarrow \text{OFF} \end{array} \right. \Rightarrow \begin{cases} v_o = |v_i| \\ v_o = 0 \end{cases}$$


$$\Rightarrow \begin{cases} i_o = \frac{|v_i| - V_{DC}}{R} \\ i_o = 0 \end{cases}$$

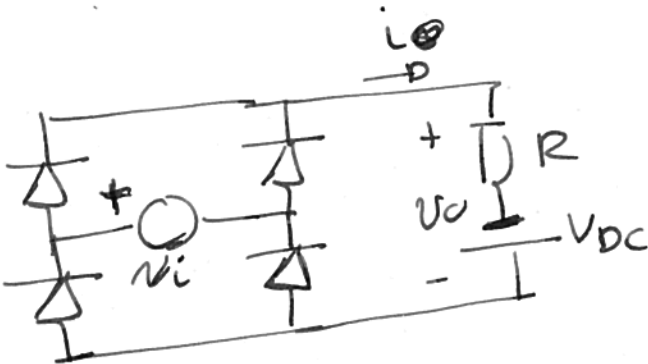

Always on  $\Rightarrow v_o = |v_i| \Rightarrow i_o = \frac{|v_i| + V_{DC}}{R}$

# DIODE'S VOLTAGES

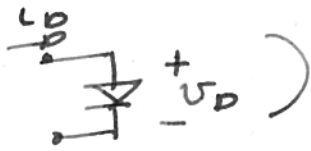(Remark: )

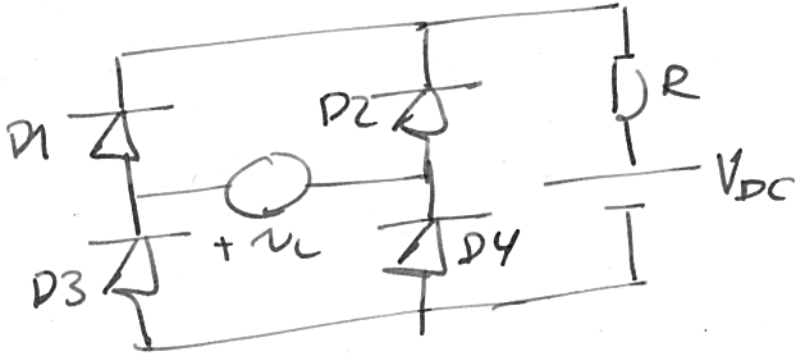

①  $v_L > V_{DC} \Rightarrow$   $\left. \begin{matrix} D1 + D4 \text{ ON} \\ D2 + D3 \text{ OFF} \end{matrix} \right\} \Rightarrow$   
 ( $v_L$  is  $> 0$ )

$$\begin{cases} v_{D1} = v_{D4} = 0 \\ v_{D2} = v_{D3} = -v_L \\ v_O = v_L \end{cases}$$

②  $v_L < -V_{DC} \Rightarrow$   $\left. \begin{matrix} D2 + D3 \text{ ON} \\ D1 + D4 \text{ OFF} \end{matrix} \right\} \Rightarrow$   
 ( $v_L$  is  $< 0$ )

$$\begin{cases} v_{D2} = v_{D3} = 0 \\ v_{D1} = v_{D4} = +v_L \\ v_O = -v_L \end{cases}$$

③  $-V_{DC} < v_L < V_{DC} \Rightarrow$   $\left. \begin{matrix} D1, D2 \\ D3, D4 \end{matrix} \right\} \underline{\underline{\text{OFF}}} \Rightarrow v_O = V_{DC}$

3.1 ~~...~~  $v_{D1} = v_{D4}$  (why not??)  $\Rightarrow$   
 $v_{D2} = v_{D3}$  (why not??)

$$-2v_{D1} + v_L = V_{DC} \Rightarrow v_{D1} = \frac{-V_{DC} + v_L}{2} = v_{D4}$$


$$-2v_{D2} = v_L = V_{DC} \Rightarrow v_{D2} = \frac{-(V_{DC} + v_L)}{2} = v_{D3}$$

## Voltage D1 diode

$$V_i = 50 \sin(100\pi t)$$

$$V_{dc} = 35 \text{ V}$$

$$R_L = 500\Omega$$

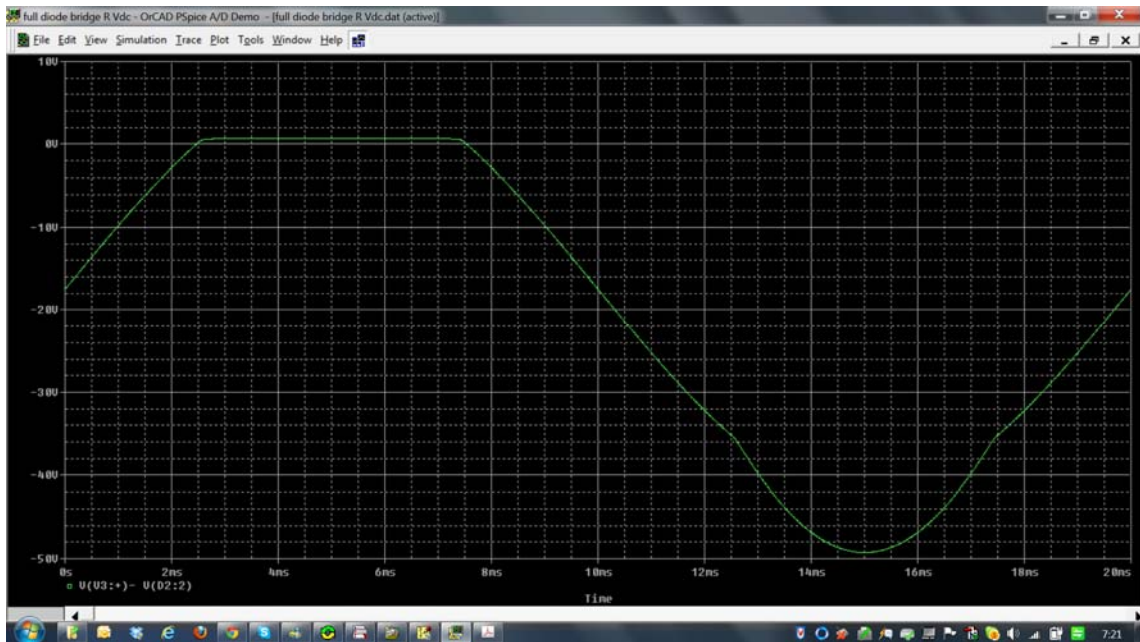


# HALF WAVE WITH RC LOAD

Analogy circuits


11/2/2012 | 25

DIODES

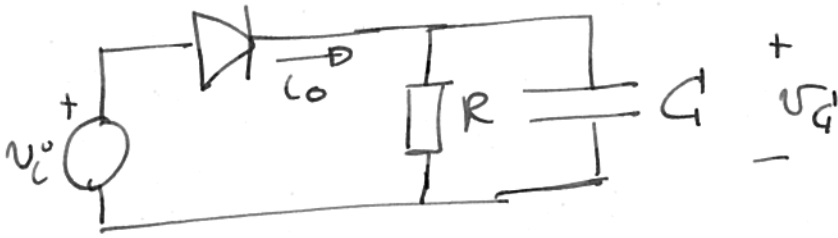

$$v_i = V \sin \omega t$$

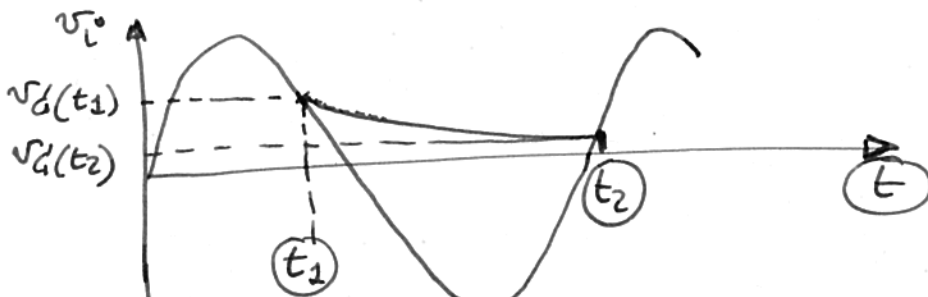First cycle analysis .  $v_D(0) = 0$  (Initial condition)



$$0 < t < t_1 \quad \text{D ON}$$

$$i_D = i_R + i_C = \frac{V}{R} \sin(\omega t) + V C \omega \cos \omega t$$

$$\left. \begin{array}{l} i_R > 0 \quad (0 < t < \frac{T}{2}) \\ i_C > 0 \quad (0 < t < \frac{T}{4}) \\ i_C < 0 \quad (\frac{T}{4} < t < T) \end{array} \right\} \Rightarrow \exists t_1 / i_D = 0$$

$$t_1 \quad \frac{V}{R} \sin \omega t_1 + V C \omega \cos \omega t_1 = 0 \Rightarrow t_1 \Rightarrow$$

$$v_D(t_1) = V \sin(\omega t_1)$$

If  $Z = RC$  is ~~high~~ <sup>big</sup> enough, so that the capacitor will not be discharged ( $v_D(t) = 0$  is not reached):

$t_1 < t < t_2$  (DOFF)

$$v_d(t) = v_d(t_1) \left( 1 - e^{-\frac{t-t_1}{R_d}} \right)$$

Analogue circuits  
 11/2/2012 | 26  
 DIODES

$$i_o(t) = 0$$

$$v_R(t) = \frac{v_d(t)}{R} = -v_d(t)$$

obviously

$t_2 < t < T + t_1$  (DON)

and the steady state is already reached.

$$v_d \text{ ripple} = \Delta v_d = V - v_d(t_2)$$

~~It can be shown that:~~

It can be shown:

- $\Delta v_d \downarrow \downarrow$  if  $C \uparrow \uparrow$  ( $R, \omega \equiv ct$ )
- $\Delta v_d \downarrow \downarrow$  if  $\omega \uparrow \uparrow$  ( $R, d \equiv ct$ )
- $\Delta v_d \downarrow \downarrow$  if  $R \uparrow \uparrow$  ( $d, \omega \equiv ct$ )

If  $\tau = R_d C$  is small enough, so that the capacitor is fully discharged ~~again~~

