

Digital Systems

Mid-semester examination. April 28, 2021

Time limit: 90 minutes.

1 Problem: A Finite State Machine (50%)

The graph in *Figure 1* describes a synchronous (clock-driven) FSM.

 


Figure 1: Graph of a synchronous (clock-driven) FSM.

- a) Describe the previous FSM in VHDL. Help yourself to the following VHDL sketch. Use one **process** statement to describe the sequential part, and one or two more **process** statements, as you like, to describe the combinational part.

```
library ieee;
use ieee.std_logic_1164.all;

entity fsm is
    port( clk      : in std_logic;
          event    : in std_logic_vector(1 downto 0);
          y1,y2,y3 : out std_logic);
end;

architecture arch of fsm is
    type multiplier_state is (A, B, C, D);
    signal current_state : multiplier_state := A;
    signal next_state : multiplier_state;
begin
    process(clk) is
    begin
        ...
    end process;

    ...
end;
```

b) Complete the waveform of *Figure 2*.

 


Figure 2: Clock and event input of the FSM.

2 Problem: Pipelining of FIR filters (50 %)

In this problem we are going to consider the so called pipelining technique applied to FIR digital filters (it doesn't matter if now you don't know what a FIR filter is). *Figure 3* shows the block diagram of a FIR filter (of memory two) in which the output y can be written as a combination of the current input x_0 and the two previous values of this input, x_1 and x_2 : $y = a*x_0 + b*x_1 + c*x_2$. It is worth noting that each *clock* period a new output is computed.

 


Figure 3: Block diagram of a FIR filter of memory two.

The VHDL description of this block diagram is listed below. Note that different signals have different lengths.

```

library ieee;
use ieee.std_logic_1164.all, ieee.numeric_std.all;

entity fir is
  port( clk : in std_logic;
        x  : in std_logic_vector(7 downto 0);
        y  : out std_logic_vector(7 downto 0));
end;

architecture arch of fir is
  signal x0,x1,x2 : signed(7 downto 0):=(others=>'0');
  constant a : signed(3 downto 0):=to_signed(1,4);
  constant b : signed(3 downto 0):=to_signed(-2,4);
  constant c : signed(3 downto 0):=to_signed(3,4);
  signal prod_a_x0,prod_b_x1,prod_c_x2,sum_1,sum :
    signed(a'length+x0'length-1 downto 0);

```

```

begin
  process(clk) is
  begin
    if rising_edge(clk) then
      x0<=signed(x);
      x1<=x0;
      x2<=x1;
      y<=std_logic_vector(resize(sum,y'length));
    end if;
  end process;

  prod_a_x0<=a*x0;
  prod_b_x1<=b*x1;
  prod_c_x2<=c*x2;
  sum_1<=prod_a_x0+prod_b_x1;
  sum<=sum_1+prod_c_x2;
end;

```

- a) Identify the critical path of *Figure 3*. Compute the maximum clock frequency f_{clk} at which the system can work. Consider the following delays:
- Clock to output delay, $t_{co}=8\text{ns}$.
 - Set-up time, $t_{su}=2\text{ns}$.
 - Multiplier delay, $t_{mult}=85\text{ns}$.
 - Adder delay, $t_{add}=45\text{ns}$.
- b) The clock frequency f_{clk} is fixed to 7MHz by the design constraints. Draw the block diagram and write the VHDL code that synthesize a new filter using the pipelining technique (i.e. shortening the critical path adding some registers) in order to work at $f_{clk} = 7\text{MHz}$. Compare the latency of this design with the previous one.
- c) Consider the new design (same delays as before): Identify the critical path. Compute the maximum clock frequency f_{clk} at which the system can work. If this frequency is lower than 10MHz propose another design.