

Code example: Product of two complex numbers

Jordi Bonet

iTIC <http://ocw.itic.cat>

March 2020

multiplier.vhd (1/6)

```
library ieee;
use ieee.std_logic_1164.all, ieee.numeric_std.all;

entity multiplier is
    generic (WIDTH: natural:=5);
    port( clk,reset : in std_logic;
          input_rdy : in std_logic;
          a_r,a_i,b_r,b_i: in signed(WIDTH-1 downto 0);
          p_r,p_i : out signed(2*WIDTH-1 downto 0));
end;

architecture arch of multiplier is
-- datapath
signal a_operand, b_operand : signed(WIDTH-1 downto 0);
signal pp, pp1, pp2, sum : signed(2*WIDTH-1 downto 0);

-- control section
signal a_sel,b_sel,
       pp1_ce, pp2_ce,
       sub, p_r_ce, p_i_ce : std_logic;

-- control section (finite state machine)
type multiplier_state is (step1, step2, step3, step4, step5);
signal current_state, next_state : multiplier_state;
```

multiplier.vhd (2/6)

```
begin
    -- datapath
    a_operand <= a_r when a_sel='0' else a_i;
    b_operand <= b_r when b_sel='0' else b_i;

    pp <= a_operand*b_operand;

    pp1_reg : process(clk) is
    begin
        if rising_edge(clk) then
            if pp1_ce='1' then
                pp1 <= pp;
            end if;
        end if;
    end process;

    pp2_reg : process(clk) is
    begin
        if rising_edge(clk) then
            if pp2_ce='1' then
                pp2 <= pp;
            end if;
        end if;
    end process;
```

multiplier.vhd (3/6)

```
sum <= pp1 + pp2 when sub='0' else pp1-pp2;

p_r_reg : process(clk) is
begin
  if rising_edge(clk) then
    if p_r_ce='1' then
      p_r <= sum;
    end if;
  end if;
end process;

p_i_reg : process(clk) is
begin
  if rising_edge(clk) then
    if p_i_ce='1' then
      p_i <= sum;
    end if;
  end if;
end process;
```

multiplier.vhd (4/6)

```
-- control section (implemented with a finite state machine)
state_reg : process(clk,reset) is
begin
  if reset='1' then
    current_state <= step1;
  elsif rising_edge(clk) then
    current_state <= next_state;
  end if;
end process;
```

multiplier.vhd (5/6)

```
next_state_logic : process(current_state, input_rdy) is
begin
    case current_state is
        when step1 =>
            if input_rdy = '0' then
                next_state <= step1;
            else
                next_state <= step2;
            end if;
        when step2 =>
            next_state <= step3;
        when step3 =>
            next_state <= step4;
        when step4 =>
            next_state <= step5;
        when step5 =>
            next_state <= step1;
    end case;
end process;
```

multiplier.vhd (6/6)

```
output_logic : process (current_state) is
begin
    a_sel <= '0'; b_sel <= '0';
    pp1_ce <= '0'; pp2_ce <= '0';
    sub <= '0'; p_r_ce <= '0'; p_i_ce <= '0';
    case current_state is
        when step1 =>
            pp1_ce <= '1';
        when step2 =>
            a_sel <= '1'; b_sel <= '1';
            pp2_ce <= '1';
        when step3 =>
            sub <= '1'; p_r_ce <= '1';
            b_sel <= '1';
            pp1_ce <= '1';
        when step4 =>
            a_sel <= '1';
            pp2_ce <= '1';
        when step5 =>
            p_i_ce <= '1';
    end case;
end process;

end;
```

multiplier_tb.vhd (1/5)

```
library ieee;
use ieee.std_logic_1164.all, ieee.numeric_std.all;

entity multiplier_tb is
    generic (t_WIDTH: natural:=5);
end;

architecture behav of multiplier_tb is
    signal t_a_r, t_a_i, t_b_r, t_b_i : signed(t_WIDTH-1 downto 0);
    signal t_p_r, t_p_i : signed(2*t_WIDTH-1 downto 0);
    signal t_clk, t_reset, t_input_rdy : std_logic;
begin
dut: entity work.multiplier(arch)
    generic map (WIDTH=>t_WIDTH)
    port map (clk=>t_clk, reset=>t_reset, input_rdy=>t_input_rdy,
              a_r=>t_a_r, a_i=>t_a_i, b_r=>t_b_r, b_i=>t_b_i,
              p_r=>t_p_r, p_i=>t_p_i);
```

multiplier_tb.vhd (2/5)

```
-- clock of the system
clk_process: process
begin
    t_clk <= '0';
    wait for 300 us;
    for i in 1 to 20 loop
        t_clk <= not t_clk;
        wait for 500 us;
    end loop;
    wait;
end process;

-- reset signal
reset_process: process
begin
    t_reset<='1';
    wait until rising_edge(t_clk);
    wait for 100 us;
    t_reset<='0';
    wait;
end process;
```

multiplier_tb.vhd (3/56)

```
-- input_rdy signal
input_rdy_process: process
begin
    t_input_rdy <='0';
    for i in 1 to 3 loop
        wait until rising_edge(t_clk);
    end loop;
    wait for 100 us;
    t_input_rdy <='1';
    wait until rising_edge(t_clk);
    wait for 100 us;
    t_input_rdy <='0';
    wait;
end process;
```

multiplier_tb.vhd (4/5)

```
-- (a_r, a_i) and (b_r, b_i) signals
ab_process: process
  procedure apply_test
    (p_t_a_r, p_t_a_i,p_t_b_r, p_t_b_i : in integer) is
  begin
    t_a_r<=to_signed(p_t_a_r,t_a_r'length);
    t_a_i<=to_signed(p_t_a_i,t_a_i'length);
    t_b_r<=to_signed(p_t_b_r,t_b_r'length);
    t_b_i<=to_signed(p_t_b_i,t_b_i'length);
  end procedure;
begin
  for i in 1 to 3 loop
    wait until rising_edge(t_clk);
  end loop;
  wait for 100 us;
  apply_test(2,1,1,3);
  wait;
end process;
```

multiplier_tb.vhd (5/5)

```
-- verification
assert_process: process
  procedure p_assert
    (p_t_p_r, p_t_p_i: in integer) is
  begin
    assert t_p_r=to_signed(p_t_p_r,t_p_r'length)
      report "bad_p_r_computation" severity warning;
    assert t_p_i=to_signed(p_t_p_i,t_p_i'length)
      report "bad_p_i_computation" severity warning;
  end procedure;
begin
  for i in 1 to 8 loop
    wait until rising_edge(t_clk);
  end loop;
  wait for 100 us;
  p_assert(-1,7);--5th rising_edge clk after input_rdy
  wait;
end process;

end architecture;
```

Makefile

```
#Top-Level Entity
TLE = multiplier_tb
STOP_TIME = 200ms
GHDL_SIM_OPT = --stop-time=$(STOP_TIME)
FORMAT = wave
EXTENSION = ghw
GHDL_SIM_RES = --$(FORMAT)=$(TLE).$(EXTENSION)
WAVEFORM_VIEWER = gtkwave

.PHONY: clean
all: compile elaborate run view
compile:
    ghdl -a *.vhd
elaborate:
    ghdl -e $(TLE)
run:
    ghdl -r $(TLE) $(GHDL_SIM_OPT) $(GHDL_SIM_RES)
view:
    $(WAVEFORM_VIEWER) $(TLE).$(EXTENSION)
clean:
    rm *.$(EXTENSION) work-obj93.cf *
```

gtkwave

