

Digital Systems - Mini AVR 2

Pere Palà - Alexis López

iTIC <http://itic.cat>

April 2016


VHDL Implementation of the Status Register

```
type status_reg is
  record
    Z : std_logic;
    C : std_logic;
  end record;
```

```
signal pr_SR,
      nx_SR    : status_reg;
```

Control Unit

 - ▶ Input: Present opcode
- ▶ Decode the instruction
- ▶ Generate signals:
 - ▶ Register write enable `reg_we`
 - ▶ Output multiplexer selection: decide if data written to register comes from:
 - ▶ The present opcode (such as LDI)
 - ▶ The ALU (such as ADC)
 - ▶ Generate d and r register addresses `d_reg`, `s_reg`
 - ▶ Indicate the desired operation to the ALU `alu_op`



VHDL Implementation of the Control Unit (1/2)

```
type    out_mux_type is (mux_alu,mux_lit);
signal out_mux : out_mux_type;

CONTROL : process(pr_op,pr_pc)
begin
    r_reg    <= (others => '-');      --Defaults
    d_reg    <= (others => '-');
    k        <= (others => '-');
    ALU_op   <= (others => '-');
    reg_we  <= '0';
    case pr_op(15 downto 12) is -- These bits are enough to
                                -- decide among our reduced
                                -- instruction set!
        when NOP => -----NOP Instruction
                      null;
        when LDI => -----LDI Instruction
                      d_reg    <= pr_op(7 downto 4);
                      out_mux <= mux_lit;
                      k        <= pr_op(11 downto 8) & pr_op(3 downto 0);
                      reg_we <= '1';
    end case;
end process;
```

VHDL implementation of the Control Unit (2/2)

```
when MOV => -----MOV Instruction
    r_reg    <= pr_op(3 downto 0); --Source register
    d_reg    <= pr_op(7 downto 4); --Destination register
    out_mux <= mux_alu;
    reg_we  <= '1';           --Enable register write
    ALU_op   <= ALU_MOV;


when ADC => -----ADC Instruction
    r_reg    <= pr_op(3 downto 0);
    d_reg    <= pr_op(7 downto 4);
    out_mux <= mux_alu;
    reg_we  <= '1';           --Enable register write
    ALU_op   <= ALU_ADC;

when others =>
    null;
end case;
end process;

constant ALU_MOV : std_logic_vector(2 downto 0) := "010";
constant ALU_ADC : std_logic_vector(2 downto 0) := "001";
```

The ALU: Arithmetic and Logic Unit

 - ▶ Inputs
 - ▶ Operands `alu_in_a`, `alu_in_b`
 - ▶ Operation code `alu_op`
 - ▶ Status register (for carry) `pr_SR`
- ▶ Outputs
 - ▶ Operation result `alu_out`
 - ▶ Updated status register `nx_SR`




VHDL implementation of the ALU

```
ALU : process(alu_op,alu_in_a,alu_in_b,pr_SR,add_temp)
begin
    nx_SR <= pr_SR;      --by default, preserve status register
    add_temp <= (others => '-');
    case alu_op is
        when ALU_MOV  => -----MOV: in_b --> out
            alu_out <= alu_in_b;
        when ALU_ADC   => -----ADC: Carry in/out
            add_temp <= std_logic_vector(          --auxiliar SLV(9..0)
                unsigned('0' & alu_in_a & '1') +
                unsigned('0' & alu_in_b & pr_SR.C));  --Carry In
            alu_out <= add_temp(8 downto 1);
            nx_SR.C <= add_temp(9);                  --Update Carry Flag
            if add_temp(8 downto 1) = x"00" then --Update Zero Flag
                nx_SR.Z <= '1';
            else
                nx_SR.Z <= '0';
            end if;
        when others => -----Should not happen
            alu_out <= (others => '-');           --Don't care
    end case;
end process;
```

Register Data-In Multiplexer

 - ▶ Decide which data has to be stored in one of the registers
 - ▶ Data from the ALU, as in ADC or MOV instructions
 - ▶ Data from the opcode, as in the LDI instruction




VHDL implementation of the Register Multiplexer

```
MUX : process(out_mux, alu_out, k)
begin
  case out_mux is
    when mux_alu => nx_reg <= alu_out;
    when mux_lit  => nx_reg <= k;
    when others    => nx_reg <= (others => '-');
  end case;
end process;
```

Synchronous Elements

 - ▶ Registered signals
 - ▶ Program counter pr_pc
 - ▶ Stauts register pr_SR



VHDL implementation of the Synchronous Elements

```
process(clk,reset) --Synchronous elements
begin
  if reset='1' then          --Initialize Processor
    pr_pc <= (others => '0');
    pr_SR.C <='0';
    pr_SR.Z <='0';
  elsif (rising_edge(clk)) then
    pr_pc      <= nx_pc;
    pr_SR      <= nx_SR;
  end if;
end process;

nx_pc    <= std_logic_vector(unsigned(pr_pc) + 1);
```

Whole Processor

- ▶ Entity

```
entity mini_avr_01 is
  port (
    clk      : in  std_logic;
    reset   : in  std_logic;
    -- Let's have some registers as outputs :
    r16     : out std_logic_vector( 7 downto 0);
    r17     : out std_logic_vector( 7 downto 0)
  );
end entity;
```

- ▶ Auxiliar signals for debugging

```
r16 <=regs(0);
r17 <=regs(1);
debug_carry <= pr_SR.C;
debug_zero  <= pr_SR.Z;
```

Simulation

