

Digital Systems - 2

Pere Palà - Alexis López

iTIC <http://itic.cat>

February 2016

Numeric Basics

- ▶ Coding of numeric information:
 - ▶ Decimal system: 37_{10} means $3 \times 10^1 + 7 \times 10^0$.
 - ▶ Decimal system: 203_{10} means $2 \times 10^2 + 0 \times 10^1 + 3 \times 10^0$.
 - ▶ $37_{10} = 1 \times 2^5 + 0 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$.
 - ▶ $37_{10} = 100101_2$.
-
- ▶ n bits : $0 \dots 2^n - 1$.
 - ▶ To represent $0 \dots N - 1$ we need $\log_2 N$ bits.

Unsigned Integers

- ▶ Declaration: `signal s_unsig : unsigned(3 downto 0);`

Assignments

Legal: `s_unsig <= "1110";`

Illegal: `s_unsig <= 0;`

Legal: `s_unsig_dest <= s_unsig+1;`

Conversions

- ▶ `my_slv <= std_logic_vector(my_unsigned);`


- ▶ `my_unsigned <= unsigned(my_slv);`

A VHDL type test example

```
library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity num_tb is
end num_tb ;

architecture behav of num_tb is
    signal s_logic : std_logic_vector(3 downto 0) ;
    signal s_unsig : unsigned(3 downto 0);
begin
    s_logic <= std_logic_vector(s_unsig);
    process
        begin
            s_unsig <= "1110";
            wait for 1 sec;
            s_unsig <= s_unsig+1;
            wait for 1 sec;
            s_unsig <= s_unsig+1;
            wait for 1 sec;
            s_unsig <= s_unsig+1;
            wait for 1 sec;
            wait;
        end process ;
end behav ;
```

 

Assignments

Resizing an unsigned integer

```
signal a : unsigned(3 downto 0);  
signal b : unsigned(7 downto 0);  
  
b <= "0000" & a;  
a <= b(3 downto 0);
```

- ▶ Concatenation operator: &
- ▶ Only in the right hand of assignments!

Alternate way


```
signal a : unsigned(3 downto 0);  
signal b : unsigned(7 downto 0);  
  
b <= resize(a,8);  
a <= resize(b,4);
```

Adding Unsigned Integers

Algorithm

1	1	1	1	1	0	0	0	
	0	0	1	1	1	0	0	1
	1	1	0	0	1	1	0	0
1	0	0	0	0	0	1	0	1

Implementation

 

`c_out <= (a and b) or (c_in and (a xor b));` This is slooow!

Adders

Fast-carry-chain adder



- ▶ Carry kill: $k_i = \text{not } x_i \text{ and not } y_i$
- ▶ Carry propagate: $p_i = x_i \text{ xor } y_i$
- ▶ Carry generate: $g_i = x_i \text{ and } y_i$

```
si = pi xor c_in;  
co = gi or pi and c_in;
```

Carry-lookahead generator

- ▶ Example for 4 bits
  
```
c4 = g3 or (p3 and g 2)  
    or (p3 and p2 and g1)  
    or (p3 and p2 and p1 and g 0)  
    or (p3 and p2 and p1 and p0 and c0)
```



Adder in VHDL

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
...  
  signal a,b,s : unsigned(3 downto 0);  
...  
  s <= a + b;
```

- ▶ Do not specify the equations!
- ▶ The software automatically detects the best type of adder.
- ▶ This is dependent on the technology and the requirements of the designer (speed, area).

Adder with Carry Out

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
...
signal a,b,s : unsigned(7 downto 0);
signal temp  : unsigned(8 downto 0); --MSB:carry
signal c_out : std_logic;
...
temp  <= ('0' & a) + ('0' & b); -- compute sum with 9 bits
s     <= temp(7 downto 0);      -- true sum is in LSBs
c_out <= temp(8);              -- carry is the MSB
```

Comparing unsigned integers

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity ...
    port temp      : in  unsigned(7 downto 0);
    port target    : in  unsigned(7 downto 0);
    port heat      : out std_logic;
architecture ...
    heat <= '1' when temp < target - 5 else '0';
```

- ▶ Synthesis software will implement the function.

Comparing unsigned integers

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity ...  
  port temp      : in  unsigned(7 downto 0);  
  port target    : in  unsigned(7 downto 0);  
  port heat      : out std_logic;  
architecture ...  
  heat <= '1' when temp < target - 5 else '0';
```

- Synthesis software will implement the function.

