

# Digital Systems - 4

Pere Palà - Alexis López

iTIC <http://itic.cat>

February 2016

# Shift Register

```
library ieee; use ieee.std_logic_1164.all;

entity shift_reg is
port( serial_in, clk, shift_ena : in std_logic;
      serial_out : out std_logic);
end shift_reg;

architecture behav of shift_reg is
  signal q: std_logic_vector(3 downto 0);
begin
  -- clock process
  process(clk)
  begin
    if rising_edge(clk) then
      if shift_ena = '1' then
        q(3 downto 1) <= q(2 downto 0);
        q(0) <= serial_in;
      end if;
    end if;
  end process;
  -- concurrent assignment
  serial_out <= q(3);
end behav;
```

# Shift Register Test Bench 1/3

```
library ieee; use ieee.std_logic_1164.all;
entity sr_tb is end sr_tb ;

architecture behav of sr_tb is
component my_sr port(
    serial_in : in std_logic;
    clk        : in std_logic;
    shift_ena : in std_logic;
    serial_out : out std_logic);
end component;
for dut : my_sr use entity work.shift_reg;

signal serial_in :std_logic;
signal clk       :std_logic;
signal shift_ena :std_logic;
signal serial_out:std_logic;
begin
dut: my_sr port map(
    serial_in  => serial_in,
    clk        => clk,
    shift_ena  => shift_ena,
    serial_out => serial_out);
```

## Shift Register Test Bench 2/3

```
clk_process: process
begin          --the clock process
    clk <= '0';
    wait for 5 ns;
    for i in 1 to 20 loop
        clk <= not clk;
        wait for 5 ns;
    end loop;
    wait;
end process clk_process;

shift_ena <='1', --one way to set signal
           '0' after 50 ns, '1' after 60 ns;

stim_process:process
begin          --another way
    serial_in <= '1';
    wait for 20 ns;
    serial_in <='0';
    wait for 10 ns;
    serial_in <='1';
    wait for 90 ns;
    wait;          --wait forever
end process stim_process;
end behav ;
```

# Shift Register Test Bench 3/3

```
$ ghdl -a sr.vhd
$ ghdl -a sr_tb.vhd
$ ghdl -e sr_tb
$ ghdl -r sr_tb --vcd=sr.vcd
$ gtkwave sr.vcd
```



# Counter

```
library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity counter is
port( clk, reset : in std_logic;
      tc          : out std_logic);
end counter;

architecture behav of counter is
  signal q: unsigned(3 downto 0);
begin
  process(clk) -- clock process
  begin
    if rising_edge(clk) then
      if reset = '1' then
        q <= "0000";
      elsif q = 9 then
        q <= "0000";
      else
        q <= q + 1;
      end if;
    end if;
  end process;
  tc <= '1' when q = "0000" else '0';
end behav;
```

# Counter Test Bench 1/2

```
...
begin
dut: my_counter port map...

clk_process: process
begin          --the clock process
  clk <= '0';
  wait for 5 ns;
  for i in 1 to 40 loop
    clk <= not clk;
    wait for 5 ns;
  end loop;
  wait;
end process clk_process;

reset <='1', '0' after 10 ns;
end behav ;
```

## Counter Test Bench 2/2

```
$ ghdl -a counter.vhd
$ ghdl -a counter_tb.vhd
$ ghdl -e counter_tb
$ ghdl -r counter_tb --vcd=counter.vcd
$ gtkwave counter.vcd
```

