

# Digital Systems - 7


Pere Palà - Alexis López

iTIC <http://itic.cat>

March 2016

## Register Transfer Level Description (1/2)


- ▶ Our example...

 


- ▶ ... is a specific case of ...

## Register Transfer Level Description (2/2)

► General Synchronous System

 


# Synchronous Timing

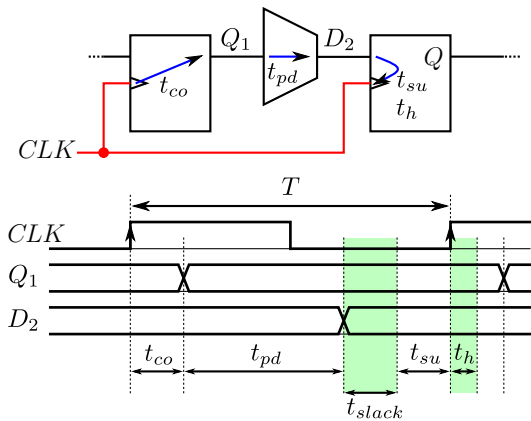

- ▶  $t_{co}$ ,  $t_{pd}$  and  $t_{su}$  ns are device-dependent.
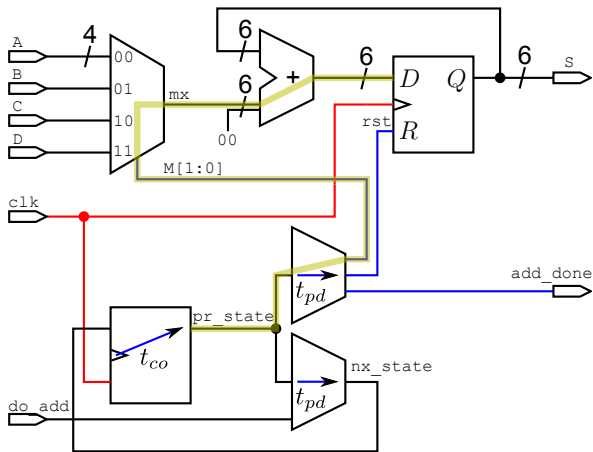
## Critical Path

- ▶ The control path adds (a significant amount of) delay.
- ▶ Critical path: Combinational path between register with the longest delay.



# Timing Constraints

## Views

- ▶ First interpretation:  $T > t_{co} + t_{pd} + t_{su}$
- ▶ Sets a limit on the maximum clock frequency.
- ▶ Second interpretation:  $t_{pd} < T - t_{co} - t_{su}$
- ▶ Sets a limit on the maximum combinational delay.


## Solution

- ▶ Choose a better implementation technology.
- ▶ Trade area (complexity) for speed.
- ▶ Pipelining: Breaking the longest combinational delay in parts, using intermediate registers. This adds some clocks of latency.

# Clock Skew (1/2)
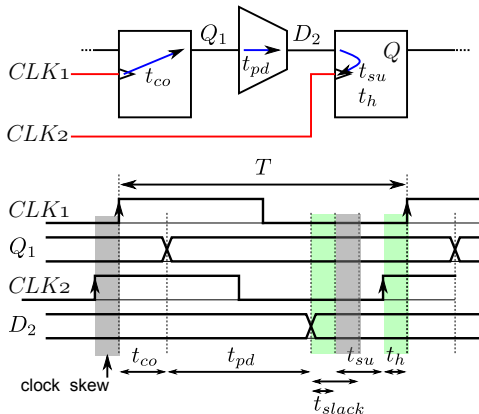
## Problem

- ▶ Clock net is not able to deliver edges which are exactly synchronous.
  - ▶ At the board level.
  - ▶ And even inside the FPGA.



# Clock Skew (2/2)

## Solution

- ▶ Reduce clock to accommodate skew.
- ▶ Suitable clock distribution network.
- ▶ Line length equalization.
- ▶ Inserting delays in clock network.




# Outside Connections

- ▶ Additional delays at connections
  - ▶ Pin delays.
  - ▶ Wiring delays.
- ▶ Exactly the same timing rules.
- ▶ Inputs and outputs may be registered to avoid extra delay in the critical path
 
## Asynchronous Inputs


- ▶ External inputs may change at any time.
  - ▶ May violate setup or hold time constraints.
  - ▶ Unavoidable!
- ▶ The output of the flip-flop has an exponential evolution with time:



- ▶ Destination registers may interpret the signal differently as they are not clearly '1' or '0': System failure.
- ▶ Allow sufficient time for the flip-flop to stabilize.

# Synchronizer

## Two-stage synchronizer

 

- ▶ Normal case: Input is delayed by one extra clock period.
- ▶ First flip-flop has one clock period to stabilize.
- ▶ Only affects the second flip-flop: No incoherent signals in the system.

# Slow Inputs and Bouncing

## Hardware Solutions

- ▶ S-R flip-flop with SPDT switch.
- ▶ RC filtering.
- ▶ Schmitt Trigger.
  
- ▶ Pros: No digital resources spent.
- ▶ Cons: Components, connections, reliability. Fixed solution.

## Software Solutions

- ▶ Take successive samples of input signal.
- ▶ Look for  $n$  ( $n > 1$ ) successive samples which are different than the current state. Signal the change.
  
- ▶ Pros: No additional components. Only FPGA. Configurable.
- ▶ Cons: Consumes digital resources.