

Systems Engineering

Oscillators

Pere Palà

iTIC <http://itic.cat>


v1.0 April 2013

Oscillators

- ▶ Objective: generate a pure tone $A(\cos\omega t + \phi)$
- ▶ (or a square wave)
- ▶ Oscillation frequency
- ▶ Frequency drift
- ▶ Oscillator jitter
- ▶ Power
- ▶ Fixed or variable-frequency
- ▶ Dependence of frequency (ppm) with
 - ▶ Power supply
 - ▶ Load variations
 - ▶ Age
 - ▶ ...


Oscillator Stability

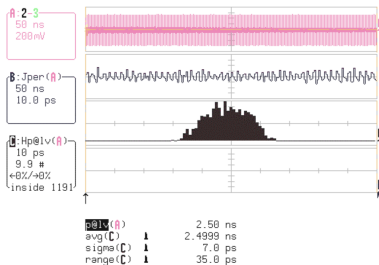- ▶ Long-term stability: ppm
- ▶ Short-term stability: jitter



Source: Cardinal Components Inc. A.N. 1006

Jitter in the time-domain


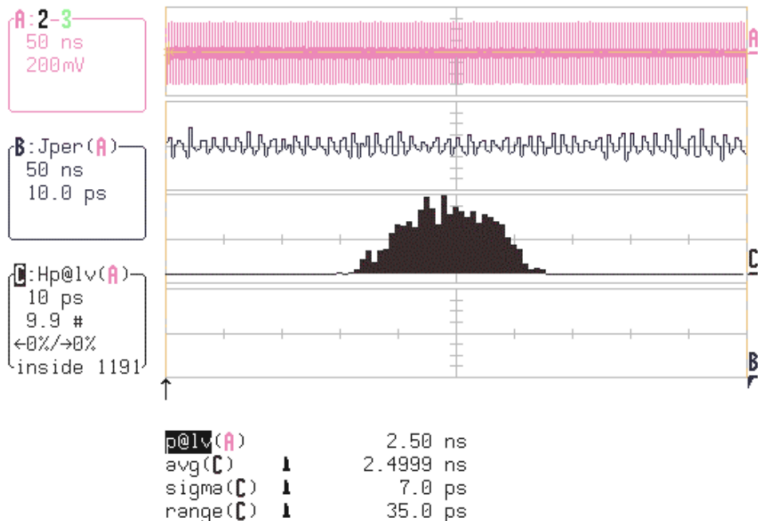


Source: Cardinal Components Inc. A.N. 1006

Jitter in the frequency-domain



Phase Noise

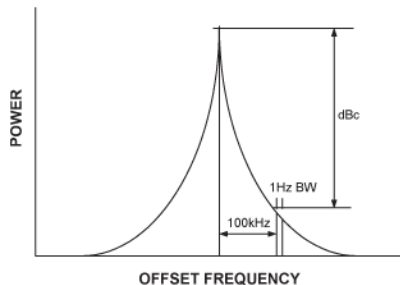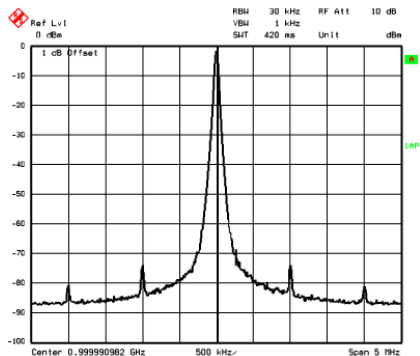- ▶ Phase Noise (dBc @ 100 kHz)
- ▶ Different phase-noise profiles








Oscillator Theory

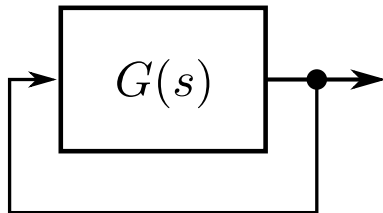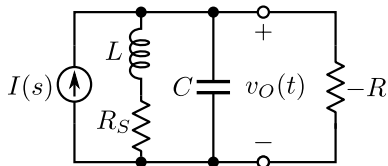- ▶ Negative resistance approach
- ▶ Unity feedback approach
- ▶ Both approaches are exactly equivalent
 - ▶ But some circuit structures are easier to understand with one or the other



Negative resistance oscillators


- ▶ Negative resistance approach

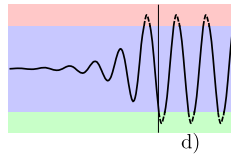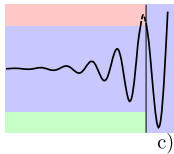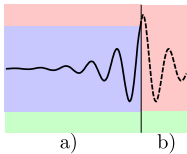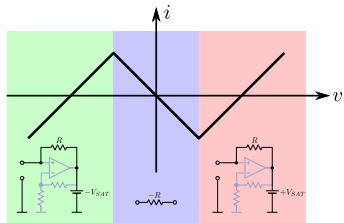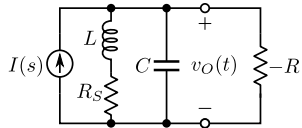

d)

Feedback oscillators


- ▶ $G(\omega) = 1$ approach

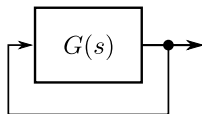




- ▶ These are two (!) conditions:
 - ▶ Magnitude = 1
 - ▶ Phase = 0

Feedback oscillators

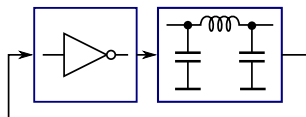- ▶ A popular approach with inverting gain element



- ▶ Detailed circuit analysis


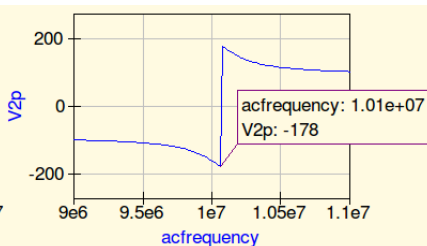
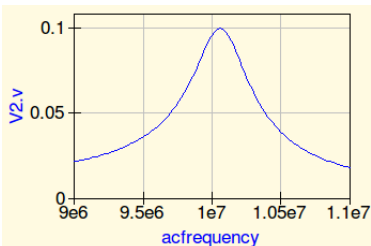
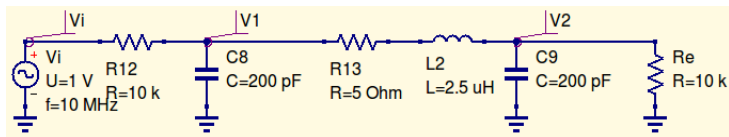


Resonators

- ▶ LC circuits
 - ▶ $Q \sim 50$
 - ▶ Bad stability
- ▶ Ceramic resonators
 - ▶ $Q \sim 50$
 - ▶ stability 500 ppm
- ▶ Crystals
 - ▶ $Q \sim 50000$
 - ▶ stability better than 20 ppm
- ▶ Others
 - ▶ Transmission lines
 - ▶ Ceramic coaxial resonators
 - ▶ Cavities
 - ▶ ...

Crystals


- ▶ Piezoelectric material
- ▶ AT-cut

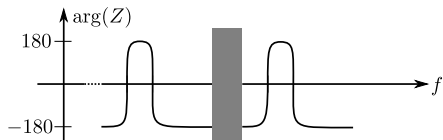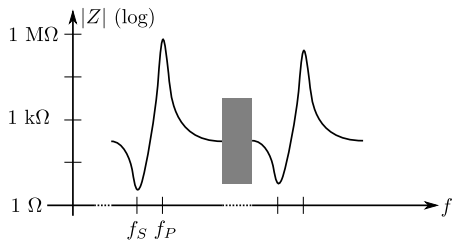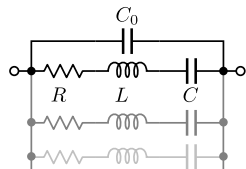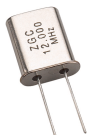

Crystals

- ▶ Equivalent circuit 10 MHz crystal
 - ▶ $R=12\ \Omega$, $C=24\ \text{fF}$,
 $C_0=6\ \text{pF}$ $L=105\ \text{mH}$
 - ▶ $Q=50000$
- ▶ Equivalent circuit 12 MHz crystal
 - ▶ $R=10\ \Omega$, $C=9\ \text{fF}$,
 $C_0=4\ \text{pF}$, $L=19\ \text{mH}$
 - ▶ $Q=130000$

Crystal modules

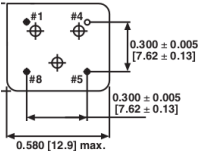

ENABLE/DISABLE FUNCTION	
INPUT (PIN 1)	OUTPUT (PIN 5)
OPEN	ENABLE
$V_{IH} \geq 2.2 V_{DC}$	ENABLE

PIN	CONNECTION
#1	N.C.
#4	GND
#5	OUTPUT
#8	V_{DD}

