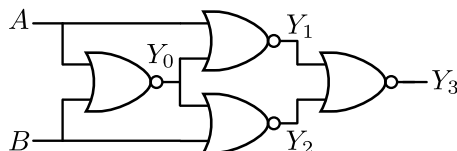


Introducció als Sistemes Digitals

Prova Parcial. 7 de novembre de 2018

Temps per a la resolució: 2 hores. Publicació de resultats: 21 de novembre.

- (10 points) Cryptography uses ciphers to protect secrets. Substitution ciphers are one of the simplest methods to encrypt a message that started to be used 2500 years ago. The Atbash cipher is a substitution cipher that maps the alphabet to its reverse. We are going to use this cipher to encrypt a decimal digit I that takes values 0-9 coded with 4 bits $I_3I_2I_1I_0$ using the BCD representation. The encrypted decimal digit A is also coded with 4 bits $A_3A_2A_1A_0$ using the BCD representation. The Atbash cipher encrypts each of these digits $I = \{0, 1, 2, 3, 4, 5, 6, 7, 8, 9\}$ in the following $A = \{9, 8, 7, 6, 5, 4, 3, 2, 1, 0\}$. For example, $I = 2$ will be encrypted into $A = 7$.
 - (1 point) Determine the truth table that relates the inputs $I_3I_2I_1I_0$ with the outputs $A_3A_2A_1A_0$.
 - (2 points) Use the Karnaugh map to simplify the Boolean expression of each output.
 - (2 points) Implement the Atbash cipher with two-input logic gates AND and OR (and NOT). Count the total number of gates (ignore the NOT gates).
 - (2 points) Consider the sequence of digits 20181107. Compute the ciphered sequence of digits. Repeat the computation considering that, due to a malfunction, the input I_3 is always high.
 - (3 points) Finally, design the decipherer that will turn back the digit A to its original value I . Use the notation $A_3A_2A_1A_0$ for the input of the decipherer, and $O_3O_2O_1O_0$ for its output. Considering the malfunction of the previous question, which will be the sequence of digits O when at the input we have 20181107?
- (6 punts) Una de les opcions per a construir una porta XNOR a partir de portes NOR és la següent.



Representeu el cronograma dels senyals Y_0 , Y_1 , Y_2 i Y_3 quan les entrades AB segueixen la seqüència de valors '01', '00', '10' i '00'. Primer ignoreu l'existència de retard i després considereu un temps de propagació Δ per a totes les portes.

- (8 punts) Considereu $Y = f(I_2, I_1, I_0)$ que val '1' quan $3 \leq 4I_2 + 2I_1 + I_0 \leq 5$. Implementeu Y amb les següents restriccions.
 - (1 punt) Usant només un 8:1 MUX.
 - (2 punts) Usant un 4:1 MUX i portes NOT si cal. Considereu totes les opcions.
 - (3 punts) Usant un 2:1 MUX i portes lògiques si cal. Considereu totes les opcions.
 - (2 punts) Usant un 1:8 DEMUX i portes lògiques si cal. Realitzeu dues implementacions diferents.