
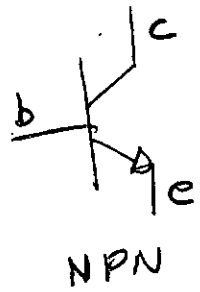



• BJT (Bipolar junction transistor)

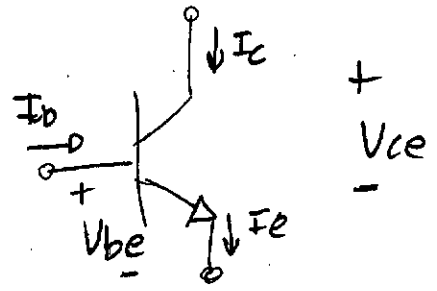

• Basic functional description (NPN)



• ACTIVE ZONE MODEL

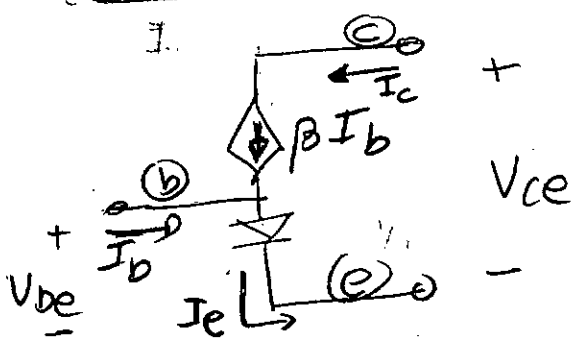


ACTIVE ZONE CONDITIONS
 $V_{ce} > 0.2 \text{ Volt}$
 $I_b > 0$

$\beta = \text{Current gain (10 to 500)}$

$$I_c = \beta I_b$$

$$I_e = (\beta + 1) I_b$$

• EXAMPLE

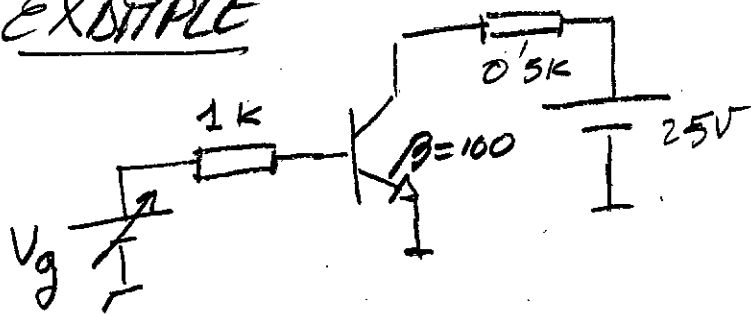

Analog Systems
28/2/2012 (2)
TRANSISTOR

• If the BJT operates in active zone

$$I_b = \frac{V_g - 0.7}{1} \Rightarrow I_c = 100 \left(\frac{V_g - 0.7}{1} \right) \Rightarrow$$
$$V_{ce} = 25 - 0.5 I_c$$


• If $V_g = 4V \Rightarrow I_b = 0.3mA \Rightarrow I_c = 30mA \Rightarrow$
 $V_{ce} = 25 - 0.5 \cdot 30 = 10 \text{ Volt} \Rightarrow 0k$

• If $V_g = 5V \Rightarrow I_b = 4.3mA \Rightarrow I_c = 430mA \Rightarrow$
 $V_{ce} = 25 - 0.5 \cdot 430 = -190 \text{ Volt} \Rightarrow \text{NOT IN ACTIVE ZONE}$

• If $V_g = 0.2 \text{ Volt} \Rightarrow I_b = -0.5mA \Rightarrow \text{NOT IN ACTIVE ZONE}$

BASIC CIRCUITS

①

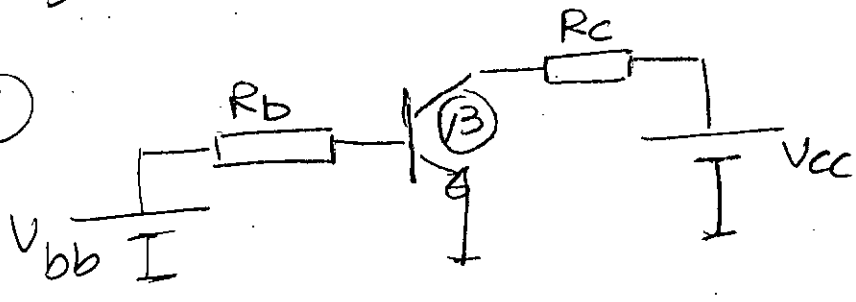

BASE CIRCUIT


$$\frac{V_{bb} - 0.7}{R_b} = I_b$$

COLLECTOR CIRCUIT

$$V_{cc} - I_c R_c = V_{ce}$$

ACTIVE ZONE


$$I_c = \beta I_b$$

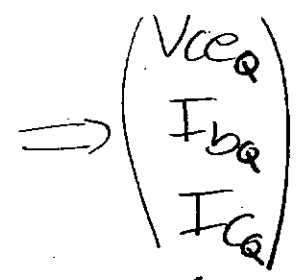


VALID RESULTS ONLY IF $V_{ceQ} > 0.2$, $I_{bQ} > 0$


GRAPHS

• BASE CIRCUIT

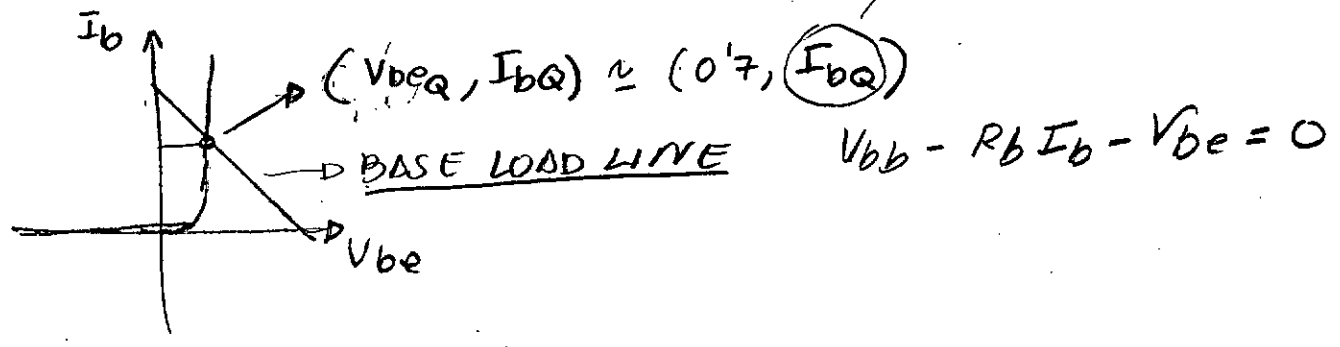

• COLLECTOR CIRCUIT

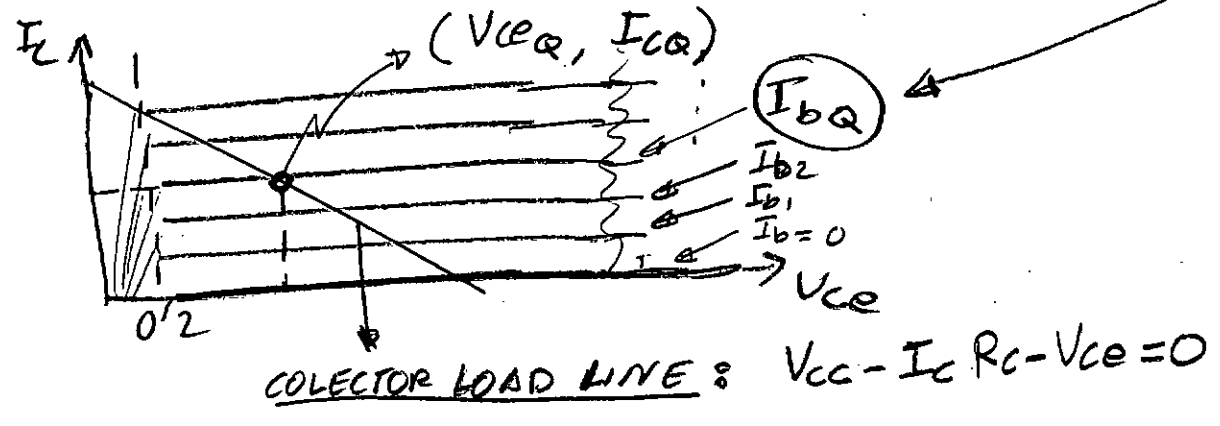

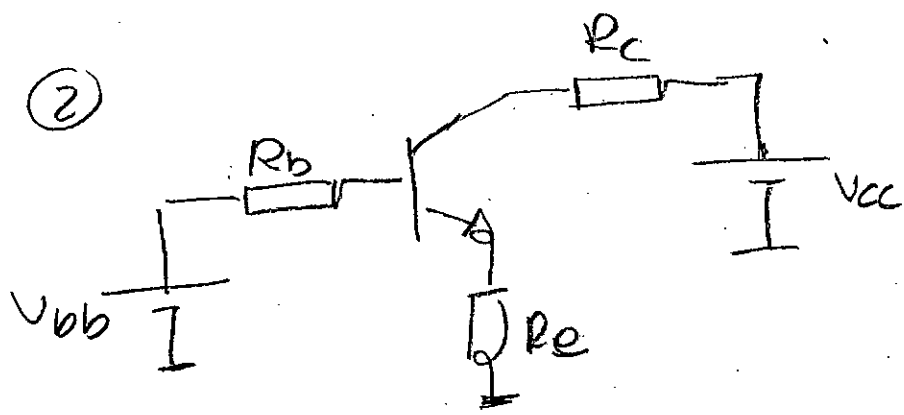

BASE CIRCUIT: $V_{bb} - I_b R_B - V_{be} - I_e R_e = 0$

COLLECTOR CIRCUIT: $V_{cc} - I_c R_c - V_{ce} - I_e R_e = 0$

ACTIVE : $V_{be} = 0.7$

$I_c = \beta I_b$

$I_e = (\beta + 1) I_b$

$\{ V_{ceq}, I_{cq}, I_{bq}, I_{eq}, V_{be} = 0.7 \}$ can be obtained

VALID RESULTS IF $V_{ceq} > 0.2$ and $I_{bq} > 0$

It can be obtained:


$V_{bb} - (R_b + (\beta + 1) R_e) I_b - V_{be} = 0$

$V_{cc} - (R_c + (\frac{\beta + 1}{\beta}) R_e) I_e - V_{ce} = 0$


The equations are similar than the ones of the first circuit (the slopes of the

load lines are different)

(3)

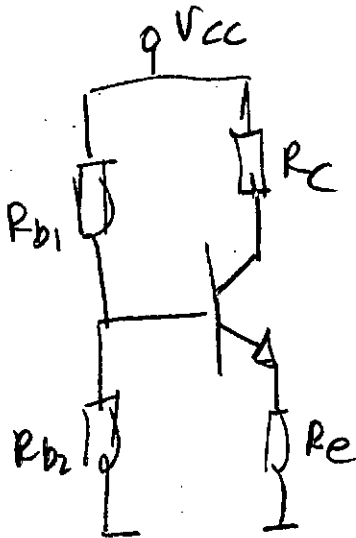

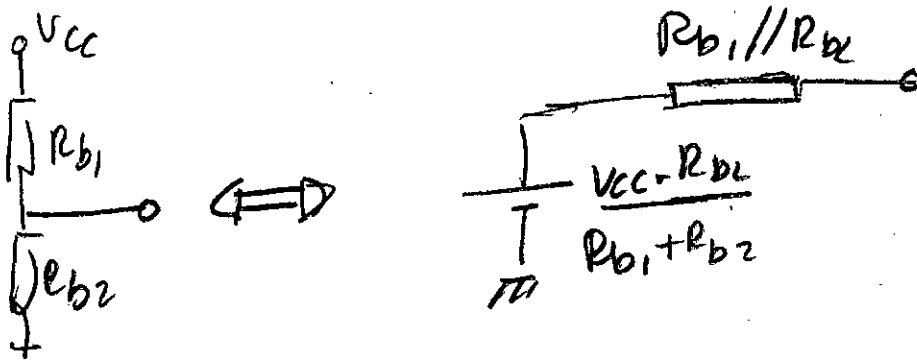A Thevenin equivalent circuit can be used:




Then the same circuit as in (2) is obtained.

but only one DC source is needed to determine Q point.

Q DEPENDENCY ON β

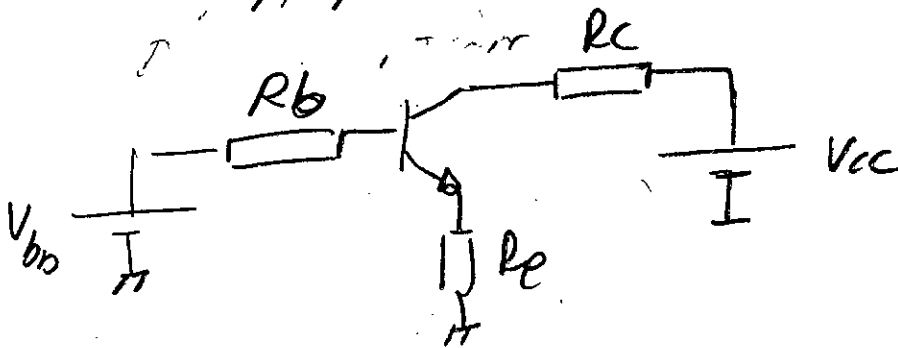- ① β is not known for a single BJT
(statistical distribution on manufacturing)
- ② V_{ceq} , I_{cq} & h must be determined, without ^{any} dependency on β .
- ③ This performance is achieved using R_e .



$$\begin{cases} V_{bb} - I_b R_b - 0.7 - (\beta + 1) R_e I_b = 0 \\ V_{cc} - \beta I_b - V_{ce} - (\beta + 1) I_b R_e = 0 \end{cases} \Rightarrow$$

$$I_{bq} = \frac{V_{bb} - 0.7}{(\beta + 1) R_e + R_b}$$

$$I_{cq} = \beta \frac{(V_{bb} - 0.7)}{(\beta + 1) R_e + R_b}$$

$$V_{ceq} = V_{cc} - (\beta R_c + (\beta + 1) R_e) \frac{(V_{bb} - 0.7)}{(\beta + 1) R_e + R_b}$$

If:

① β is large enough ($\beta > 20$)

② $(\beta + 1) R_e \gg R_b$

$$I_{CQ} \approx \frac{V_{bb} - 0.7}{R_e}$$

$$V_{CEQ} \approx V_{CC} - (\beta R_C + (\beta + 1) R_e) \cdot \frac{V_{bb} - 0.7}{(\beta + 1) R_e} \approx$$

$$\approx V_{CC} - \left(\frac{R_C + R_e}{R_e} \right) \cdot (V_{bb} - 0.7) =$$


$\frac{\beta}{\beta + 1} \approx 1$

$$V_{CEQ} = V_{CC} - \left(1 + \frac{R_C}{R_e} \right) (V_{bb} - 0.7)$$

I_{CQ}, V_{CEQ} have no dependency on β

BUT SATURATION ZONE

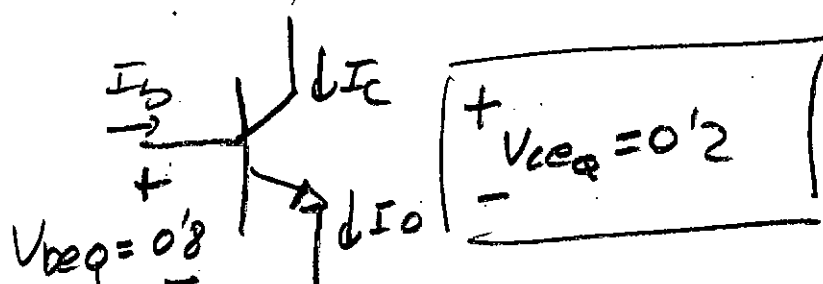If I_{CQ} is large enough, V_{CEQ} falls to zero (in fact falls to $V_{CEQ} = 0.2$)



- V_{CEQ} is greater than in active zone
- $I_{CQ} \neq \beta I_{BQ}$


The BJT is like a switch in its ON STATE
(I_C is flowing and $V_{CE} \approx 0$)

- This zone is used in logic (digital) circuits
- A BJT comes to the saturation zone if $(R_C + R_E)$ is large, and if I_B is also large

BJT CUT OFF ZONE

$$\left. \begin{aligned} I_b = 0 \\ V_{ce} > 0 \end{aligned} \right\} \Rightarrow I_c = 0, I_e = 0$$

The BJT behaves like a switch in its OFF STATE, that is

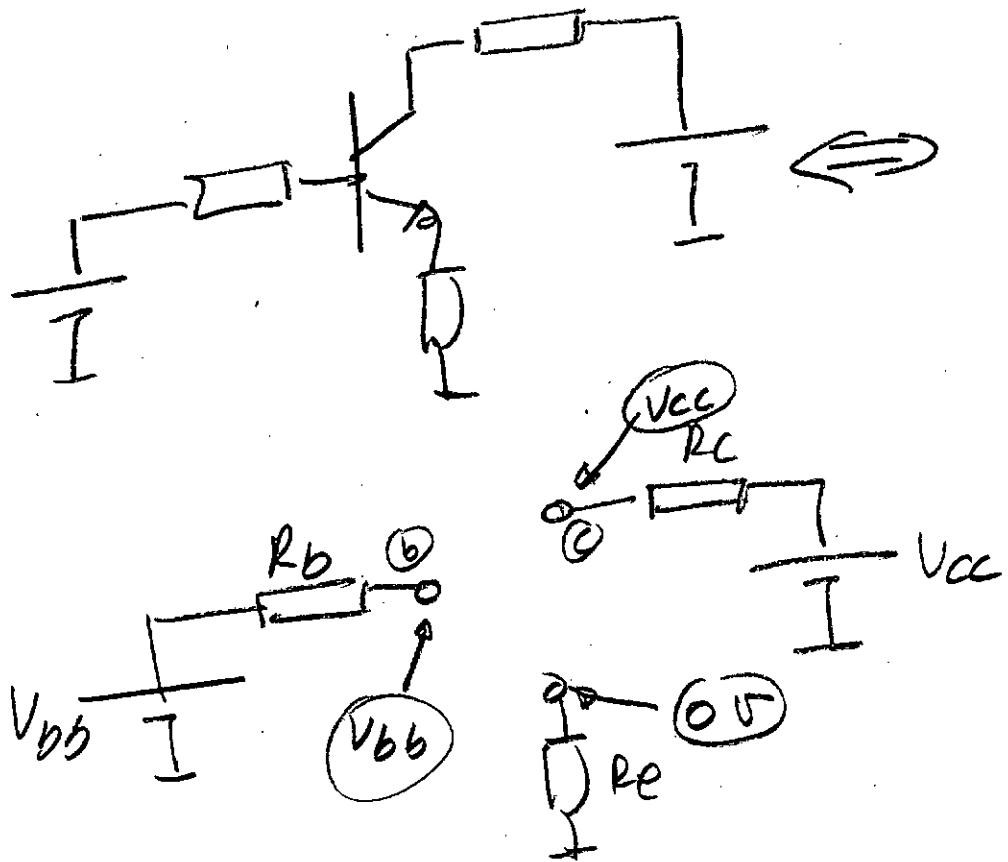

THIS IS:

$$V_{be} = V_{bb}$$

$$V_{ce} = V_{cc}$$

$$I_c = I_e = I_b = 0$$



A BJT comes to the OFF STATE if $V_{bb} < 0.7$

BJT
Small signal model

Analog Systems

15/3/2022 | 10

TRANSMITTER

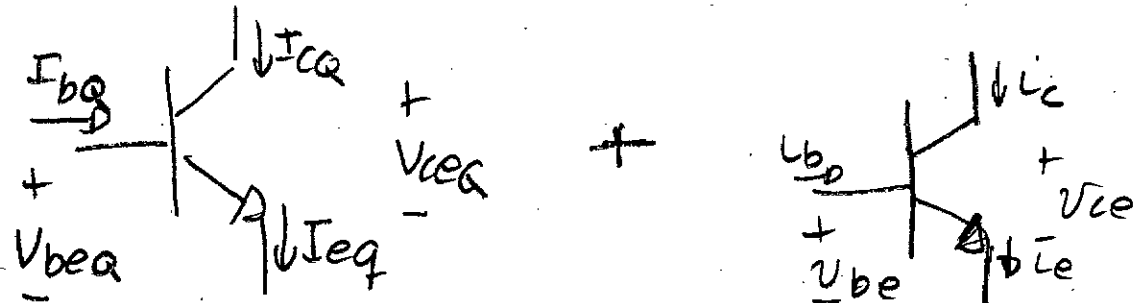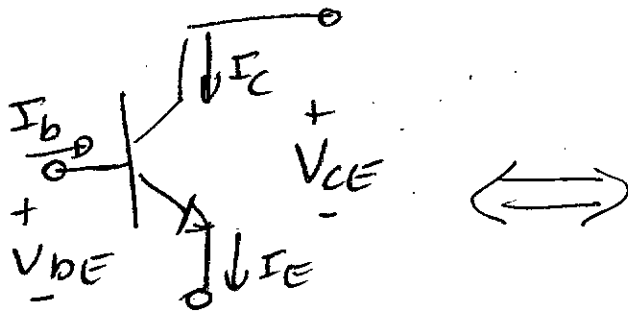


Q MODEL

Small signal model

(lower case means Δ , that is $i_b \triangleq \Delta I_b \dots$)

The small signal model is based on Taylor's series of $i_b, i_c, i_e, v_{be}, v_{ce} \dots$

It can be shown:

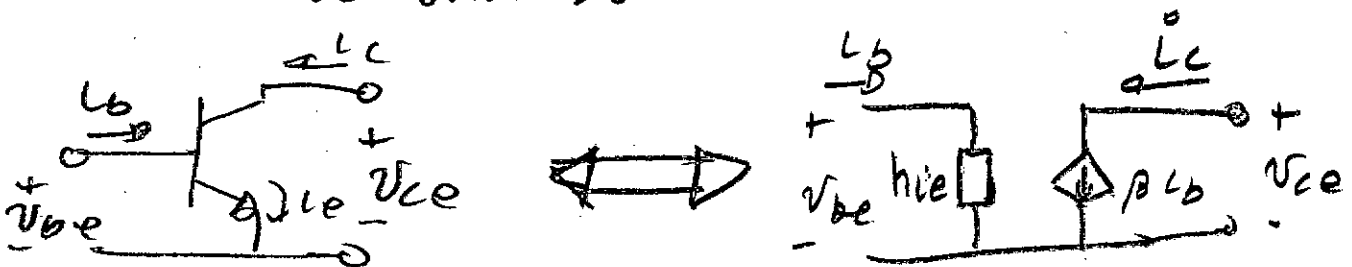


hie calculus

Analog Systems

15/3/2012 11

Transistor

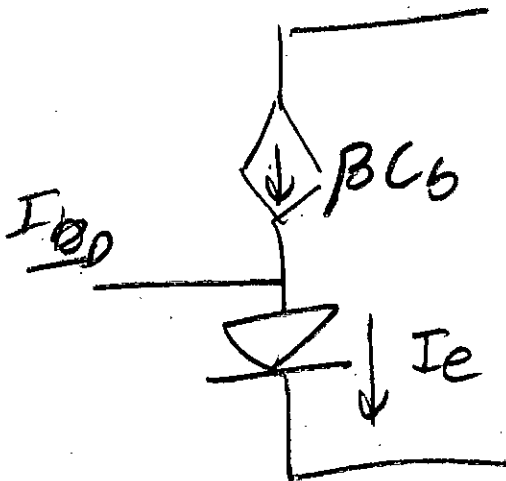

$$I_e = I_b + \beta I_b = (\beta + 1) I_b = I_s \left(e^{\frac{V_{be}}{V_T}} - 1 \right)$$

$$I_b = \frac{1}{\beta + 1} \cdot I_s \left(e^{\frac{V_{be}}{V_T}} - 1 \right)$$

↑
TAYLOR'S SERIES



$$h_{ie} = \left. \frac{\partial I_b}{\partial V_{be}} \right|_Q \cdot V_{be} \Rightarrow$$

$$h_{ie} = \left(\frac{1}{\beta + 1} \cdot \frac{1}{V_T} \cdot I_s e^{\frac{V_{be}(Q)}{V_T}} \right) \cdot V_{be} \Rightarrow$$

$$h_{ie} = \frac{1}{V_T} \cdot I_b(Q) \cdot V_{be} \Rightarrow$$

$$\frac{V_{be}}{h_{ie}} = h_{ie} = \frac{V_T}{I_b(Q)}$$

hence

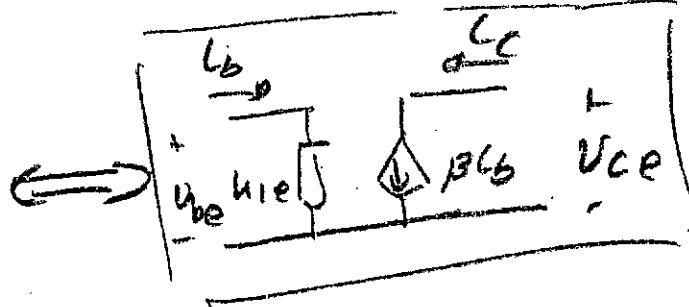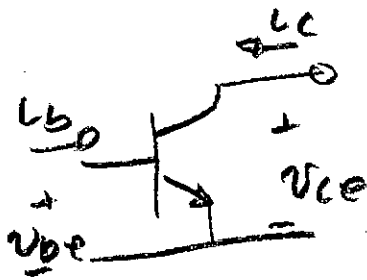

$$h_{ie} = \frac{V_T}{I_{b|Q}}$$

For instance

$$I_{b|Q} = 20 \mu A \Rightarrow h_{ie} = 1.25 K$$

$$I_{b|Q} = 0.1 mA \Rightarrow h_{ie} = 250 \Omega$$

AMPLIFIERS (BJT BASED)


Analog Systems

15/12/2012

13

Transistor

Single stage inverter amplifier

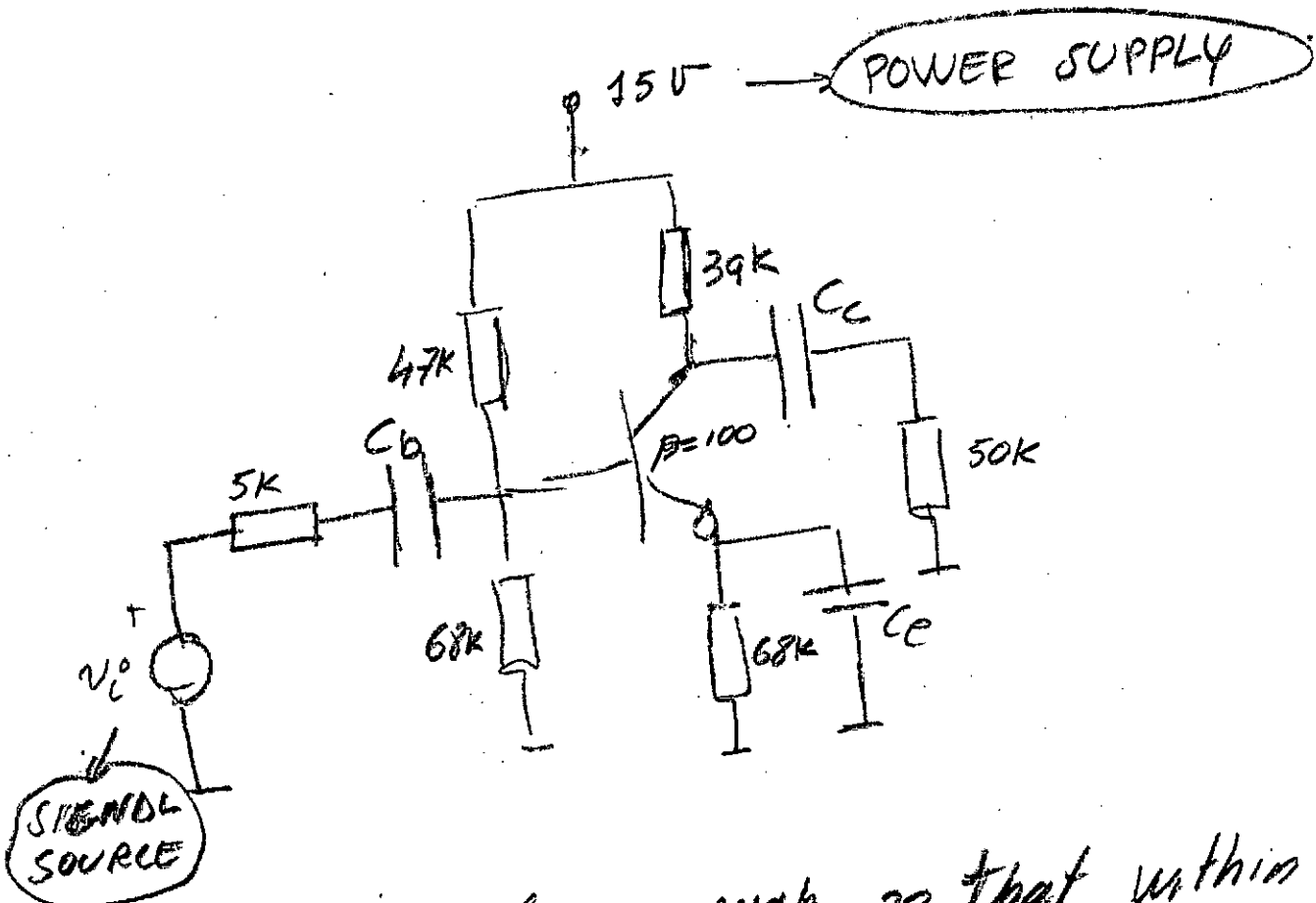

- C_b, C_e, C_c are large enough, so that within the frequency range of interest



$$5k + [C_b] \approx 5k$$

$$68k \parallel [C_e] \approx 0$$

$$50k + [C_c] \approx 50k$$

That is, the capacitor impedance $Z_c = \frac{j}{\omega C}$ is very small within the frequency range of interest

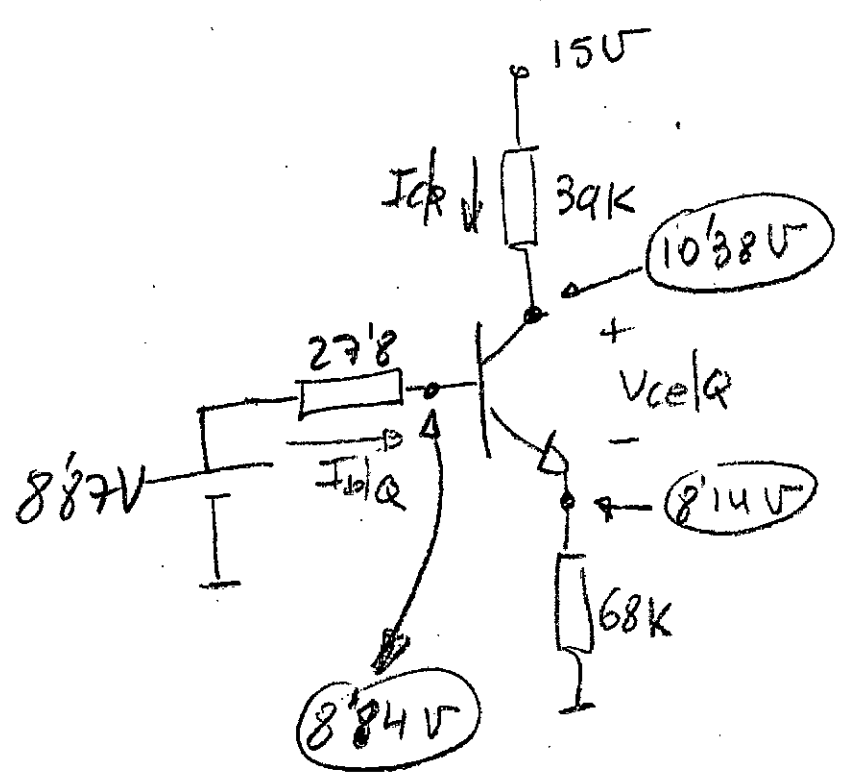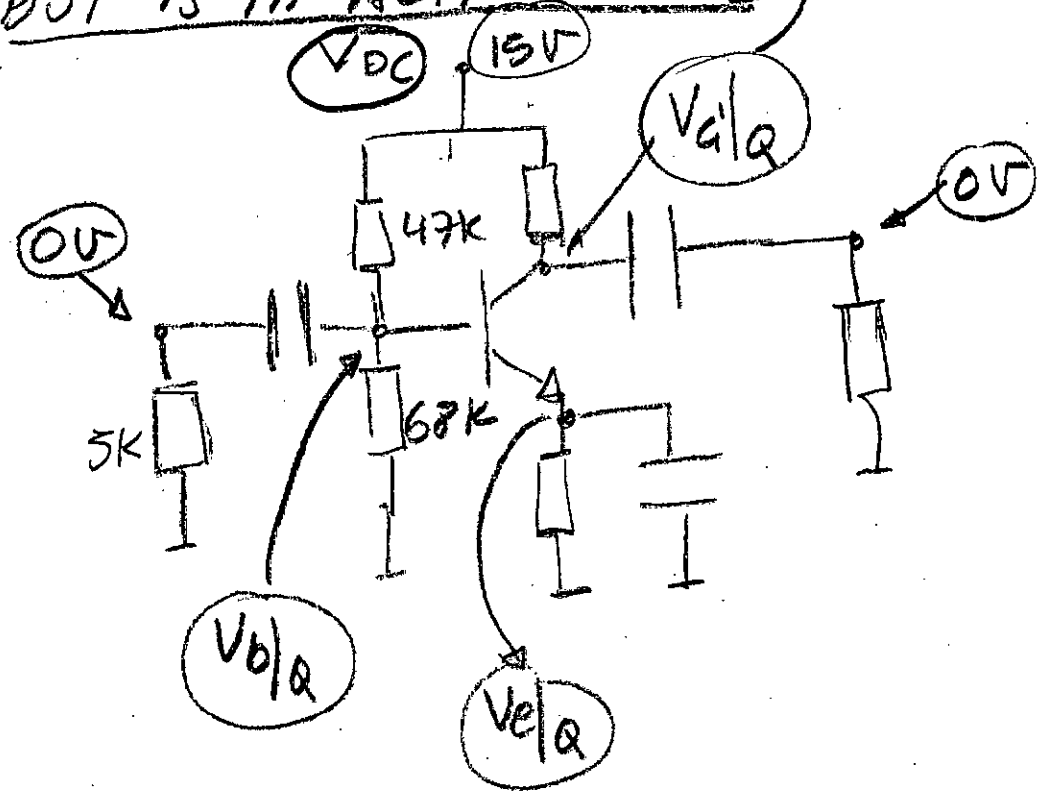• DC analysis - Q point: $V_C = 0$
 (BJT IS IN ACTIVE ZONE)



Base Thevenin equiv.

$$R_b = 47K // 68K = 27.8K$$

$$V_{th} = \frac{15}{68+47} \cdot 68 = 8.87V$$

• BASE LOOP

$$\textcircled{1} \quad 8'87 - I_{b|Q} \cdot 27'8 - 0'7 - 101 \cdot 68 \cdot I_{b|Q} = 0$$

• COLLECTOR LOOP

$$\textcircled{2} \quad 15 - 100 I_{b|Q} \cdot 39 - V_{ce|Q} - 101 \cdot I_{b|Q} \cdot 68 = 0$$

From $\textcircled{1}$ $I_{b|Q} = 1'185 \mu A \Rightarrow \begin{cases} I_{CQ} = 0'1185 \text{ mA} \\ I_{EQ} = 0'1197 \text{ mA} \end{cases}$

From $\textcircled{2}$ $V_{ce|Q} = 2'24 \text{ Volt}$


Also $V_{e|Q} = 0'1197 \cdot 68 = 8'14 \text{ Volt}$

$$V_{c|Q} = 8'14 + 2'24 = 10'38 \text{ Volt}$$


(It can be seen also: $V_{cQ} = 15 - I_{CQ} \cdot 39 =$
 $= 15 - 0'1185 \cdot 39 = 10'38 \text{ Volt}$)

Small signal analysis


• V_{DC} (power supply) $\equiv 0$

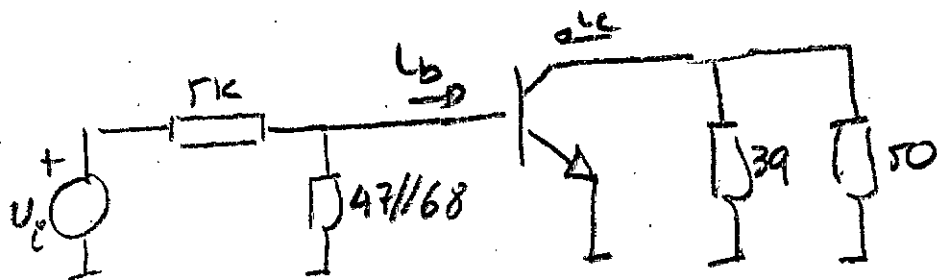

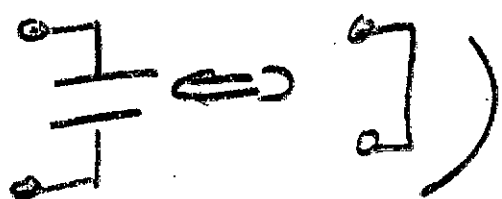(It has been assumed that $\omega \uparrow \uparrow$ and



Substituting the BJT:

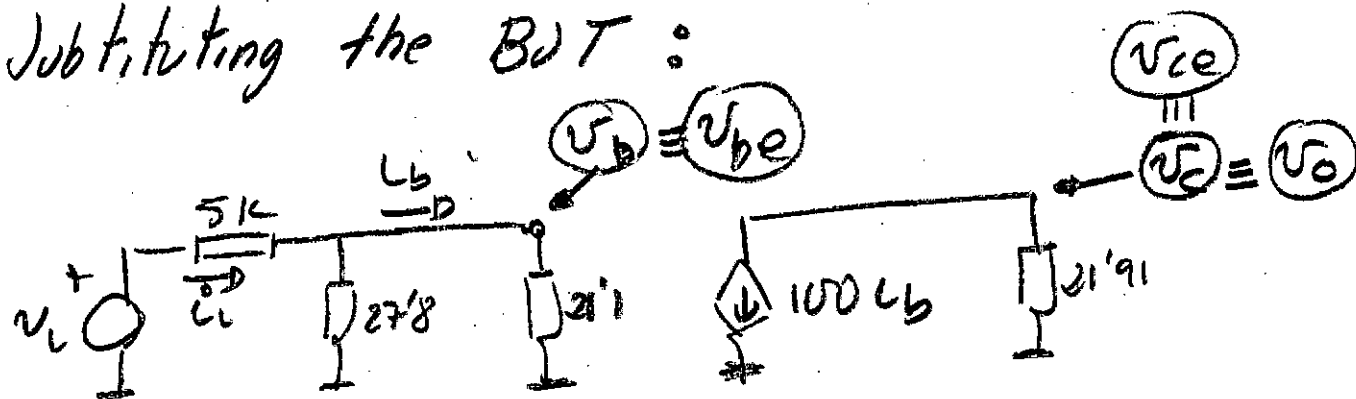

$$h_{ie} = \frac{V_T}{I_{B|Q}} = \frac{0.025}{0.001185} = 21.1K$$

The analysis can be performed:

$$v_b = \underbrace{\frac{v_i}{5 + (27.8 // 21.1)}}_{i_b} \cdot \underbrace{\frac{27.8}{27.8 + 21.1}}_{\text{CURRENT DIVIDER}} = v_i \cdot 0.03345$$

$$v_o = -100 v_b \cdot 21'91 =$$


$$= -100 \cdot v_i \cdot 0'03345 \cdot 21'91 \Rightarrow$$

$$v_o = -73'29 v_i$$

That is, $V_o = V_o|_q + v_o \iff$

$$V_o = 10'38 - 73'29 v_i$$

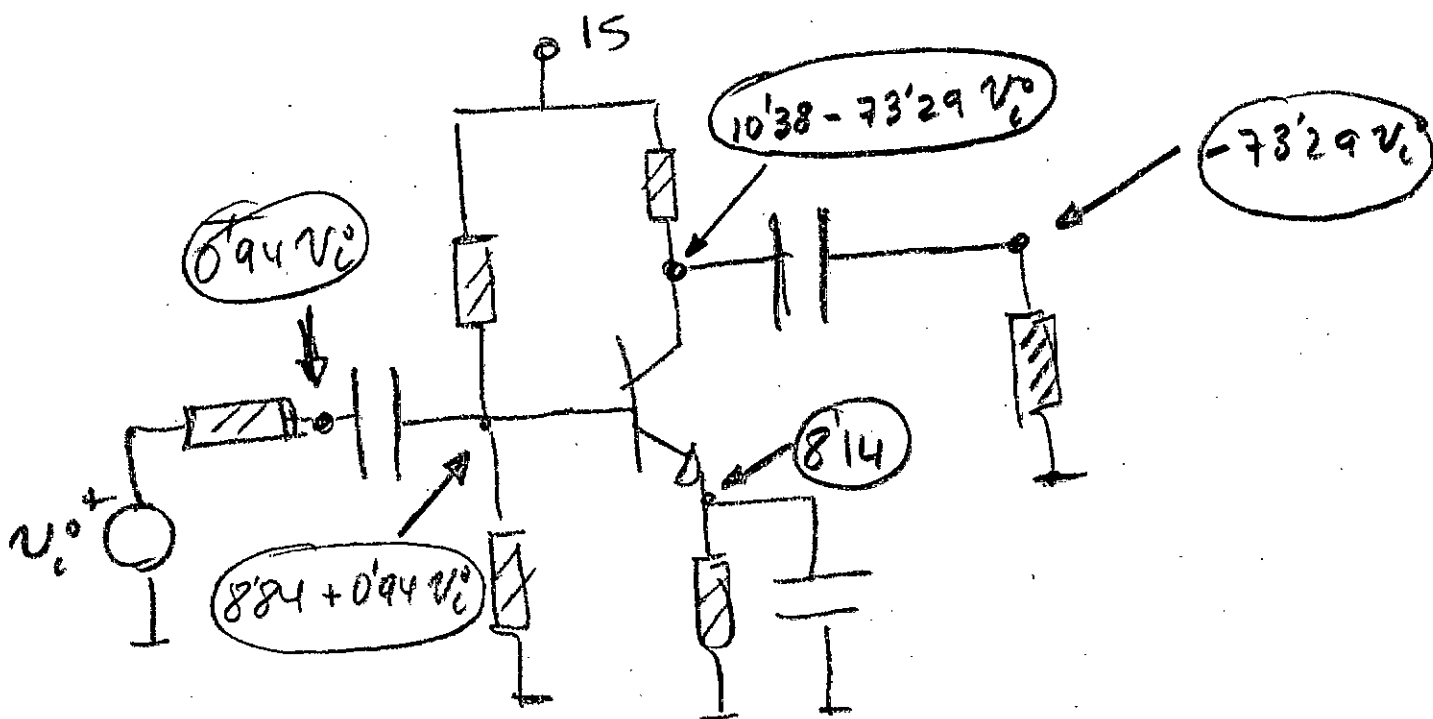V_o is an amplified (73'29), inverted (-) version of v_i



$$(v_b = v_b \cdot 22'1 = 0'94 v_i)$$

Dynamic range of v_i

Some considerations are needed


① This is an AC coupled amplifier.


V_o (either in the collector or in the load resistor) are 'non sensitive' to DC- v_i voltage.

That is, V_o is the same for $v_i(t)$ or for $(v_i(t) + V)$.

The base capacitor blocks DC

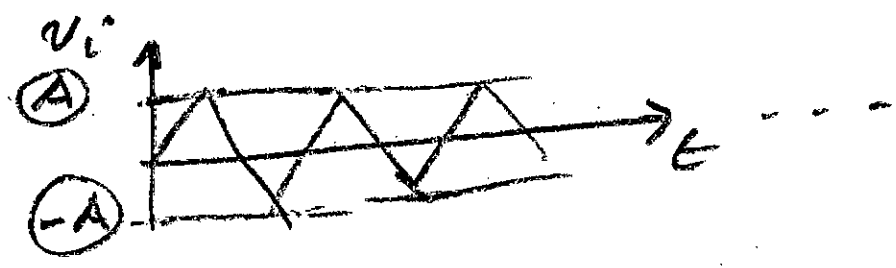② If the $v_i(t)$ signal source is symmetric (equal maximum and minimum values):



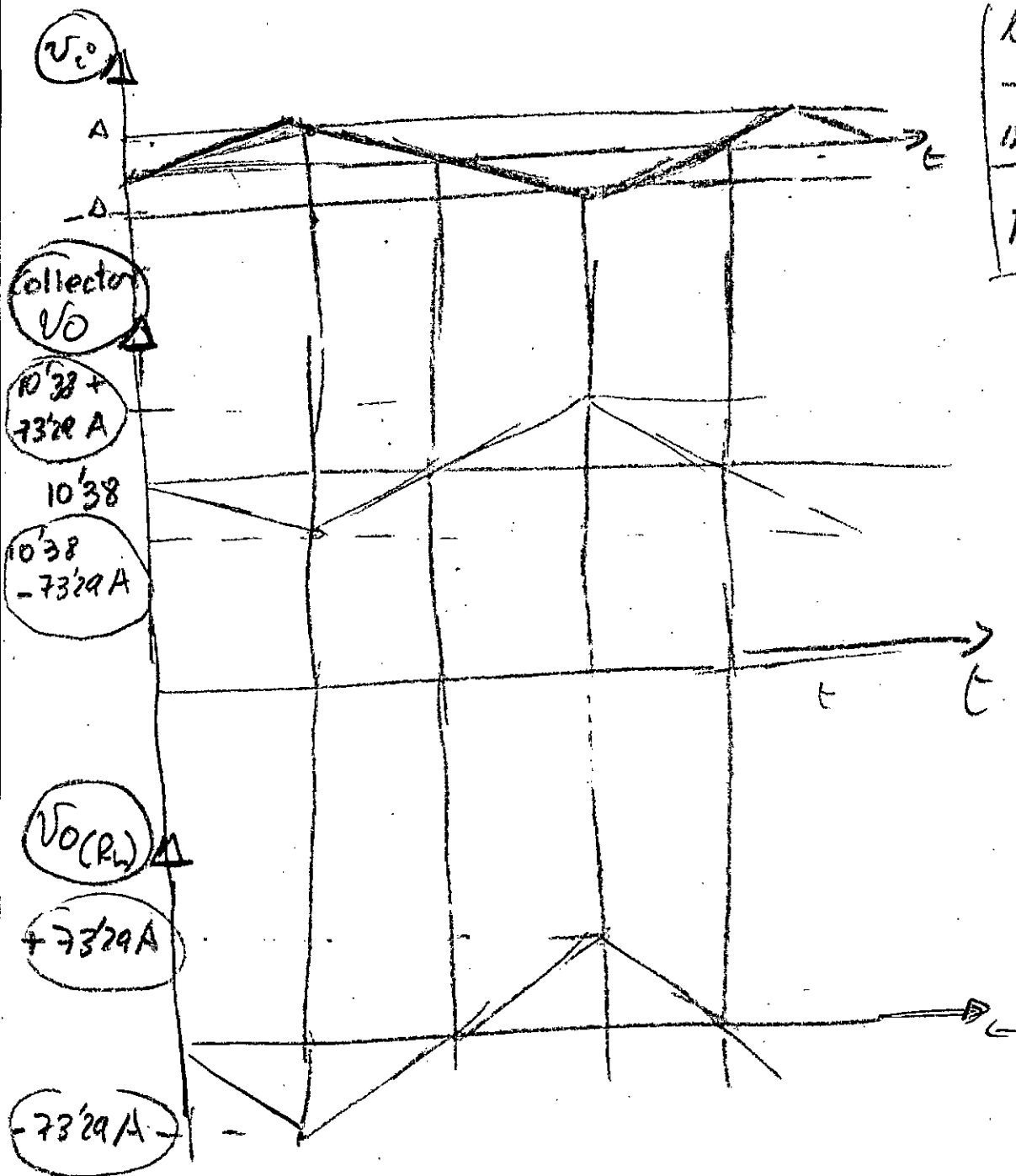

$$V_o(\text{collector})|_{\max} = 10'38 + 73'29 A = 15$$

MAXIMUM V_o value

$$V_o(\text{collector})|_{\min} = 10'38 - 73'29 A =$$

$8'14 + 0'2$

V_{ce}/sat

MINIMUM V_o value

$$A = \frac{15 - 10'38}{73'29} = 63'03 \text{ mV}$$

OR

$$\Delta = \frac{10'38 - 8'16}{73'29} = 30'29 \text{ mV}$$

The $\Delta = 30'29 \text{ mV}$ is the dynamic range of v_i .

"Non distortion" is obtained.