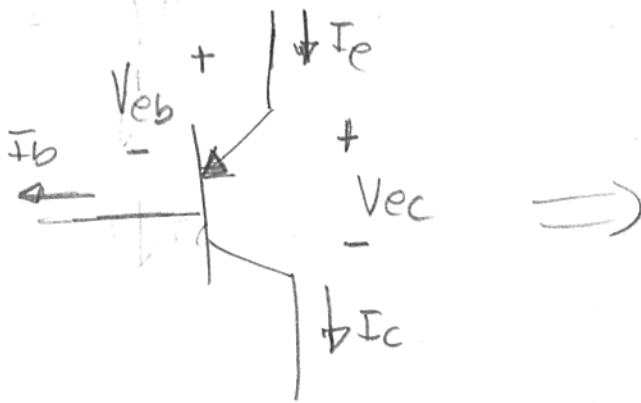


PNP BJT• ACTIVE ZONE

$$\left. \begin{array}{l} V_{eb} = 0.7 \\ V_{ec} > 0.2 \end{array} \right\} \begin{array}{l} I_c = \beta I_b \\ I_e = (\beta + 1) I_b \end{array}$$

• SATURATION ZONE


$$\left. \begin{array}{l} V_{ec} = 0.2 \text{ Volt} \\ V_{eb} = 0.8 \text{ Volt} \end{array} \right\} \begin{array}{l} I_c < \beta I_b \\ I_e = I_c + I_b \end{array}$$

• OFF ZONE

$$V_{eb} < 0.5 \quad I_b = 0 \quad I_c = 0 \quad I_e = 0$$

$V_{ec} > 0$, but if $V_{ec}|_{\max}$ is obtained from datasheet.


BJT

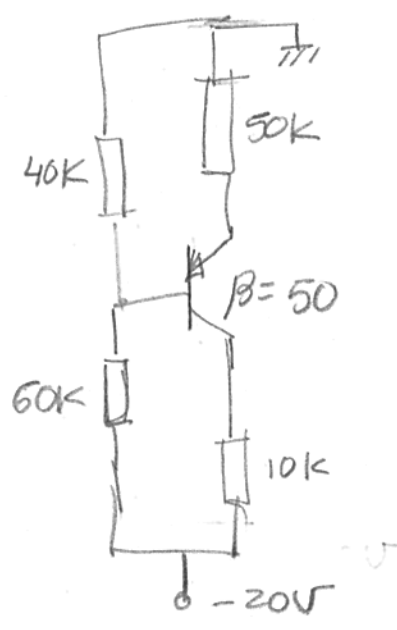

FIND OUT

Q VOLTAGES AND CURRENTS

SOLUTION

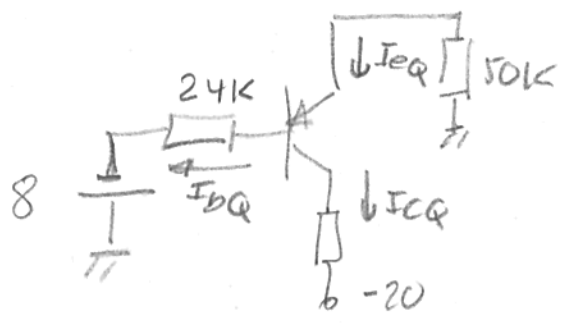

$\beta + 1$

BASE LOOP $-8 + 24 I_{bQ} + 0.7 + 51 I_{bQ} \cdot 50 = 0$ (1)

COLLECTOR LOOP $-20 + 10 \cdot 50 \cdot I_{bQ} + V_{ceQ} + 51 I_{bQ} \cdot 50 = 0$ (2)


From (1) $I_{bQ} = 2.84 \mu A \Rightarrow I_{cQ} = 0.142 mA \Rightarrow$

$I_{eQ} = 0.145 mA$

From (2) $V_{ceQ} = 11.34 Volt$


Finally :


Analog Systems
 22/3/2012 | (3)
 BJT

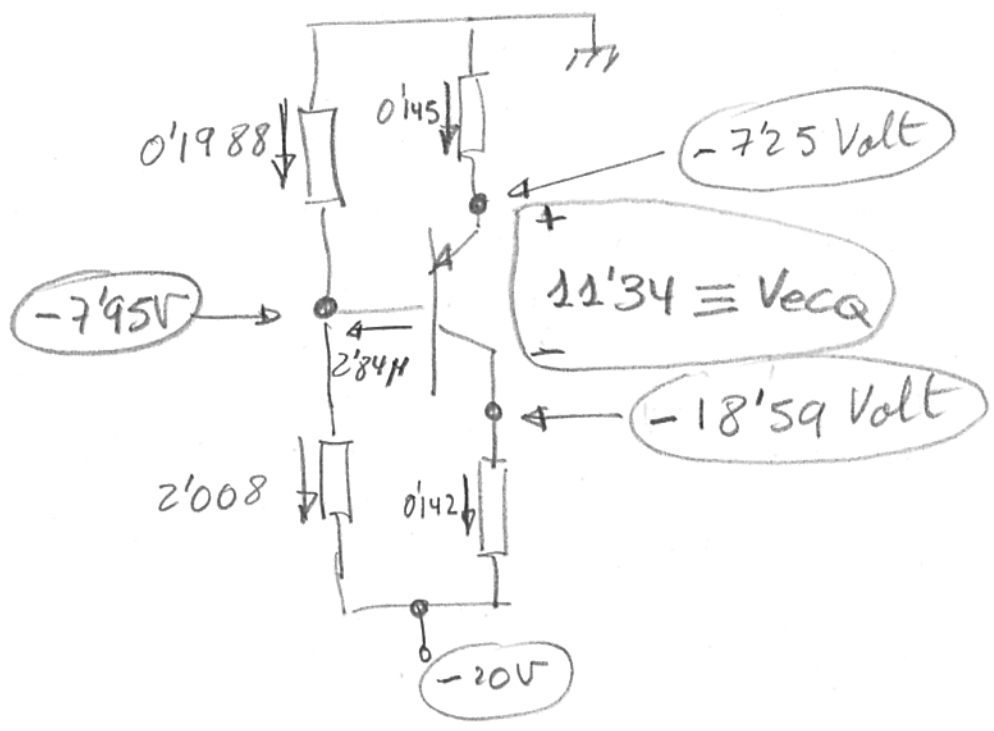


PUSH-PULL CONFIGURATION

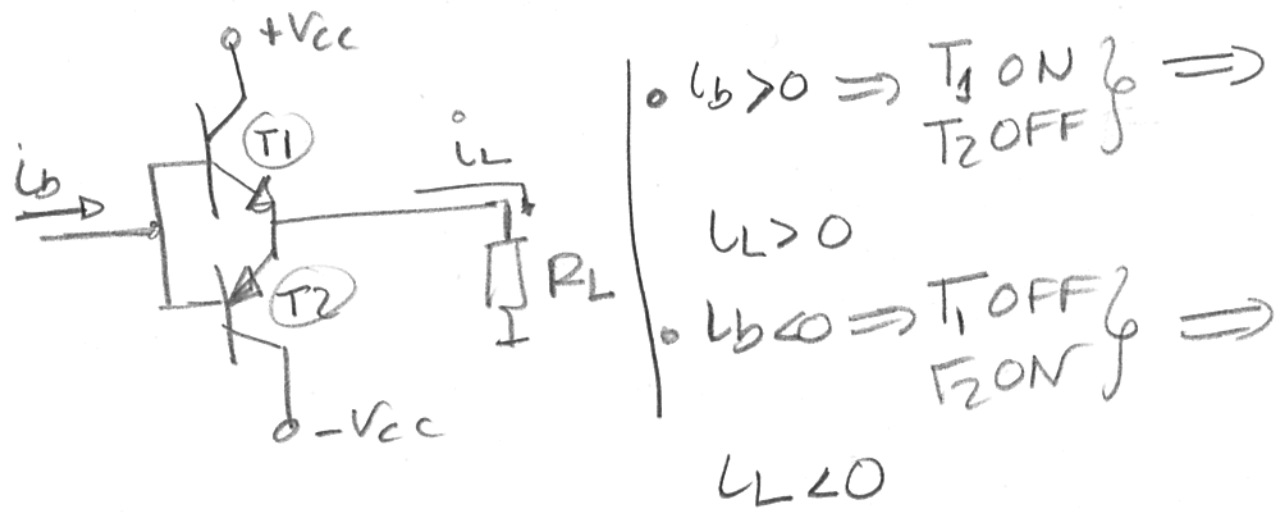When the output current of a device must be increased, the push-pull configuration is suitable.



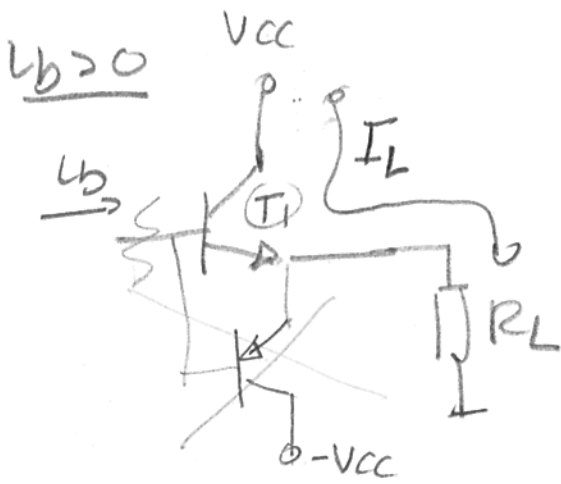

$I_b < 0$

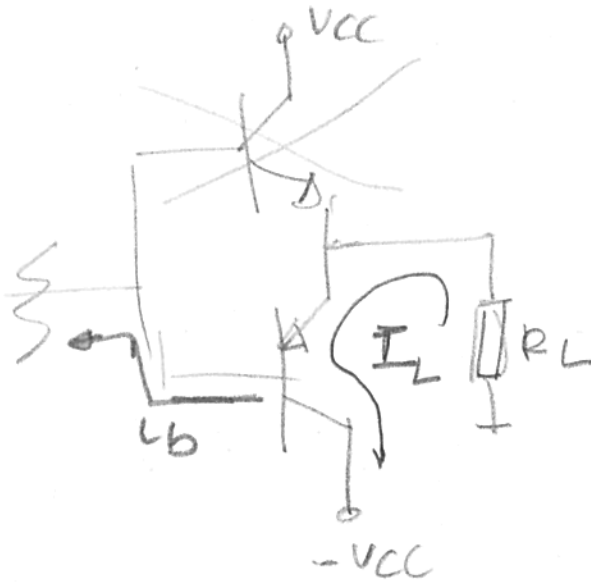

$I_L = \beta I_b$


When the current output of an OA is not large enough:

Analog System

22/3/2012 (5)


BJT

①

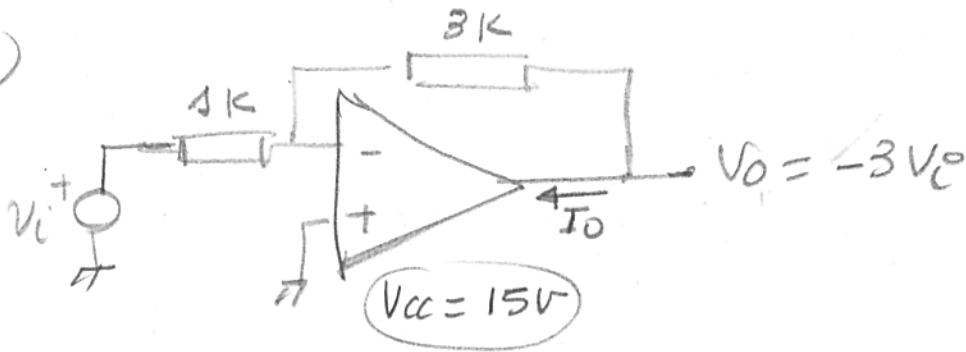

If $V_{i_{\max}} = \pm 4 \text{ Volt} \Rightarrow V_{O_{\max}} = \mp 12 \text{ Volt} \Rightarrow I_O = 4 \text{ mA}$

② If $R_L = 1k \rightarrow$

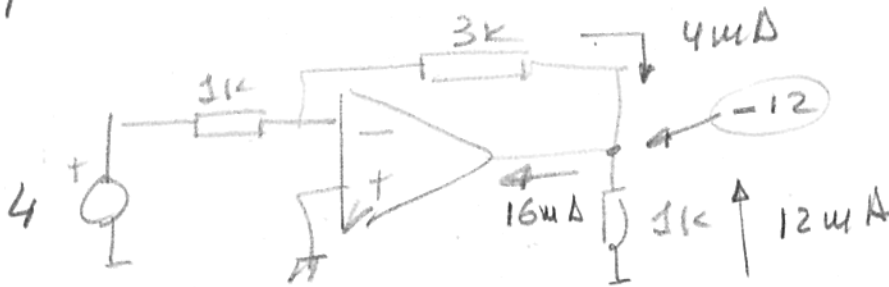

$I_O = 16 \mu A$
The OA can handle it


③ If $R_L = 0 \Omega \Rightarrow I_O = 124 \mu A$. The OA can't handle it! \Rightarrow PUSH-PULL IS NEEDED

• $20A + \text{PUSH-PULL}$

Analog Systems

22/3/2022 | 6

BJT

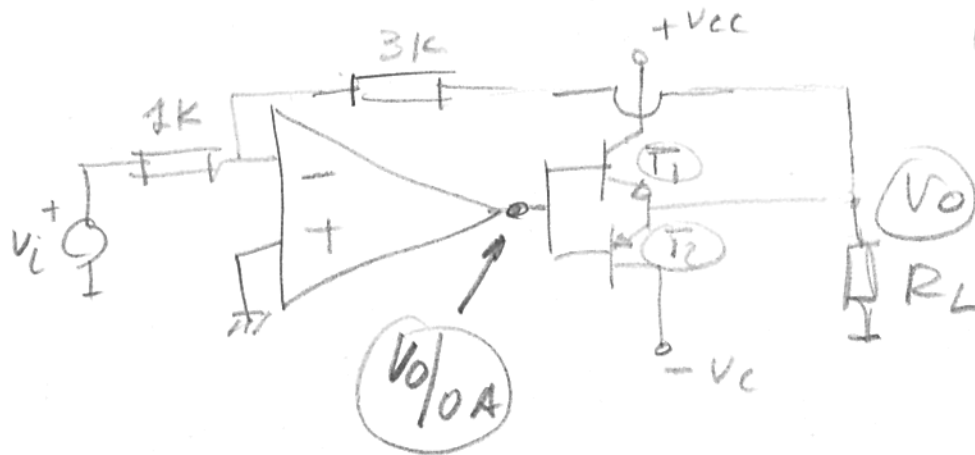

The negative feedback guarantees $v_o = -3v_i$ as in the previous circuit.

The voltage output of the OA is

$$v_{o/OA} = v_o + 0.7 \quad \text{if } v_o > 0$$

$$v_{o/OA} = v_o - 0.7 \quad \text{if } v_o < 0$$


BJT ↔ SWITCH

Analog Systems

22/3/2022 | ②

BJT-SWITCH


BASIC CIRCUIT

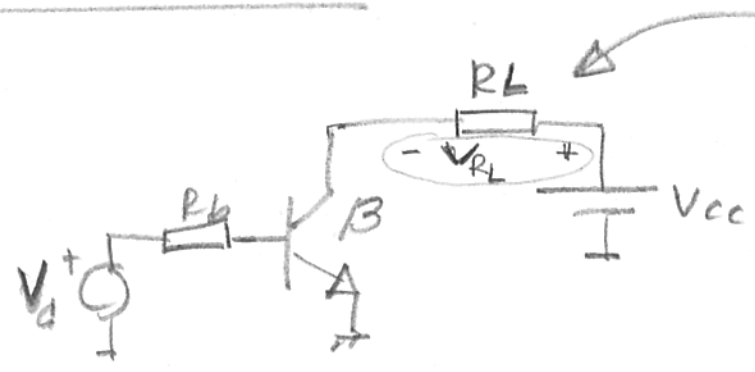

FLOATING RL
NOT GROUNDED

If $V_d = 0 \Rightarrow I_b = 0 \Rightarrow \begin{cases} I_L = 0 \\ V_{ce} = V_{cc} \end{cases}$ (BJT OFF)

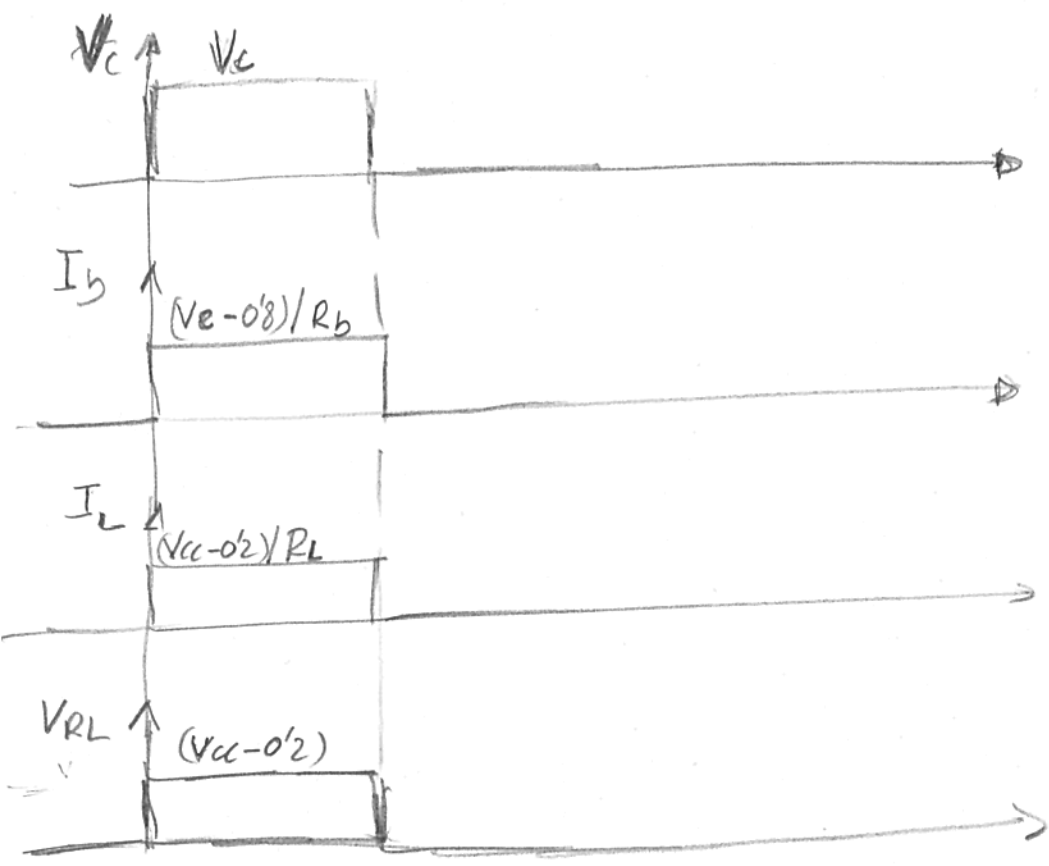If $V_d = \uparrow \uparrow \Rightarrow I_b = \frac{V_c - 0.8}{R_b} \Rightarrow \begin{cases} V_{ce} = 0.2 \\ I_L = \frac{V_{cc} - 0.2}{R_L} \end{cases}$
 (BJT SATURATED)




• EXAMPLE

Analog Systems

22/3/2012 | 8

BJT-SWITCH

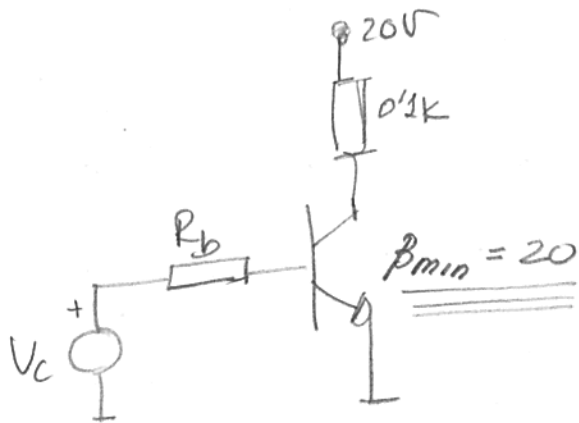

If $V_C(\text{ON}) = 5V$
 $V_C(\text{OFF}) = 0.2V$ } find out R_b , for a proper operation

$V_C = 5 \Rightarrow$ BJT ON (SAT)

$$I_b = \frac{5 - 0.8}{R_b} = \frac{4.2}{R_b}$$


$$I_c = \frac{20 - 0.2}{0.1} = 198 \text{ mA}$$

$$198 < \beta I_b \Rightarrow$$

$$198 = \underset{\beta_{\min}}{20} \cdot I_{b_{\min}} \Rightarrow I_{b_{\min}} = 9.9 \text{ mA} \Rightarrow R_b = 0.424 \text{ K}_{\max}$$

• A greater β will improve the performance of the circuit \Rightarrow


• DARLINGTON ASSEMBLY

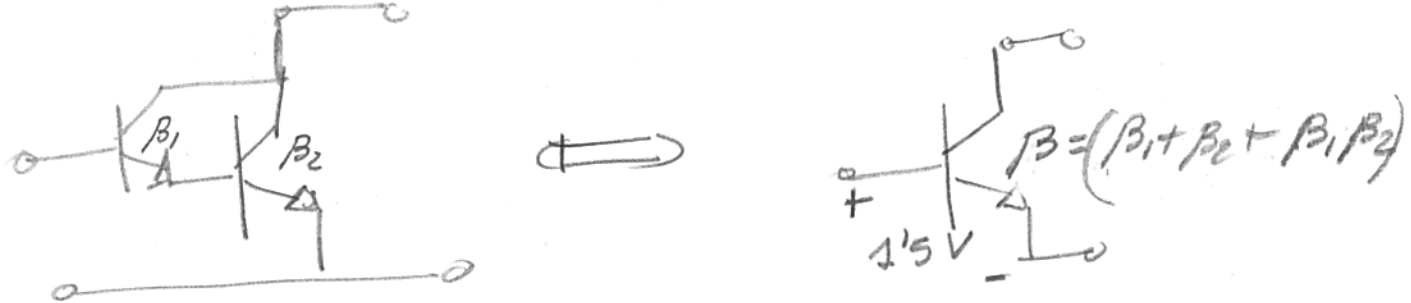

If saturated: $V_{be|_2} = 0.8$ (SAT)

$V_{be|_1} = 0.7$ (CUT) \rightarrow (Notice that $V_{ce_1} > 0.2$)

If a Darlington ($\beta = 500$) is used:

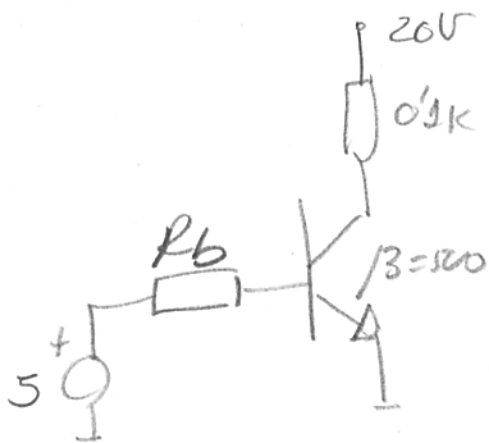

$$I_b = \frac{5 - 1.5}{R_b} = \frac{3.5}{R_b}$$


$$I_c = \frac{20 - 0.2}{0.1} = 198 \mu A$$

$$198 < 500 \cdot I_b \Rightarrow$$


$$I_{b \min} = 0.396 \mu A \Rightarrow R_{b \max} = \frac{5 - 1.5}{0.396} = 8.84 k\Omega$$

(better than previous circuit)

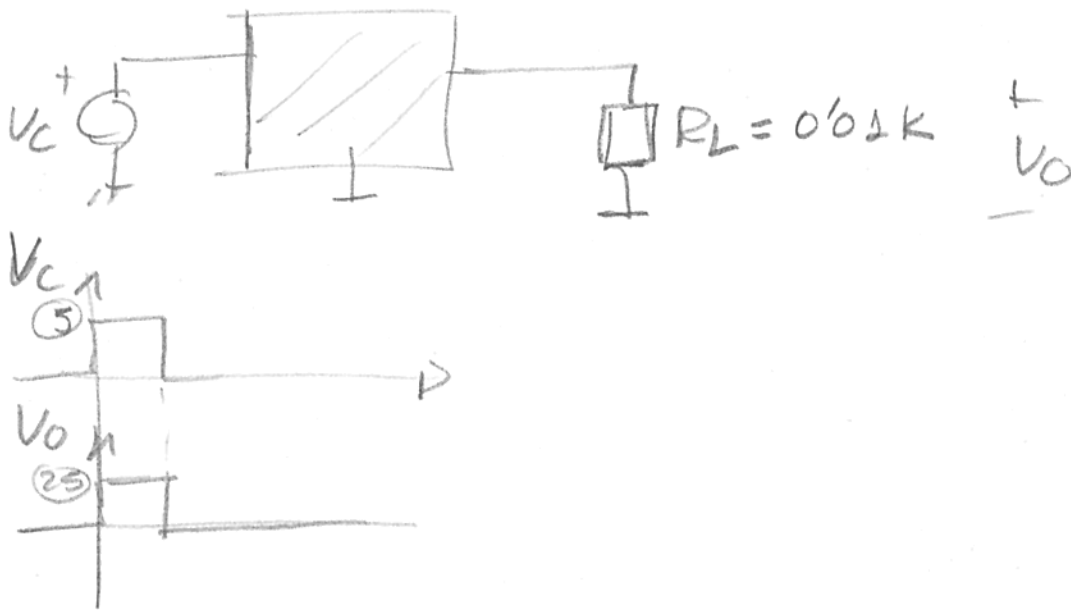- A switch based circuit must be designed :



- Proposed circuit

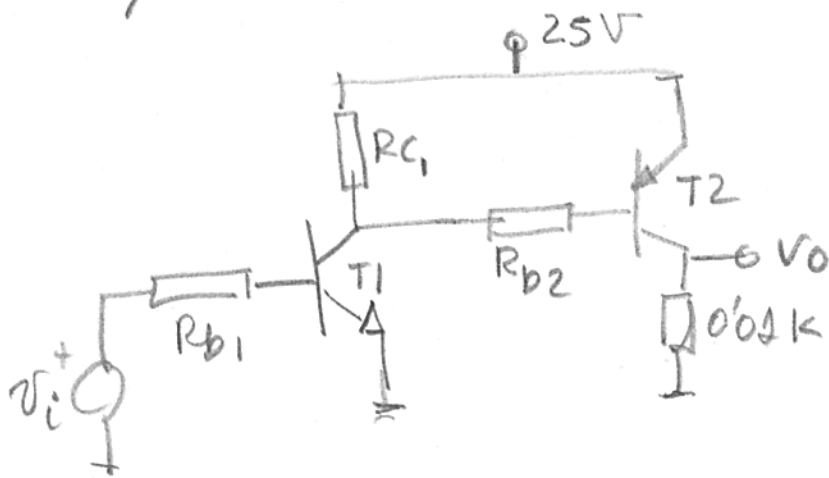

$$\beta_1(\min) = 20$$

$$\beta_2(\min) = 20$$

- $\{R_{b1}, R_{b2}, R_{c1}\}$ have to be found out:

If $V_c \downarrow (V_c < 0.5) \Rightarrow T_1 \text{ OFF} \Rightarrow T_2 \text{ OFF} \Rightarrow V_0 = 0$

If $V_c = 5V \Rightarrow T_1 \text{ ON (SAT)} \Rightarrow T_2 \text{ ON (SAT)} \Rightarrow$
 $V_0 = 25 - 0.2 = 24.8 \text{ Volt}$

• $V_c = 5V$ (ANALYSIS)

$$I_{e2} = \frac{25 - 0'2}{0'01} = 2480 \text{ mA}$$

$$I_{b2} = \frac{25 - 0'8 - 0'2}{R_{b2}} = \frac{24}{R_{b2}}$$

• $\beta_{min} I_{b2} > 2480$ (IZ ON (SDT)) \Rightarrow

20. $\frac{24}{R_{b2}} > 2480 \Rightarrow R_{b2} < 0'193 \text{ k}$ \Rightarrow $\boxed{R_{b2} = 0'18}$

$\boxed{I_{b2} = 133 \text{ mA}}$

• $I_{b1} = \frac{5 - 0'8}{R_{b1}} = \frac{4'2}{R_{b1}}$


• $I_{c1} = \frac{25 - 0'2}{R_{c1}} + 133 = \frac{24'8}{R_{c1}} + 133$

• $\beta_{min} I_{b1} > I_{c1} \Leftrightarrow \frac{20 \cdot 4'2}{R_{b1}} > \frac{24'8}{R_{c1}} + 133$

$\Rightarrow \frac{84}{R_{b1}} > 133 + \frac{24'8}{R_{c1}} \Rightarrow \text{e.g. } \circ$

$\boxed{R_{b1} = 0'5 \text{ k}} \rightarrow \boxed{I_{b1} = 8'4 \text{ mA}}$
 $\boxed{R_{c1} \geq 0'708} \Rightarrow \boxed{R_{c1} = 0'8 \text{ k}}$

Finally

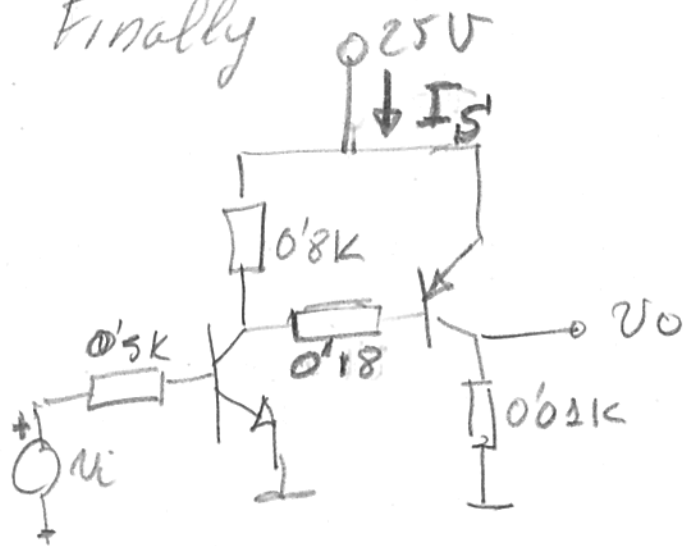

Analogue Systems
22/3/2012 | 12
BJT-SWITCH

- If a Darlington ($\beta_{\min} = 500$) is used (T2)

$$I_{e2} = 2480 \quad ; \quad I_{b2} = \frac{25 - 1.5 - 0.2}{R_{b2}} = \frac{23.3}{R_{b2}}$$

$$500 \cdot \frac{23.3}{R_{b2}} > 2480 \Rightarrow R_{b2} < 4.69k \Rightarrow$$

$$\boxed{R_{b2} = 4.5k} \Rightarrow \boxed{I_{b2} = 5.18 \mu A}$$

$$\begin{aligned}
 & \left. \begin{aligned}
 & I_{b1} = \frac{4.2}{R_{b1}} \\
 & I_{c1} = \frac{24.8}{R_{c1}} + 5.18
 \end{aligned} \right\} \begin{aligned}
 & \beta_{\min} \\
 & \downarrow \\
 & 20 \cdot \frac{4.2}{R_{b1}} > 5.18 + \frac{24.8}{R_{c1}}
 \end{aligned}
 \end{aligned}$$

$$\boxed{R_{b1} = 15K} \Rightarrow R_{c1} > 59K \Rightarrow$$


$$\boxed{R_{c1} = 60K}$$

Analogue System

22/3/2012/13

BJT-SWITCH

Finally

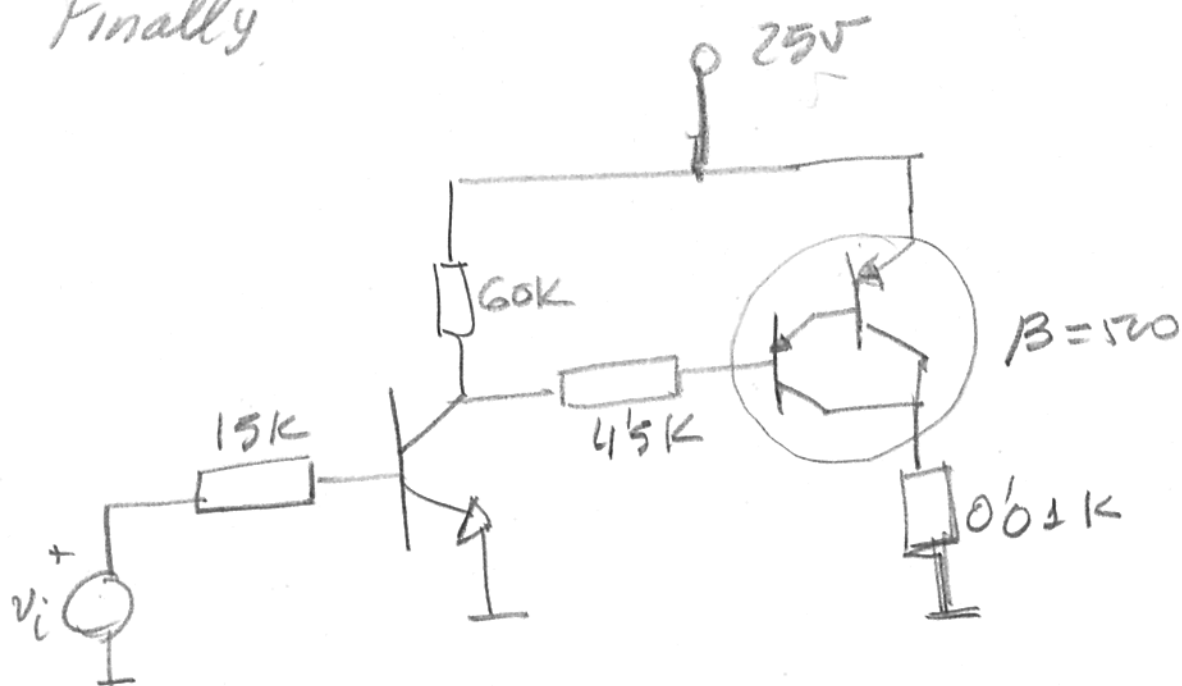

Which is best?

Power losses are the key:

$P = v_i I_i + 25 \cdot I_s$, is the power supplied by the sources

• CIRCUIT ①

• ON STATE ($V_L = 5V$)

$$P = 5 \cdot I_{b1} + 25 (I_{0'8k} + I_{e2}) = 65'37 \text{ W}$$

$$\text{NOTICE: } P_{\text{LOAD}} = 0'01 \cdot (2480)^2 = 61'50 \text{ W}$$

$$I_{0'8k} = \frac{25 - 0'2}{0'8} = 31$$

$$I_{e2} = I_{c2} + I_{b2} = 2480 + 133 = 2'613$$

$$I_{b1} = 8'4$$

$$\text{Power losses} = 65'37 - 61'50 = 3'87 \text{ W}$$

• OFF STATE

$$I_{b1} = 0, I_{e1} = 0, I_{0'8k} = 0 \Rightarrow P = 0$$

CIRCUIT ② (DARLINGTON)

• ON STATE ($V_L = 5V$)

$$P = 5 \cdot I_{b1} + 25(I_{60k} + I_{e2})$$

$$P = 5 \cdot 0'28 + 25(0'413 + 2485'18) = 62'14W$$

$$I_{b1} = \frac{4'2}{15} = 0'28$$

$$I_{60k} = \frac{25 - 0'2}{60} = 0'4133$$

$$I_{e2} = 2480 + I_{b2} = 2480 + 5'18 = 2485'18$$

$$P_{LOSSES} = 62'14 - 61'50 = 0'64W.$$

BEST: DARLINGTON ASSEMBLY!