
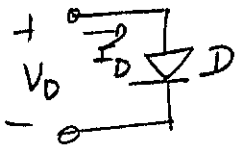


Diode

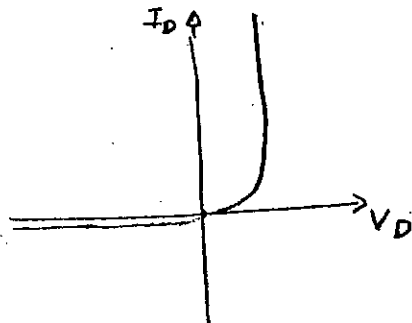



$$I_D = I_0 \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

- I_0 : Reverse saturation current (ORDER OF 10^{-12} to 10^{-15})
- V_T : Thermal Threshold Voltage $\approx 25\text{mV}$ (300°K)



- We can see that: if $I_D \uparrow \Rightarrow V_D \approx \text{constant}$ and
if $V_D \downarrow \Rightarrow I_D \approx 0$

• Diode in a circuit

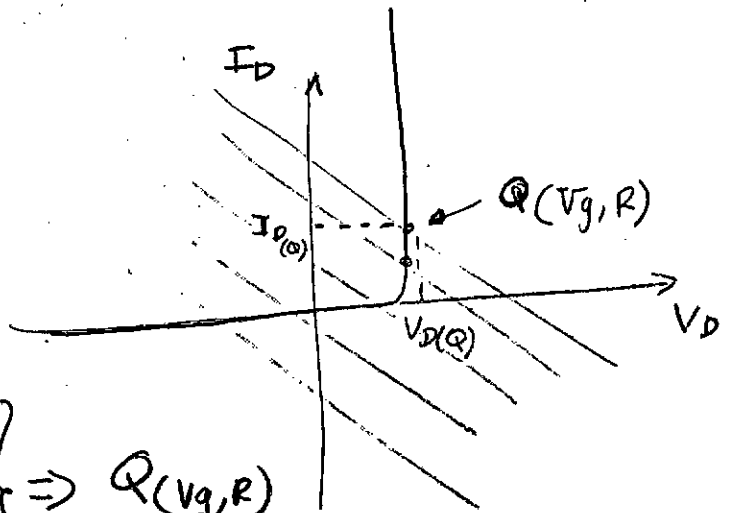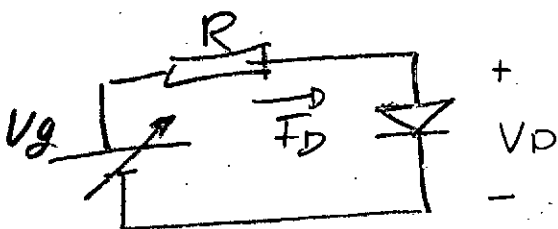

$$\left. \begin{array}{l} \textcircled{1} V_g - I_D R - V_D = 0 \text{ (Load)} \\ \textcircled{2} I_D = I_0 \left(e^{\frac{V_D}{V_T}} - 1 \right) \text{ (Diode)} \end{array} \right\} \Rightarrow Q(V_g, R) \\ \text{|||} \\ (V_{DQ}, I_{DQ})$$

The equation is highly non linear.

It is interesting to model the diode in a piecewise linear model

Typical diode


$$I_D = 6.9144 \cdot 10^{-13} \left(e^{\frac{V_D}{0.025}} - 1 \right)$$

In Matlab:


- ① $V = [-1; 0.003; 2]$
- ② $I = I_0 \left(e^{\frac{V}{0.025}} - 1 \right)$
- ③ Plot(V, I)

Several models can be obtained:

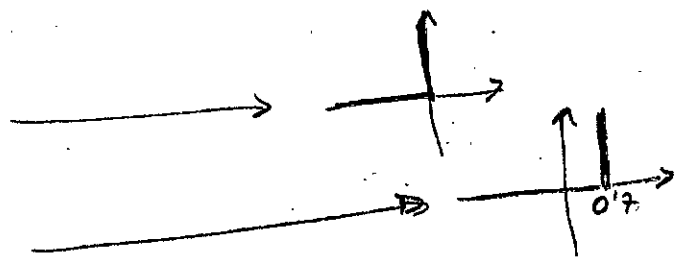
- Ideal diode
- Ideal diode with offset
- Piecewise linear model
- Small signal model




Ideal diode

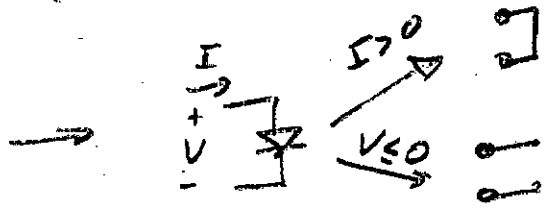

Ideal with offset

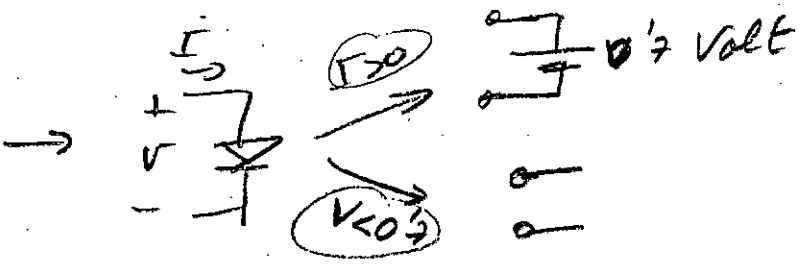

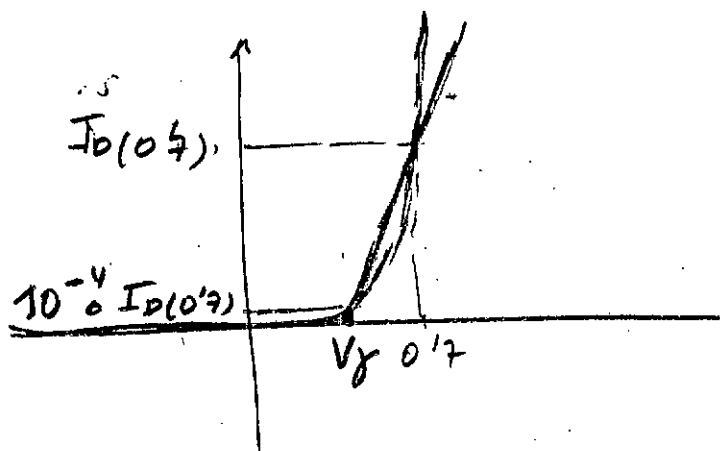Piecewise linear model

It's assumed to model the diode, that:

$$\textcircled{1} I_D(V < V_f) \stackrel{\Delta}{=} 0$$

$$\textcircled{2} I_D(V > V_f) \text{ is Linear, slope} = \frac{I_0(0.7) - I_D(V_f)}{0.7 - V_f}$$



Let's find out V_f and slope

$$I_0 \left(e^{\frac{V_f}{0.025}} - 1 \right) = 10^{-4} \cdot I_0 \cdot \left(e^{\frac{0.7}{0.025}} - 1 \right) \Rightarrow$$


$$\bullet V_f = 0.47 \text{ Volt (Note that } V_f \text{ is independent of } I_0)$$

$$\bullet \text{ slope} = \frac{0.1 - 9.7077 \cdot 10^{-5}}{0.7 - 0.47} = 0.4344 \Omega^{-1}$$


We can graph the model

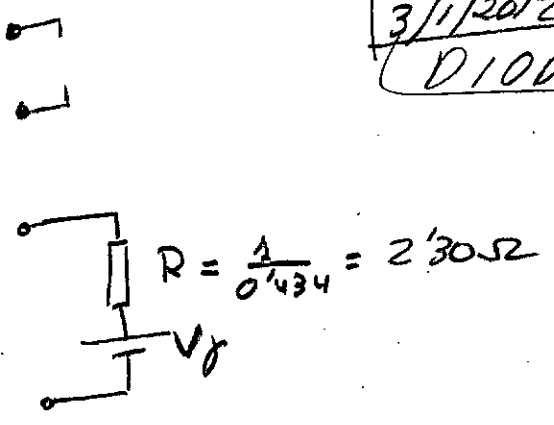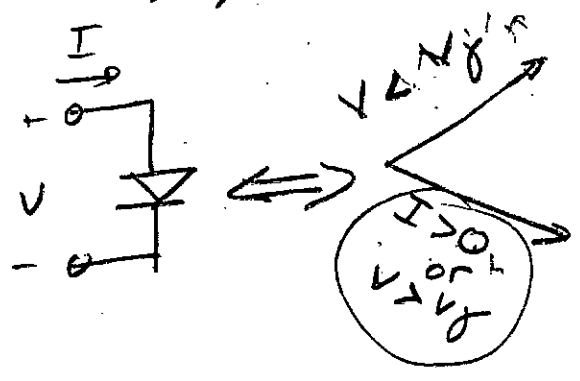

And The (I-V) is

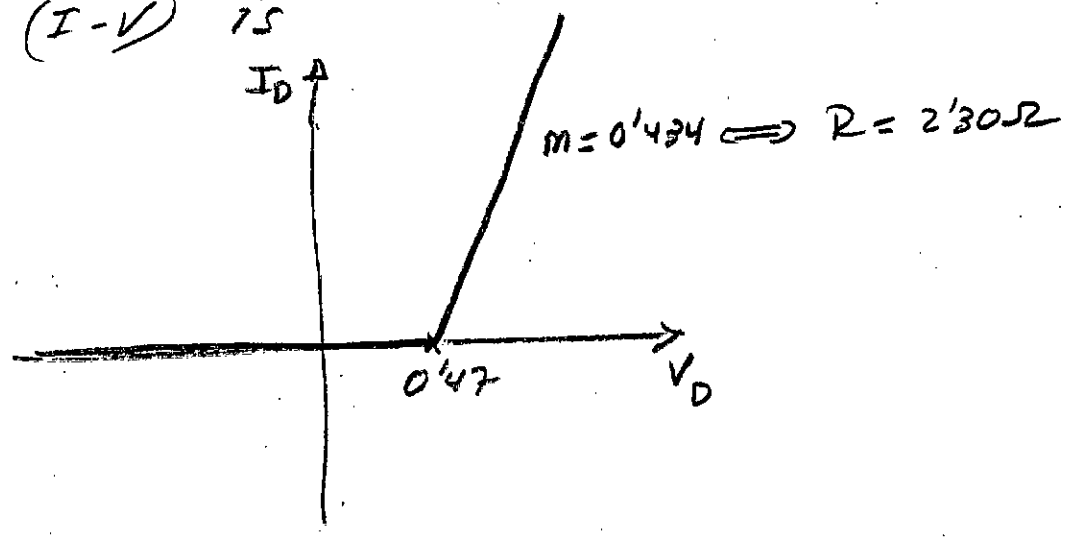

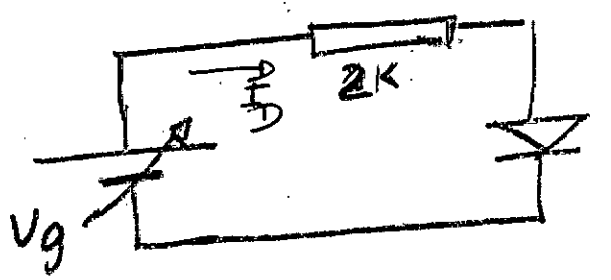The ideal, offset and piecewise models as well as the original equation will be used to solve a simple circuit.



$-1 < V_g < 100$ Volt

① Ideal model


The system is defined by two equations:

① $I_D - V_D$: Diode characteristics



② Load line: $-V_g - I_D \cdot 2 - V_D = 0$

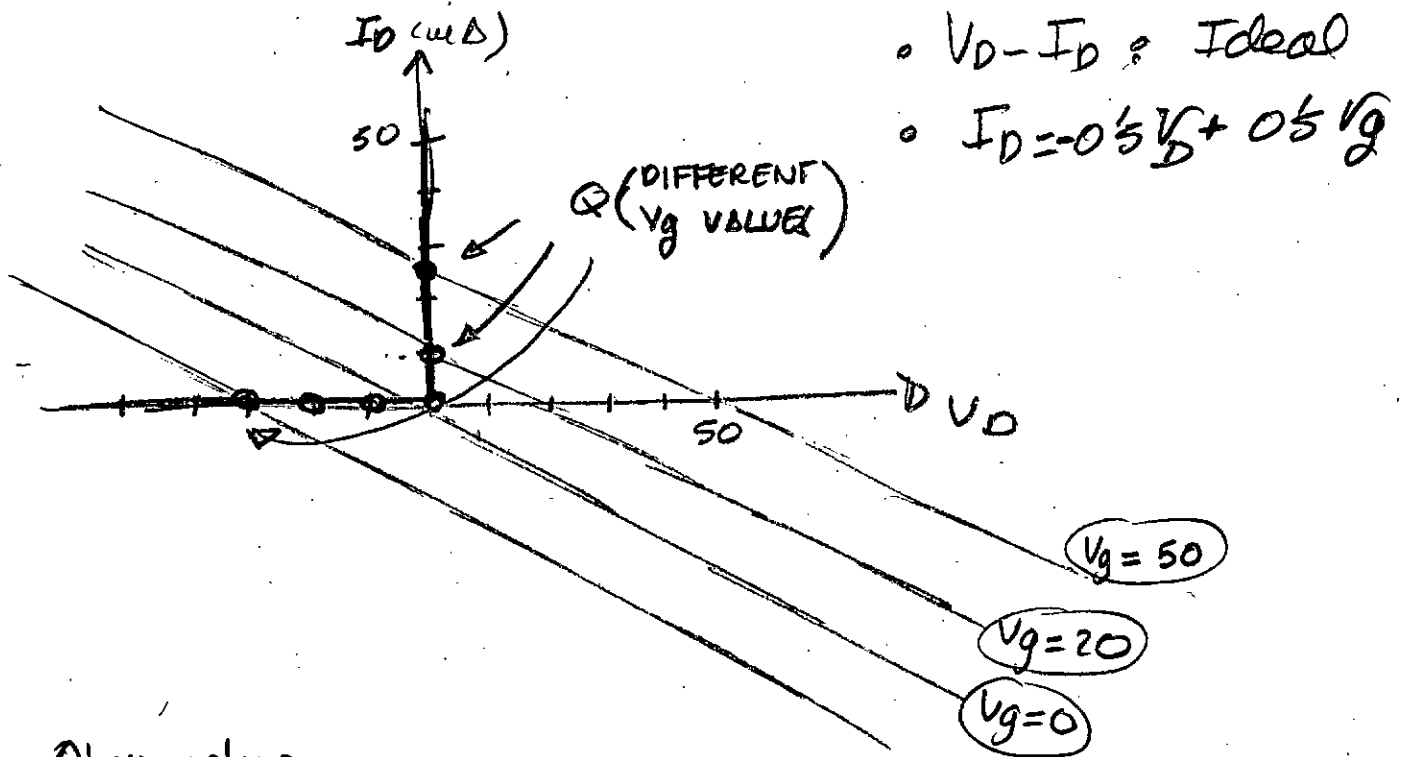If both equations are plotted in the same graph, the bias point Q can be obtained.




- $V_D - I_D$: Ideal
- $I_D = 0.5 V_D + 0.5 V_g$

Obviously:

- $V_D = 0$, $I_D = \frac{V_g}{2} = 0.5 V_g$ IF $V_g > 0$
- $V_D = V_g$, $I_D = 0$ IF $V_g < 0$

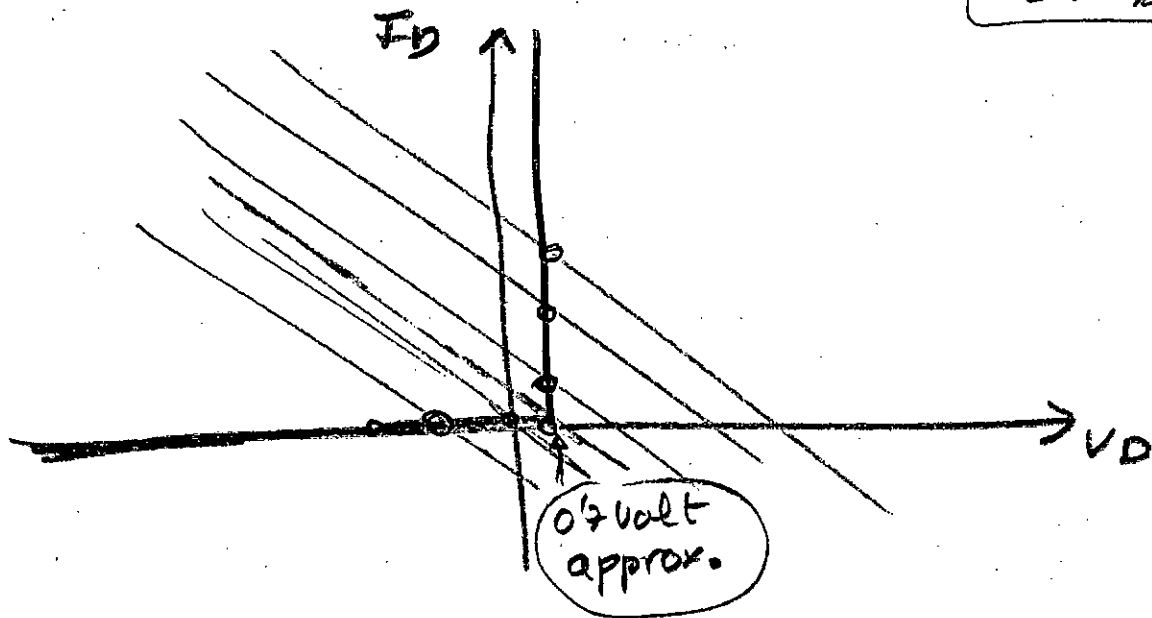- (2) Ideal with offset
The same applies and:



It's obvious that:

$$\text{IF } V_g > 0.7 \Rightarrow \begin{cases} V_D = 0.7 \\ I_D = \frac{V_g - 0.7}{2} \end{cases}$$

$$\text{IF } V_g < 0.7 \Rightarrow \begin{cases} V_D = V_g \\ I_D = 0 \end{cases}$$

- (3) The exact model (at first instance)

$$\textcircled{1} I_D = I_0 \left(e^{\frac{V_D}{V_T}} - 1 \right)$$

$$\textcircled{2} V_g - 2 I_D - V_D = 0$$


MATLAB

SOLVER!!

↓
you can work out
with it.

There's an important question to be worked out:


If $V_g = V_{DC} + v_g$, that is

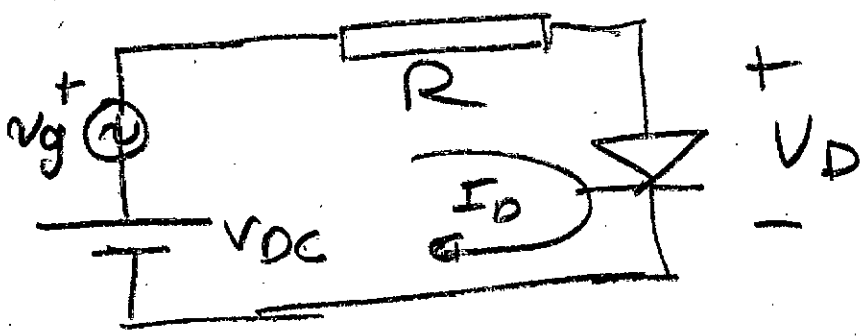

$$I_D = I_{D|Q} + i_d \quad \text{and} \quad \left. \begin{array}{l} I_D = I_{D|Q} + i_d \\ V_D = V_{D|Q} + v_d \end{array} \right\} \begin{array}{l} \bullet Q \text{ subindex means} \\ \text{BIAS POINT} \end{array}$$

$$V_D = V_{D|Q} + v_d$$

① $V_{D|Q}$ $I_{D|Q}$ can be easily obtained using the ideal models (with a small inaccuracy) That is:

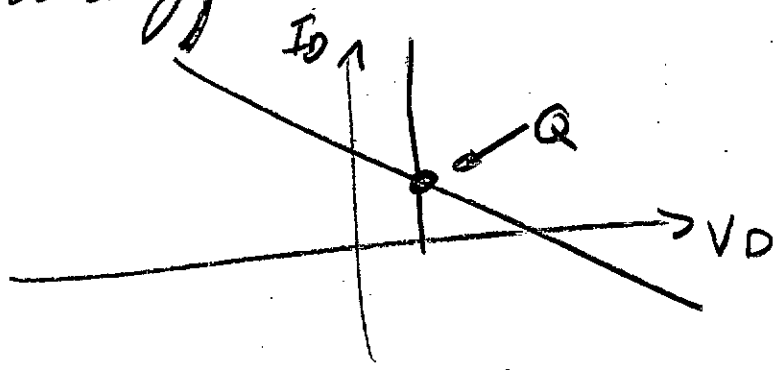

, but how i_d, v_d can be obtained if v_g is known?


SMALL SIGNAL MODEL OF A DIODE


In fact what should be worked out, is how to obtain ΔI_D , when ΔV_D is applied.

Taylor's series solve this question

$$I_D|_Q + \Delta I_D = I_D|_Q + \left. \frac{\partial I_D}{\partial V_D} \right|_Q \underbrace{(V_D - V_D|_Q)}_{\Delta V_D}$$

If $\Delta I_D \equiv i_d$ and $\Delta V_D = v_d$,
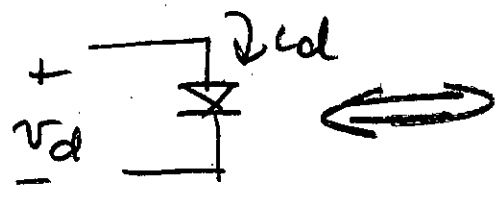
$$i_d = \left. \frac{\partial I_D}{\partial V_D} \right|_Q \cdot v_d \iff$$

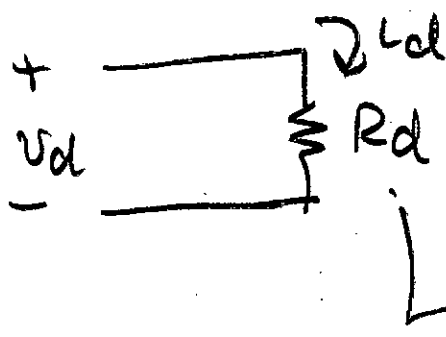


where $R_d = \frac{1}{\left. \frac{\partial I_D}{\partial V_D} \right|_Q}$

DYNAMIC RESISTANCE OF THE DIODE IN Q BIAS POINT

$$\left. \frac{\partial I_D}{\partial V_D} \right|_Q = I_0 e^{\frac{V_D}{V_T}} \cdot \frac{1}{V_T} = (R_d)^{-1}$$

Analog Systems


18/1/2012 / 9

DIODE

and, for instance, for a Si diode:

$$\left. \begin{array}{l} \text{Si DIODE: } V_{DQ} \approx 0.65 \\ I_0 \approx 3 \cdot 10^{-14} \\ V_T = 0.025 \end{array} \right\} \Rightarrow R_d = 4.26 \text{ } \Omega$$

Then

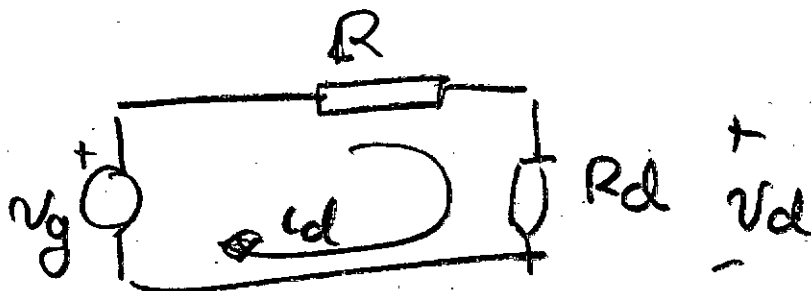



$$I_d = \frac{V_g}{R + R_d}$$

$$V_d = \frac{V_g}{R + R_d} \cdot R_d$$

Try to simulate, and verify the previous formulas

- The Breakdown Voltage:
Zener diode

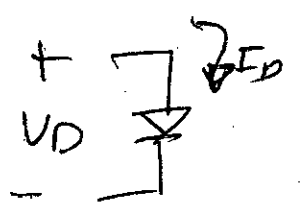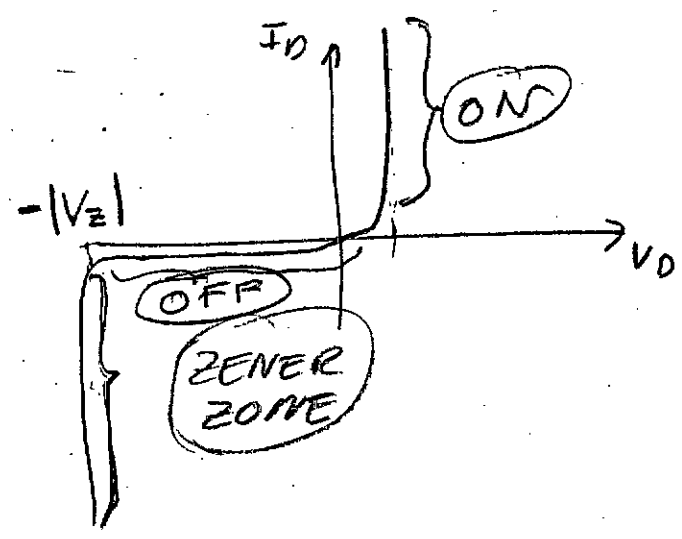When a high inverse voltage is applied, the diode enters the 'Zener zone'



- Then $V_D = 0^+$ \Rightarrow $I_D > 0$ \rightarrow **DO_N**
- $-V_Z < V_D < 0^+$ \Rightarrow $I_D \approx 0$ \rightarrow **DO_{FF}**
- $V_D = -V_Z \Rightarrow I_D < 0$ \rightarrow **D_{ZENER}**

$I_{D\min}$ is required to assure $V_D = -|V_Z|$

The power supplied to the diode is about:

DO_N: $P = |I_D| \cdot 0^+$ $V_{D(on)}$

DO_{FF}: $P \approx 0$

D_{ZENER}: $P = |I_D| \cdot |V_Z|$

obviously

$$P_{ZENER} \gg P_{ON}$$


Zener diodes are designed to withstand the heating caused by P_{ZENER} .

- P_{Zmax} is defined in the specs.

APPLICATION CIRCUITS

① HALF WAVE RECTIFIER

RESISTIVE LOAD

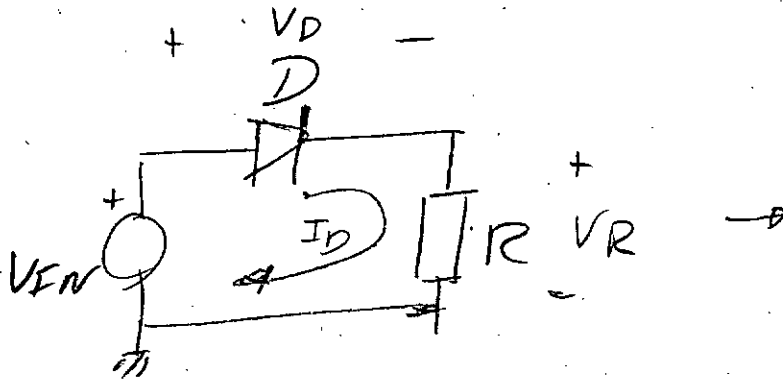

Large signal model
is assumed

• $I_D > 0 \Rightarrow \left\{ \begin{array}{l} V_R = V_{IN} - 0.7 \\ I_R = \frac{V_{IN} - 0.7}{R} \end{array} \right\} \Rightarrow V_{IN} > 0.7$

• $I_D = 0 \Rightarrow \left\{ \begin{array}{l} V_R = 0 \\ V_D = V_{IN} \end{array} \right\} \Rightarrow V_{IN} < 0.7$

When $V_{IN} > 0.7 \Rightarrow V_R = V_{IN}$	} RECTIFYING PROCESS
$V_{IN} < 0.7 \Rightarrow V_R = 0$	



• Simulate when :

① $V_{in}(t) = A \sin(\omega t)$ and $A \gg 0.7$

② $V_{in}(t) = A \sin(\omega t)$ and $A \approx 0.7$

Plot $\{V_{in}, v_D, v_R, v_d\}$ in each case

② FULL WAVE RECTIFIER
RESISTIVE LOAD

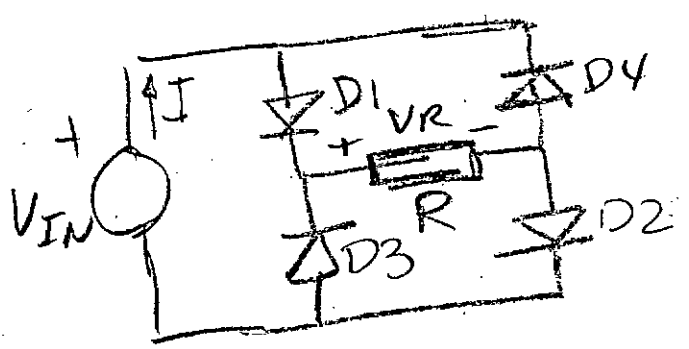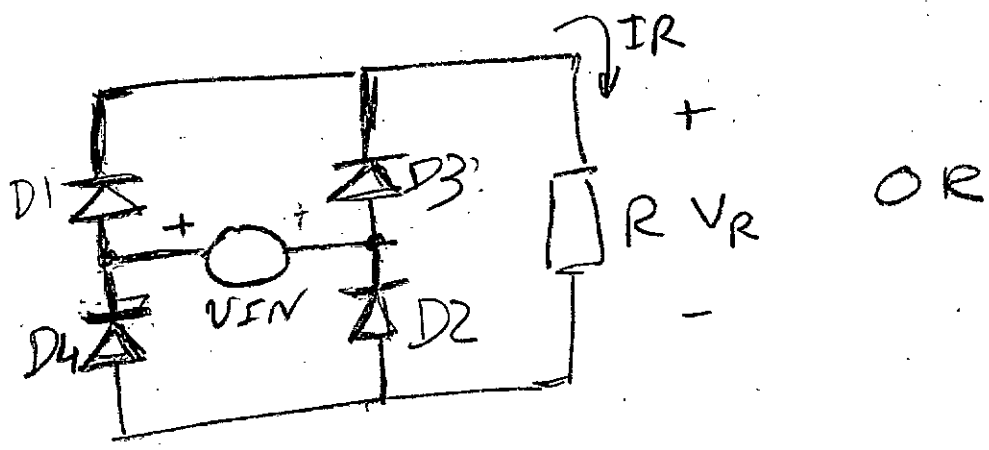

• If $I > 0 \Rightarrow$ D_1 ON D_2 OFF \Rightarrow $\begin{cases} V_R = V_{IN} = 2.0V \\ I_R = \frac{V_R}{R} \end{cases}$

DIGITAL SYSTEMS
26/11/2017 (13) 0
DIODE

\Rightarrow $V_{IN} > 2.4$ Volt

It can be seen that

$$\left. \begin{aligned} V_{D3} &= -(V_{IN} - 0.7) < 0.7 \\ V_{D4} &= -(V_{IR} - 0.7) < 0.7 \end{aligned} \right\} \Rightarrow \begin{aligned} D_3 &\text{ OFF} \\ D_4 &\text{ OFF} \end{aligned}$$

• If $I < 0$ $\left. \begin{aligned} D_3 \text{ ON} \\ D_4 \text{ ON} \end{aligned} \right\} \left. \begin{aligned} D_1 \text{ OFF} \\ D_2 \text{ OFF} \end{aligned} \right\} V_R = -V_{IN} - 2.0V$
 $I_R = \frac{V_R}{R}$


and $V_{IN} < -1.4$ Volt

• If $-1.4 < V_{IN} < 1.4$ $\Rightarrow I_R = 0 \Rightarrow V_R = 0$
 $I = 0$

$\{ D_1, D_2, D_3, D_4 \}$ OFF

• Notice that R is floating (V_{IN} and R don't have common-ground connection)

③ Zener Voltage Regulator

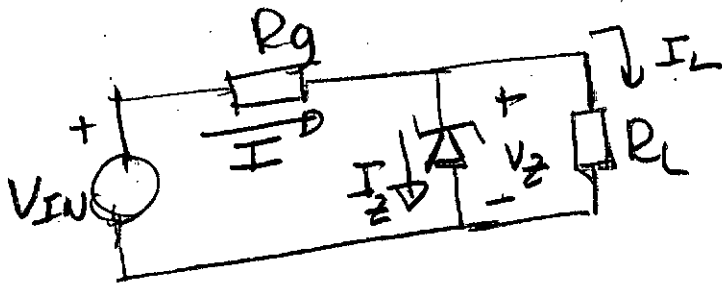

If the diode is operating in its zener zone

that is $\left. \begin{array}{l} I_Z > I_{Zmin} \\ P_Z < P_{Zmax} \end{array} \right\} , \boxed{V_{R_L} = V_Z}$

in spite of V_{IN} may change.

• $I = \frac{V_{IN} - V_Z}{R_g} = I_Z + \frac{V_Z}{R_L} \Rightarrow$

① $\boxed{V_Z = \frac{V_{IN}}{R_g} - V_Z \left(\frac{1}{R_g} + \frac{1}{R_L} \right)}$ and

② $\boxed{P_Z = V_Z \cdot I_Z}$ Also

③ $I_Z > I_{Zmin}$ and ④ $P_Z < P_{Zmax}$
 must be met

Usually, the specs of the regulator are:

Diodes Systems

26/1/2012/14

DIODE

(1) $V_{F_{min}} < V_F < V_{F_{max}}$

and

(2) $I_{L_{min}} < I_L < I_{L_{max}}$

(3) V_L

R_g and the diode have to be chosen

Example . Solve the following regulator:

$15 < V_F < 25$


$0 < I_L < 200 \text{ mA}$

$V_L = 18 \text{ Volt}$

$R_g?$

ZENER?


Voltage Limiter

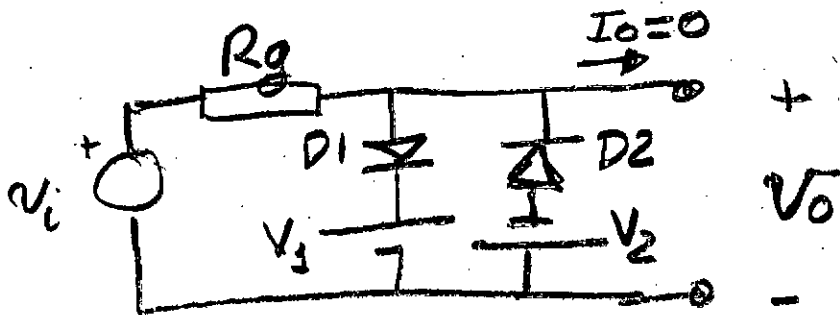


$$v_i > V_1 + 0.7 \Rightarrow v_o = V_1 + 0.7 \quad (D1 \text{ ON} \parallel D2 \text{ OFF})$$

$$v_i < -(V_2 + 0.7) \Rightarrow v_o = -(V_2 + 0.7) \quad (D1 \text{ OFF} \parallel D2 \text{ ON})$$
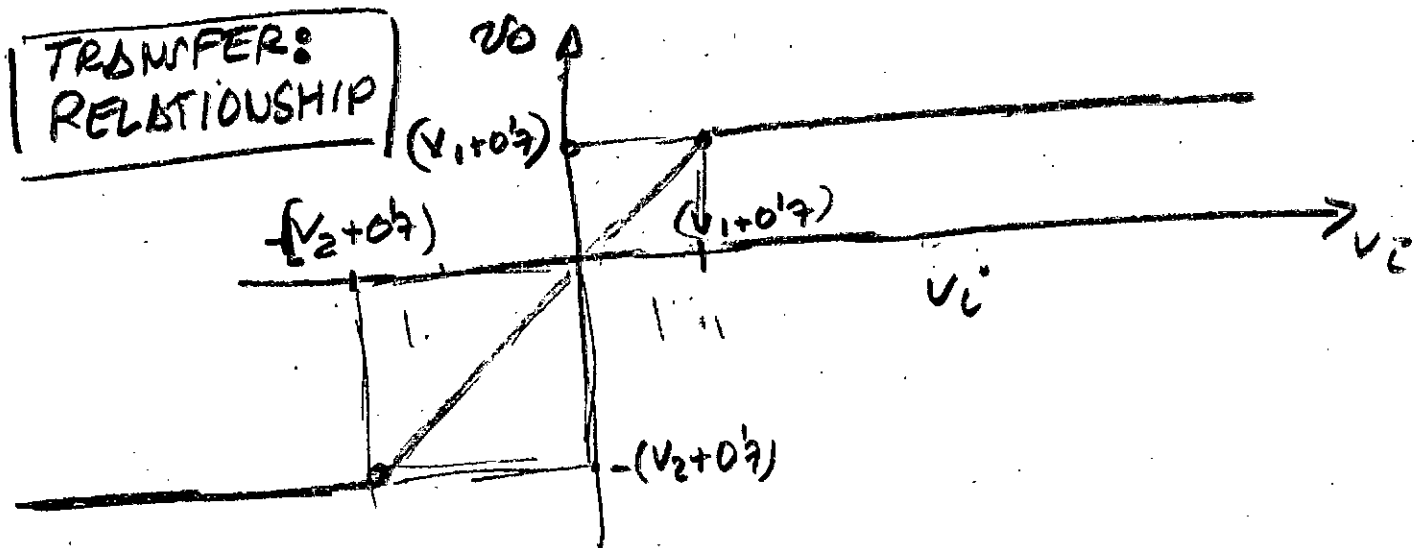
$$-(V_2 + 0.7) < v_i < (V_1 + 0.7) \Rightarrow v_o = v_i$$




• Notice that $I_o = 0$ has been assumed

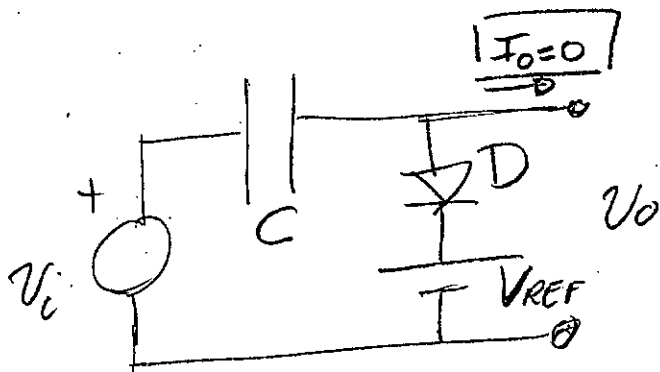Peak limiter

This circuit adds a DC voltage to v_i so that the peak voltage of v_o is V_{REF} .

You can see the pspice models
 peak_limiter.sch and
 peak_limiter_eulerod.sch

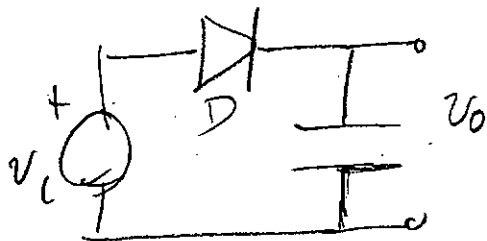Peak follower


pspice model

$v_{o(peak)}$ equals the maximum of $v_{i(peak)}$.

In fact $v_{o(peak)}$ follows the maximum of $v_{i(peak)}$.

Circuits with OPAMPs and Diodes

Limiter

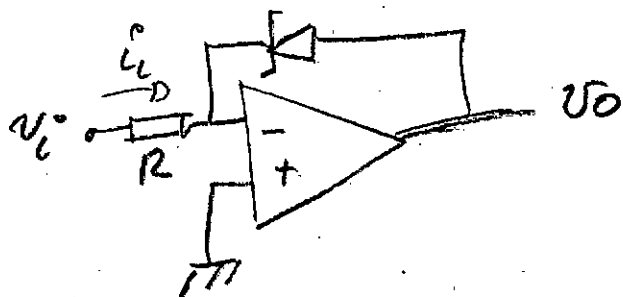

The OPAMP operates in negative feedback mode, because i_i flows through the diode.


So the diode state is ON or DIODE.

Then

$$V_i > 0 \Rightarrow V_i > 0 \Rightarrow V_o = -V_z$$

$$V_i < 0 \Rightarrow V_i < 0 \Rightarrow V_o \approx 0.7 \text{ Volt}$$

The transfer relationship?

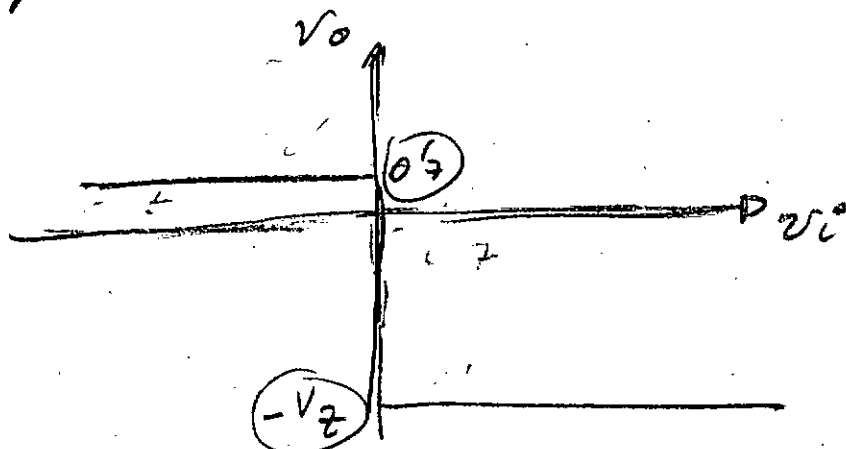


Symmetrical limiter


Analogue Systems

27/1/2012 (18)


DIODES

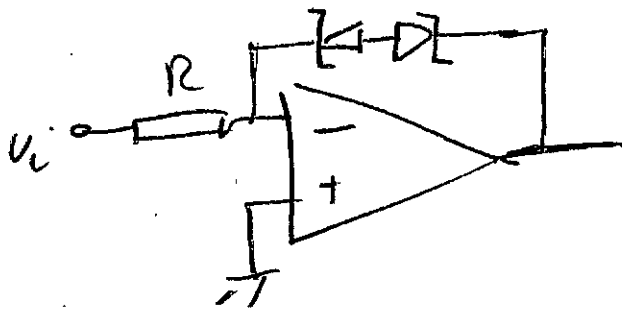

=>

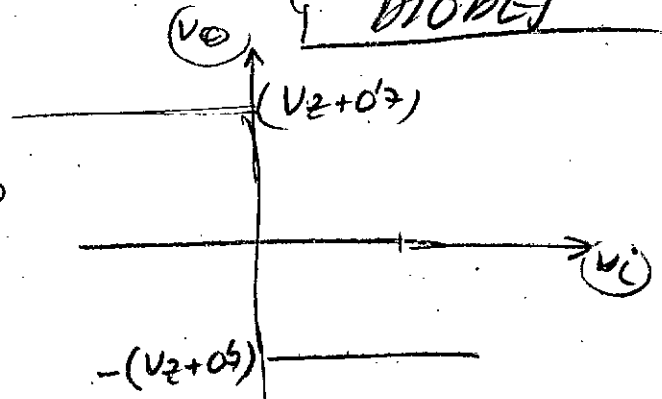


OR

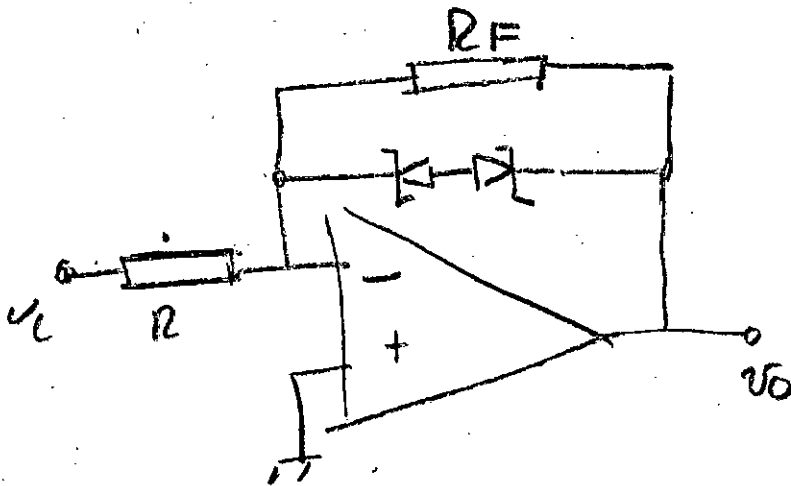


① If $\frac{|v_i|}{R} \cdot R_F < (V_z + 0.7)$: DIODES OFF
 That is : $|v_i| < (V_z + 0.7) \frac{R}{R_F} \Rightarrow v_o = -v_i \frac{R_F}{R}$

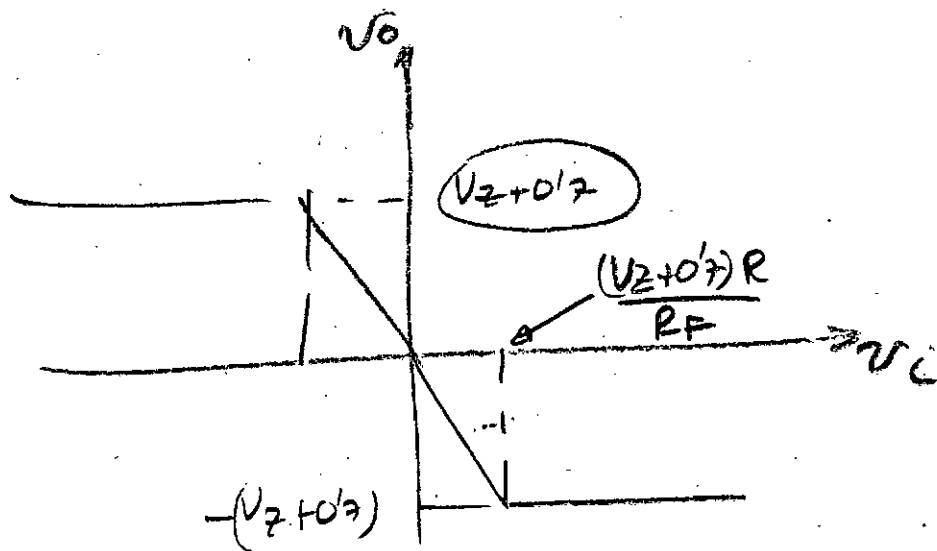② ELSE : DIODES ON
 $v_o = \pm (V_z + 0.7)$



Precision rectifier (half wave)

In fact, if $v_i(t)$ is processed by a precision-rectifier, $|v_i|$ is obtained.

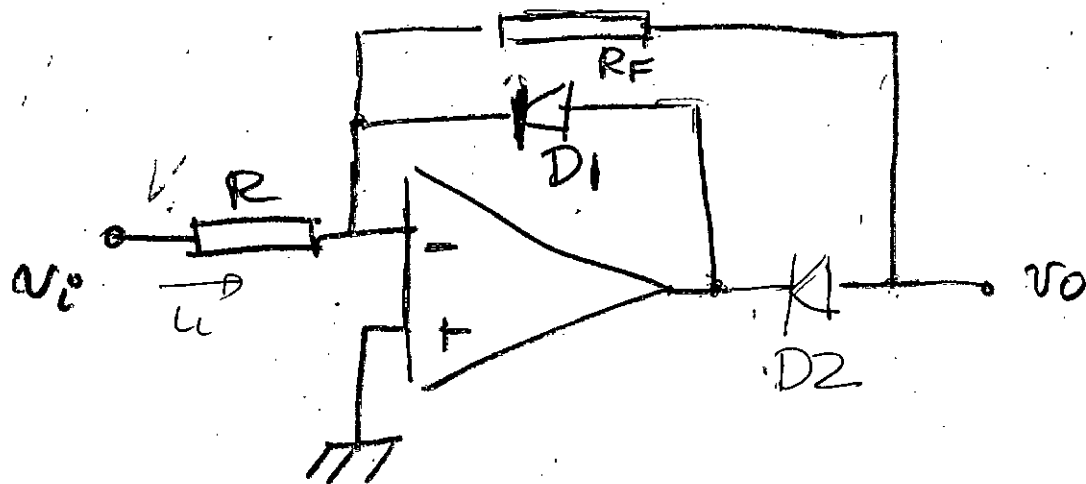


$v_i > 0 \Rightarrow i_i > 0 \Rightarrow \begin{cases} D2 \text{ ON} \\ D1 \text{ OFF} \end{cases} \Rightarrow v_o = -v_i \frac{R_F}{R}$

$v_i < 0 \Rightarrow \begin{cases} D1 \text{ ON} \\ D2 \text{ OFF} \end{cases} \Rightarrow v_o = 0$

Precision rectifier (full wave)

Analog Systems
27/1/2012 | 20
DIODES

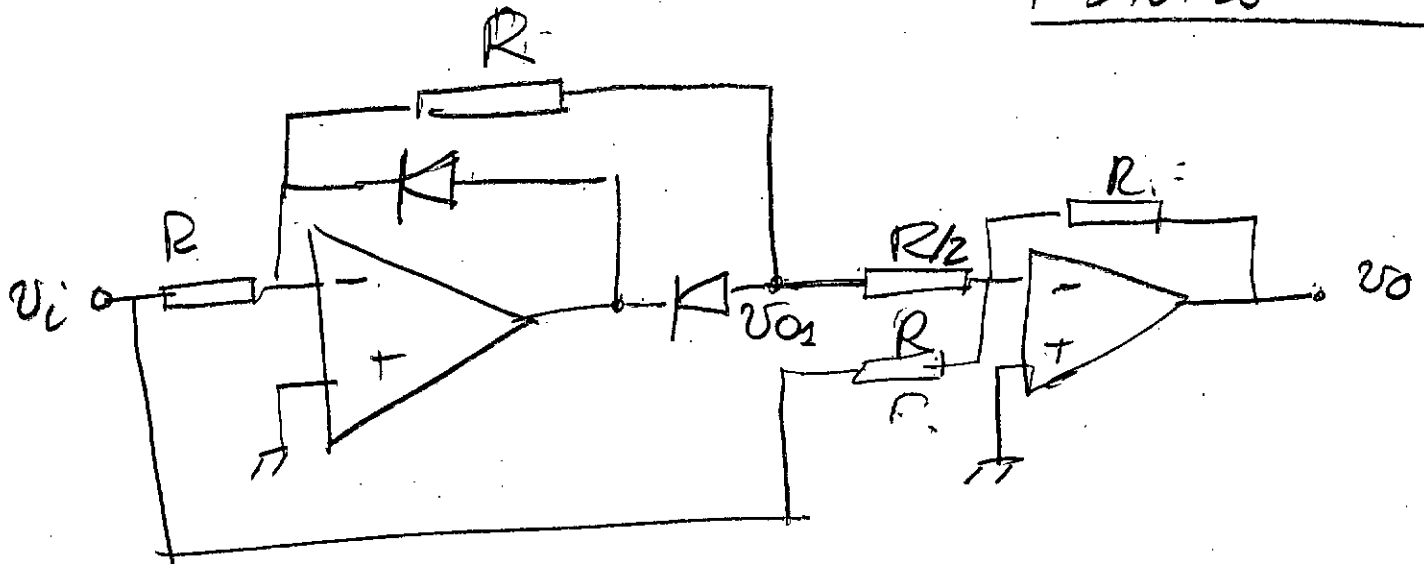

$$v_i > 0 \Rightarrow v_{o1} = -v_i \Rightarrow$$

$$v_o = v_{o1} \cdot \left(-\frac{R}{R/2}\right) + v_i \cdot \left(-\frac{R}{R}\right)$$

$$= +v_i \cdot 2 - v_i = v_i$$

$$v_i < 0 \Rightarrow v_o = -v_i$$

$$v_o = |v_i|$$