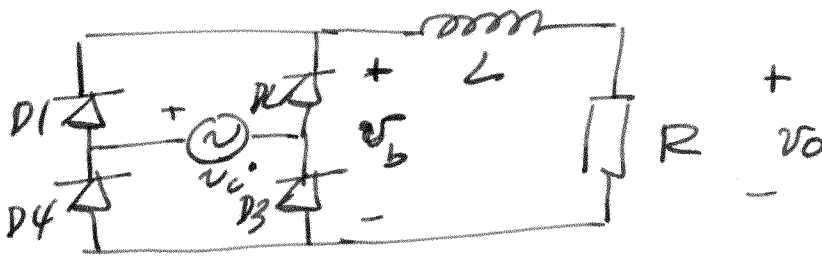


Full bridge rectifier with LR load 28/2/2013 ①



* The main goal is: $v_o(t) \stackrel{v}{=} \text{constant} = V_o |_{DC}$

HINT:

$v_b(t)$ is unknown (you can think about the bridge with resistive load, or with RC' load)

$v_b(t)$ is different in both cases.

In fact $v_b(t)$ depends on:

- 1) the full bridge rectifier
- 2) The load.

* Let's assume that $v_b(t)$ is:

- ① periodic
- ② $\bar{v}_b(t) \neq 0$ (DC level).

If it's so, the LR circuit analysis is performed as follows:

28/2/2013

(2)




Fourier series

$$v_b(t) = V_{DC} + \sqrt{V_{DC}} c(t) = V_{DC} + a_0 \cos(2\pi f_0 t + \phi_0) + a_1 \cos(4\pi f_0 t + \phi_1) + a_2 \cos(6\pi f_0 t + \phi_2) + \dots$$

Laplace analysis:
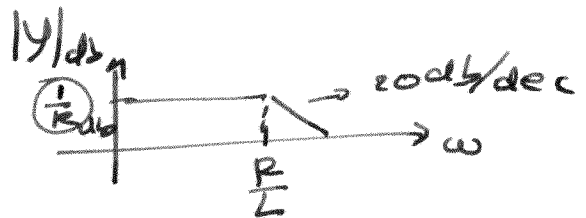
$$y(s) = \frac{I(s)}{V_b(s)} = \frac{1/L}{s + R/L}$$



If $\frac{R}{L} \ll 2\pi f_0$ (this meaning $L \uparrow \uparrow$),

the AC components in $i(t)$ can be neglected,

$$\text{and } i(t) \approx I_{DC} = \frac{V_{DC}}{R}.$$

Then $V_{o/DC} = I_{DC} \cdot R = V_{DC}$, that is

$V_{o/DC}$ is equal to the DC level of $v_b(t)$.

$$\text{So: if } \frac{R}{L} \downarrow \downarrow \Rightarrow \begin{cases} i(t) \approx I_{DC} \text{ (constant)} \\ v_o(t) \approx V_{o/DC} \text{ (constant)} \end{cases}$$

$$\text{where } I_{DC} = \frac{V_{o/DC}}{R}.$$


Let's see about v_{bct} :

28/2/2013

③

if $i_c \approx I_{oc}$ (constant), the ~~diodes are~~ bridge is
supplying intensity, there is in
every moment $\left\{ \begin{array}{l} (D1, D3) \text{ ON } (D2, D4) \text{ OFF} \\ \text{OR} \\ (D2, D4) \text{ ON } (D1, D3) \text{ OFF} \end{array} \right\}$

this meaning that

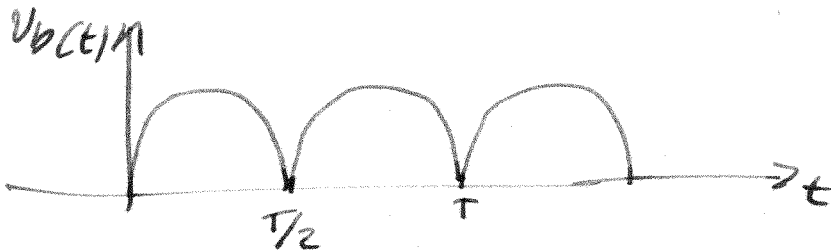

The frequency of the periodic wave v_{bct}
is $2f_i$ ($f_i \equiv$ frequency of v_i)

Then:

$f_0 = 2f_i$, this leading to: ~~the~~

$$2f_i \cdot 2\pi \rightarrow \frac{R}{L} \Rightarrow L_{min} = \frac{R}{2\pi f_i} \cdot 10$$

"Ten times criterion!"