

# Digital Systems

## Final examination. June 13, 2022

Time limit: 120 minutes.

Explain what you want to do and how you want to do it before doing anything else.

### 1 From VHDL code to a state diagram (20 %)

- Draw the block diagram of a typical synchronous (clock-driven) FSM that would be synthesized from a VHDL code made of one synchronous process and two combinational process).
- Draw the graph (or state diagram) of a synchronous (clock-driven) FSM described by

```
library ieee;
use ieee.std_logic_1164.all, ieee.numeric_std.all;

entity fsm is
  port( clk, s_coin, flag_60, flag_600 : in std_logic;
        s_temp : in std_logic_vector(6 downto 0);
        s_fan, s_heater, s_drum, s_right : out std_logic);
end;

architecture arch of fsm is
  type multiplier_state is (I, RH, LH, R, L);
  signal current_state : multiplier_state := I;
  signal next_state : multiplier_state;

begin
  state_reg : process(clk) is
  begin
    if rising_edge(clk) then current_state <= next_state;
    end if;
  end process;

  next_state_logic : process(current_state, flag_60,
                             flag_600, s_coin, s_temp) is
  begin
    next_state <= current_state;
    case current_state is
      when I =>
        if s_coin='1' then next_state <= RH;
        end if;
      when RH =>
        if flag_600='1' then next_state <= I;
        elsif flag_60='1' and unsigned(s_temp)<=80 then
          next_state <= LH;
        elsif flag_60='1' and unsigned(s_temp)>80 then
          next_state <= L;
        elsif flag_60='0' and unsigned(s_temp)>80 then
          next_state <= R;
        end if;
      when LH =>
```

```

    if flag_600='1' then next_state <= I;
    elsif flag_60='1' and unsigned(s_temp)<=80 then
        next_state <= RH;
    elsif flag_60='1' and unsigned(s_temp)>80 then
        next_state <= R;
    elsif flag_60='0' and unsigned(s_temp)>80 then
        next_state <= L;
    end if;
when R =>
    if flag_600='1' then next_state <= I;
    elsif flag_60='1' and unsigned(s_temp)>=70 then
        next_state <= L;
    elsif flag_60='1' and unsigned(s_temp)<70 then
        next_state <= LH;
    elsif flag_60='0' and unsigned(s_temp)<70 then
        next_state <= RH;
    end if;
when L =>
    if flag_600='1' then next_state <= I;
    elsif flag_60='1' and unsigned(s_temp)>=70 then
        next_state <= R;
    elsif flag_60='1' and unsigned(s_temp)<70 then
        next_state <= RH;
    elsif flag_60='0' and unsigned(s_temp)<70 then
        next_state <= LH;
    end if;
when others => null;
end case;
end process;

output_logic : process (current_state) is
begin
    s_fan <= '1'; s_heater <= '1'; s_drum <= '1'; s_right <= '1';
    case current_state is
        when I => s_fan <= '0'; s_heater <= '0';
            s_drum <= '0'; s_right <= '0';
        when RH => null;
        when LH => s_right <= '0';
        when R => s_heater <= '0';
        when L => s_heater <= '0'; s_right <= '0';
        when others => null;
    end case;
end process;
end;
```

## 2 An edge detector of asynchronous signals (10 %)

Design a **falling** edge detector for asynchronous signals.

- a) First draw the block diagram.
- b) Next describe it in VHDL.

### 3 Unregistering a signal (10 %)

The following VHDL code shows two registered signals: *a* is of type `unsigned(2 downto 0)` and *flag* is of type `std_logic`.

```
process(clk) is
begin
  if rising_edge(clk) then
    flag<='0';
    if a=5 then a<=(others=>'0');
    else a<=a+1;
    end if;
    if a=4 then flag<='1'; end if;
  end if;
end process;
```

- How many 1-bit flip-flops are used to synthesize this code?
- Reduce this number unregistering some signals without changing the functionality of the circuit. Describe in VHDL the new circuit.
- How many 1-bit flip-flops are used in this new synthesis?

### 4 Designing a time counter (20 %)

We want to describe in VHDL a counter of seconds (up to 59) and minutes (up to 59) following the structure of the next block diagram, where the signals *flag\_s* and *flag\_m* are an enable signal to the next block. The frequency of the signal *clk* is 10 Hz.

 


Figure 1: Block diagram of the time counter.

- First, identify the inputs and outputs (and its size) of the whole entity named `counter`. These inputs and outputs are of type `std_logic` or `std_logic_vector`.
- Next, describe the whole entity using one process for each one of the three blocks.

## 5 Designing a new AVR instruction (15 %)

Consider a modified Mini AVR that only has the following set of instructions.

- LDI Rd,K; Opcode: 1110 KKKK dddd KKKK
- MOV Rd,Rr; Opcode: 0010 11rd dddd rrrr
- IN Rd,A; Opcode: 1011 0AA dddd AAAA
- OUT A,Rr; Opcode: 1011 1AAr rrrr AAAA
- LD Rd, X; Opcode: 1001 000d dddd 1100
- ST X, Rr; Opcode: 1001 001r rrrr 1100

We want to add a new instruction that stores an 8 bit constant (a literal) to an output with the following syntax:

- OUTI A,K

- Propose an Opcode compatible with the existing set of instructions. Point out the range of each of the operands.
- Considering the block diagram of *Figure 2*, highlight the signals and blocks that will be used by this instruction and add, if necessary, new signals and blocks.
- Which blocks of this diagram will be modified to consider the new instructions? Briefly explain these modifications.

## 6 Understanding assembler code (15 %)

The Mini AVR architecture of *Figure 2* has in its ROM the following code:

```
0.  NOP
1.  LDI r17,0x0F
2.  IN r16,1
3.  EOR r16,r17
4.  NOP
5.  BRNE -4
6.  RJMP -1
```

- Draw a waveform with the first 8 clocks after a general reset<sup>1</sup>, considering that the asynchronous input port\_A1<sup>2</sup>, changes from 0x00 to 0x0F immediately after the first rising clock. Draw the value of:
  - program counter: pr\_pc
  - port\_A1 asynchronous input
  - r16 register
  - Z flag of the status register

<sup>1</sup>This general reset is not shown in *Figure 2*.

<sup>2</sup>See *Figure 2*.

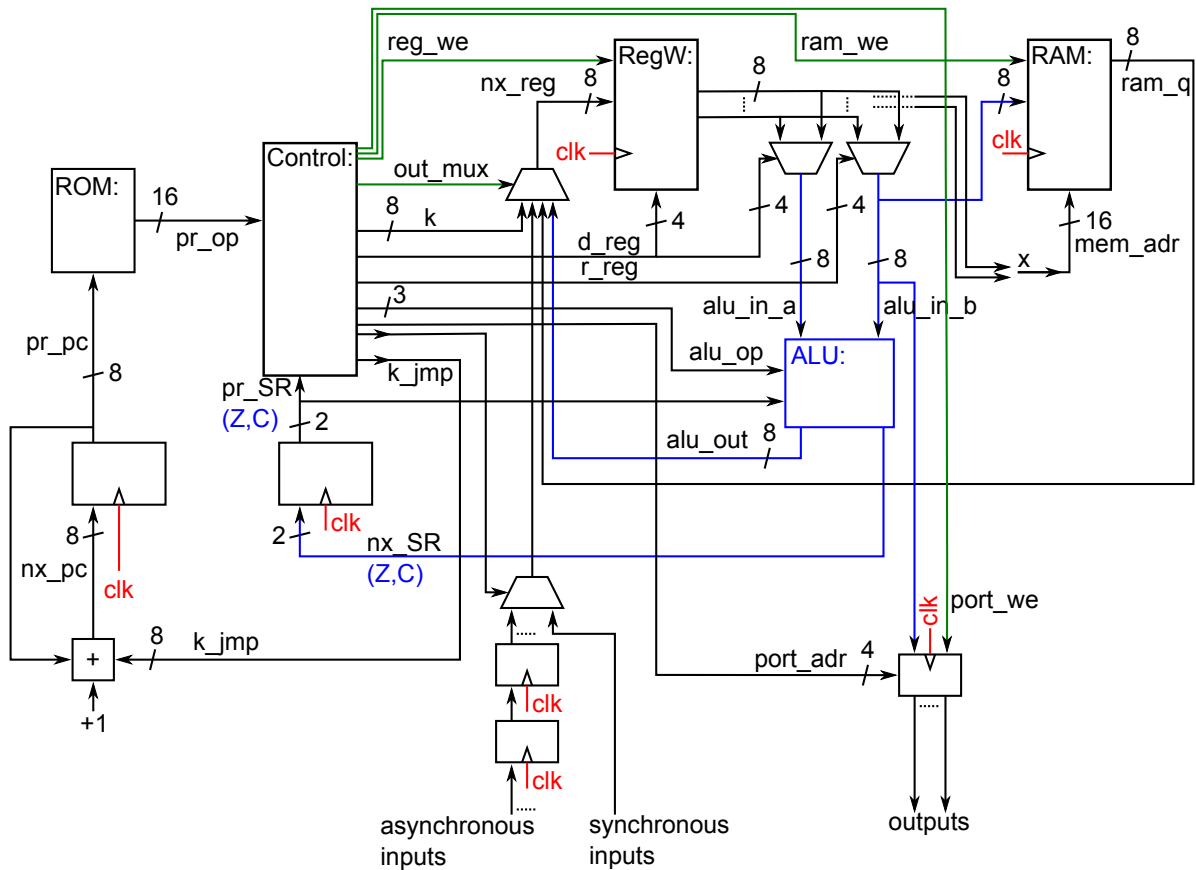


Figure 2: Mini AVR block diagram.

## 7 From assembler to opcode (5 %)

a) Knowing the syntax and opcode of the following instructions,

- LDI Rd,K; Opcode: 1110 KKKK dddd KKKK
- OUT A,Rr; Opcode: 1011 1AAr rrrr AAAA

and considering the next assembler instructions

```
0. LDI r30,0xAA
1. OUT 8,r30
```

indicate the bits in the first two positions of the Mini AVR program ROM.

## 8 Storing a literal to RAM (5 %)

a) Write the assembler instructions needed to store the value 55 in the position 512 of the Mini AVR data RAM.