

Digital Systems - Mini AVR 1

Implementing NOP, LDI, ADC, MOV


Pere Palà Schönwälder

iTIC <http://itic.cat>

April 2025

Processor Basics


- ▶ Processor: A specific (and interesting) (and complex) kind of digital system
- ▶ A processor inside a digital system
 - ▶ Specialized tasks
 - ▶ Multiple small processors
 - ▶ Other digital circuitry complements the system
- ▶ Processor basics
 - ▶ A list of instructions
 - ▶ Space to store data
 - ▶ Core that acts according to instructions
 - ▶ Input and output ports to interact with the real world
- ▶ Architectures
 - ▶ Von Neumann
 - ▶ Harvard

 

Intel 4004

Harvard Architecture

 - ▶ Separate memories
 - ▶ Program (instruction) memory
 - ▶ Data memory




- ▶ Allows accessing instructions and data simultaneously
- ▶ Eliminates bottleneck of common bus
- ▶ Common in small micro-controllers, such as the Atmel AVR

The Mini AVR

- ▶ Objective
 - ▶ To build a small AVR-compatible micro-controller
 - ▶ With a reduced number of instructions
- ▶ Why?
 - ▶ Just for fun!
 - ▶ To be able to port an AVR program to our micro-controller
- ▶ Instructions
 - ▶ NOP : No operation
 - ▶ LDI : Load immediate
 - ▶ ADC : Add with carry
 - ▶ MOV : Move
 - ▶ AND, OR, EOR : And, or, exclusive-or operations
 - ▶ RJMP : Relative jump
 - ▶ BREQ : Branch if equal
- ▶ Some flags of the Status Register (SREG)
 - ▶ C: Carry Flag
 - ▶ Z: Zero Flag

Overview (don't panic yet!)

 

Documentation of AVR instructions : NOP

- ▶ NOP – No Operation
- ▶ Description
 - ▶ This instruction performs a single cycle No Operation.
- ▶ Operation: No
- ▶ Syntax: NOP
- ▶ Operands: None
- ▶ Program Counter: $PC \leftarrow PC + 1$
- ▶ 16-bit Opcode: 0000 0000 0000 0000
- ▶ Status Register (SREG) and Boolean Formula:

I T H S V N Z C

- - - - -

Documentation of AVR instructions : LDI

- ▶ LDI – Load Immediate
- ▶ Description:
 - ▶ Loads an 8 bit constant directly to register 16 to 31.
- ▶ Operation: $Rd \leftarrow K$
- ▶ Syntax: LDI Rd,K
- ▶ Operands: $16 \leq d \leq 31, 0 \leq K \leq 255$
- ▶ Program Counter: $PC \leftarrow PC + 1$
- ▶ 16-bit Opcode: 1110 KKKK dddd KKKK
- ▶ Status Register (SREG) and Boolean Formula:

I T H S V N Z C

- - - - -

Documentation of AVR instructions : ADC

- ▶ ADC – Add with Carry
- ▶ Description:
 - ▶ Description: Adds two registers and the contents of the C Flag and places the result in the destination register Rd.
- ▶ Operation: $Rd \leftarrow Rd + Rr + C$
- ▶ Syntax: ADC Rd,Rr
- ▶ Operands: $0 \leq d \leq 31, 0 \leq r \leq 31$
- ▶ Program Counter: $PC \leftarrow PC + 1$
- ▶ 16-bit Opcode: 0001 11rd dddd rrrr
- ▶ Status Register (SREG) and Boolean Formula:
I T H S V N Z C
- - ⇔⇔⇔⇔⇔⇔
- ▶ Z: Set if the result is x"00"; cleared otherwise.
- ▶ C: Set if there was carry from the MSB of the result; cleared otherwise

Documentation of AVR instructions : MOV


- ▶ MOV – Copy Register
- ▶ Description:
 - ▶ This instruction makes a copy of one register into another.
The source register Rr is left unchanged, while the destination register Rd is loaded with a copy of Rr.
- ▶ Operation: $Rd \leftarrow Rr$
- ▶ Syntax: MOV Rd,Rr
- ▶ Operands: $0 \leq d \leq 31, 0 \leq r \leq 31$
- ▶ Program Counter: $PC \leftarrow PC + 1$
- ▶ 16-bit Opcode: 0010 11rd dddd rrrr
- ▶ Status Register (SREG) and Boolean Formula:
I T H S V N Z C
- - - - -

References

- ▶ Further information:
- ▶ 8-bit AVR instruction set manual.

Registers

 - ▶ Implement only registers from 16 to 31
- ▶ ADC 16-bit Opcode
 - ▶ 0001 11rd dddd rrrr
 - ▶ 0001 1111 dddd rrrr
- ▶ No stack, stack pointer, etc



VHDL implementation of registers


```
type register_bank is
    array (15 downto 0) of std_logic_vector(7 downto 0);
signal regs : register_bank;           --Registers r16..r31
```

```
RegW : process(clk) --Register write
begin
    if rising_edge(clk) then
        if reg_we = '1' then -- write
            regs(to_integer(unsigned(d_reg))) <= nx_reg;
        end if;
    end if;
end process RegW;
```

```
--Register read: ALU inputs
alu_in_a <= regs(to_integer(unsigned(d_reg)));
alu_in_b <= regs(to_integer(unsigned(r_reg)));
```

Program ROM

 - ▶ 256 positions (arbitrary limit)
 - ▶ Program Counter has to be 8 bits long
- ▶ 16-bit opcodes
- ▶ Not clocked: Purely combinational ROM
- ▶ Given `pr_pc`, the present program counter, the system outputs `pr_op`, the present opcode



Program listing

- ▶ A simple program code:

```
NOP          ; do nothing
LDI r16,x83   ; r16 ← x83
ADC r16,r16    ; x83 + x83 = x106 : r16 ← 06 and C is set!
ADC r16,r16    ; x06 + x06 + x01 = x0D and C is cleared
MOV r17,r16    ; r17 ← x0D
NOP          : do nothing
```

- ▶ NOP : 0000 0000 0000 0000
- ▶ LDI : 1110 kkkk dddd kkkk
- ▶ ADC : 0001 1111 dddd rrrr (0001 11rd dddd rrrr)
- ▶ MOV : 0010 1111 dddd rrrr (0010 11rd dddd rrrr)
- ▶ The first 4 bits are enough to determine the instruction
- ▶ VHDL definition:

```
constant NOP : std_logic_vector(3 downto 0) := "0000";
constant LDI : std_logic_vector(3 downto 0) := "1110";
constant ADC : std_logic_vector(3 downto 0) := "0001";
constant MOV : std_logic_vector(3 downto 0) := "0010";
```

VHDL implementation of the program memory

```
ROM : process(pr_pc) --Program ROM
begin
  case pr_pc is
    when X"00" =>
      pr_op <= NOP & "0000" & "-----";      -- NOP
    when X"01" =>
      pr_op <= LDI & "1000" & "0000" & "0011"; -- LDI r16,x83
    when X"02" =>
      pr_op <= ADC & "1111" & "0000" & "0000"; -- ADC r16,r16
    when X"03" =>
      pr_op <= ADC & "1111" & "0000" & "0000"; -- ADC r16,r16
    when X"04" =>
      pr_op <= MOV & "1111" & "0001" & "0000"; -- MOV r17,r16
    when X"05" =>
      pr_op <= NOP & NOP      & "-----";      -- NOP
    when others => pr_op <= (others => '-');
  end case;
end process;
```

- This works as a first try! Later we will learn to describe a ROM in a way that allows the synthesis tools to choose (much) better implementations.


VHDL Implementation of the Status Register

```
type status_reg is
  record
    Z : std_logic;
    C : std_logic;
  end record;
```

```
signal pr_SR,
        nx_SR    : status_reg;
```

Control Unit

 - ▶ Input: Present opcode
- ▶ Decode the instruction
- ▶ Generate signals:
 - ▶ Register write enable `reg_we`
 - ▶ Output multiplexer selection: decide if data written to register comes from:
 - ▶ The present opcode (such as LDI)
 - ▶ The ALU (such as ADC)
 - ▶ Generate d and r register addresses `d_reg`, `s_reg`
 - ▶ Indicate the desired operation to the ALU `alu_op`



VHDL Implementation of the Control Unit (1/2)

```
type    out_mux_type is (mux_alu,mux_lit);  
signal  out_mux      : out_mux_type;
```

```
CONTROL : process(pr_op)  
begin  
    r_reg    <= (others => '-');      --Defaults  
    d_reg    <= (others => '-');  
    k        <= (others => '-');  
    ALU_op   <= (others => '-');  
    reg_we   <= '0';  
    case pr_op(15 downto 12) is -- These bits are enough to  
                                -- decide among our reduced  
                                -- instruction set!  
    when NOP => -----NOP Instruction  
        null;  
  
    when LDI => -----LDI Instruction  
        d_reg    <= pr_op(7 downto 4);  
        out_mux  <= mux_lit;  
        k        <= pr_op(11 downto 8) & pr_op(3 downto 0);  
        reg_we   <= '1';
```

VHDL implementation of the Control Unit (2/2)

```
when MOV => -----MOV Instruction
    r_reg    <= pr_op(3 downto 0);  --Source register
    d_reg    <= pr_op(7 downto 4);  --Destination register
    out_mux  <= mux_alu;
    reg_we   <= '1';                --Enable register write
    ALU_op   <= ALU_MOV;


when ADC => -----ADC Instruction
    r_reg    <= pr_op(3 downto 0);
    d_reg    <= pr_op(7 downto 4);
    out_mux  <= mux_alu;
    reg_we   <= '1';                --Enable register write
    ALU_op   <= ALU_ADC;

when others =>
    null;
end case;
end process;
```

```
constant ALU_MOV  : std_logic_vector(2 downto 0) := "010";
constant ALU_ADC  : std_logic_vector(2 downto 0) := "001";
```

The ALU: Arithmetic and Logic Unit

 - ▶ Inputs
 - ▶ Operands `alu_in_a`, `alu_in_b`
 - ▶ Operation code `alu_op`
 - ▶ Status register (for carry) `pr_SR`
- ▶ Outputs
 - ▶ Operation result `alu_out`
 - ▶ Updated status register `nx_SR`




VHDL implementation of the ALU

```
ALU : process(alu_op,alu_in_a,alu_in_b,pr_SR,add_temp)
begin
    nx_SR <= pr_SR;      --by default, preserve status register
    add_temp <= (others => '-');
    case alu_op is
    when ALU_MOV => -----MOV: in_b --> out
        alu_out <= alu_in_b;
    when ALU_ADC => -----ADC: Carry in/out
        add_temp <= std_logic_vector(      --auxiliar SLV(9..0)
            unsigned('0' & alu_in_a & '1') +
            unsigned('0' & alu_in_b & pr_SR.C));  --Carry In
        alu_out <= add_temp(8 downto 1);
        nx_SR.C <= add_temp(9);                  --Update Carry Flag
        if add_temp(8 downto 1) = x"00" then --Update Zero Flag
            nx_SR.Z <= '1';
        else
            nx_SR.Z <= '0';
        end if;
    when others => -----Should not happen
        alu_out <= (others => '-');      --Don't care
    end case;
end process;
```

Register Data-In Multiplexer

 - ▶ Decide which data has to be stored in one of the registers
 - ▶ Data from the ALU, as in ADC or MOV instructions
 - ▶ Data from the opcode, as in the LDI instruction





VHDL implementation of the Register Multiplexer

```
MUX : process(out_mux, alu_out, k)
begin
    case out_mux is
        when mux_alu  => nx_reg <= alu_out;
        when mux_lit  => nx_reg <= k;
        when others   => nx_reg <= (others => '-');
    end case;
end process;
```

Synchronous Elements

  - ▶ Registered signals
 - ▶ Program counter `pr_pc`
 - ▶ Status register `pr_SR`



VHDL implementation of the Synchronous Elements

```
process(clk,reset) --Synchronous elements
begin
    if reset='1' then          --Initialize Processor
        pr_pc <= (others => '0');
        pr_SR.C <='0';
        pr_SR.Z <='0';
    elsif (rising_edge(clk)) then
        pr_pc      <= nx_pc;
        pr_SR      <= nx_SR;
    end if;
end process;

nx_pc      <= std_logic_vector(unsigned(pr_pc) + 1);
```

Whole Processor

► Entity

```
entity mini_avr_01 is
  port (
    clk      : in  std_logic;
    reset    : in  std_logic;
    -- Let's have some registers as outputs :
    r16      : out std_logic_vector( 7 downto 0);
    r17      : out std_logic_vector( 7 downto 0)
  );
end entity;
```

► Auxiliar signals for debugging

```
r16 <=regs(0);
r17 <=regs(1);
debug_carry <= pr_SR.C;
debug_zero  <= pr_SR.Z;
```

Simulation

