

Digital Systems - Mini AVR 3

Adding I/O Ports

Implementing Custom Modules: Timer

Pere Palà Schönwälder

iTIC <http://itic.cat>

April 2025

Input Ports

- ▶ We have mapped some registers as outputs
- ▶ Inputs?
- ▶ Specific instructions to interact with the world.
 - ▶ IN Rd,A
 - ▶ OUT A,Rr


Documentation of AVR instructions : IN

- ▶ IN - Load an I/O Location to Register
- ▶ Description:
 - ▶ Loads data from the I/O Space (Ports, Timers, Configuration Registers etc.) into register Rd in the Register File.
- ▶ $Rd \leftarrow I/O(A)$
- ▶ Syntax: IN Rd,A
- ▶ Operands: $0 \leq d \leq 31, 0 \leq A \leq 63$
- ▶ Program Counter: $PC \leftarrow PC + 1$
- ▶ 16-bit Opcode: 1011 0AA dddd AAAA
- ▶ Status Register (SREG) and Boolean Formula:
I T H S V N Z C
- - - - -

Documentation of AVR instructions : OUT

- ▶ OUT – Store Register to I/O Location
- ▶ Description:
 - ▶ Stores data from register Rr in the Register File to I/O Space (Ports, Timers, Configuration Registers etc.).
- ▶ $I/O(A) \leftarrow R_r$
- ▶ Syntax: OUT A,Rr
- ▶ Operands: $0 \leq r \leq 31, 0 \leq A \leq 63$
- ▶ Program Counter: $PC \leftarrow PC + 1$
- ▶ 16-bit Opcode: 1011 1AAr rrrr AAAA
- ▶ Status Register (SREG) and Boolean Formula:
I T H S V N Z C
- - - - -

Schematic: IN

 

VHDL implementation. IN

```
case pr_op(15 downto 12) is
    ...
    when IN_OUT =>
        if pr_op(11)='1' then -- OUT
        else -- IN
            out_mux <= mux_in_out;
            d_reg  <= pr_op(7 downto 4); --Destination register
            reg_we <= '1';
            case pr_op(1 downto 0) is --Decode IN address
                when "00" => in_data <= synchA0;
                when "01" => in_data <= synchA1;
                when "10" => in_data <= timer_state;
                when others => null;
            end case;
        end if;
    end if;
```


```
MUX: process(out_mux, alu_out, k, in_data) --Out MUX
begin
    case out_mux is
        ...
        when mux_in_out => nx_reg <= in_data;
        when others      => nx_reg <= (others => '-');
    end case;
end process;
```

VHDL implementation. IN (synchronizer)


```
process(clk,reset) --Synchronous elements
begin
    if reset='1' then
        ...
    elsif (rising_edge(clk)) then
        ...
        -- synchronizer for inputs ports
        presynchA0 <= port_A0;
        synchA0    <= presynchA0;
        presynchA1 <= port_A1;
        synchA1    <= presynchA1;
    end if;
end process;
```

Sample code

```
NOP          ; program waits until r17=x01
LDI  r16,x01
IN    r17,x0  ; <----
EOR   r17,r16 ;      |
BRNE  -3      ; ----
NOP
NOP
RJMP  -1      ; HALT
```

 

Schematic: OUT

 


VHDL implementation. OUT

```
... -- add new default (port_we,...)
case pr_op(15 downto 12) is
  ...
  when IN_OUT =>
    if pr_op(11)='1' then -- OUT
      port_we  <= '1';
      port_adr <= pr_op(3 downto 0);
      r_reg  <= pr_op(7 downto 4);
    else
      -- IN
    end if;
```

VHDL implementation. OUT

```
PortW: process(clk)
begin
    if rising_edge(clk) then
        if port_we = '1' then
            case port_adr is
                when "1000" =>
                    port_A8i <= regs(to_integer(unsigned(r_reg)));
                when "1001" =>
                    port_A9i <= regs(to_integer(unsigned(r_reg)));
                when "1010" =>
                    timer_limit <= regs(to_integer(unsigned(r_reg)));
                when others => null;
            end case;
        end if;
    end if;
end process PortW;
```

Implementing a Timer

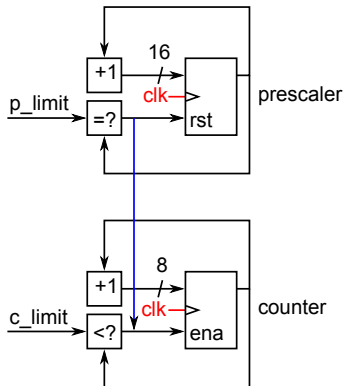

- ▶ Prescaler limit : hard coded
 - ▶ Each prescaler terminal count enables the timer counter
- ▶ Counter limit : `timer_limit` mapped to port 10 1010
- ▶ Counter keeps counting until reaching the limit
- ▶ This is signaled through `timer_state` mapped to port 2 0010

VHDL implementation of timer

```
timer_state <= x"00" when timer_count = timer_limit
                    else x"01";  -- 1:counting 0:finished
presc_tc <= '1' when presc_count=presc_count_limit--constant
                    else '0';


process(clk)
begin
    if rising_edge(clk) then
        if port_we='1' and port_adr="1010"then--reset counter
            timer_count <= (others => '0');      --when writing
            presc_count <= (others => '0');      --new timer_limit
        else
            if timer_state /= x"00" and presc_tc='1' then
                timer_count <=
                    std_logic_vector(unsigned(timer_count)+1);
            end if;
            if presc_tc='1' then
                presc_count <= (others => '0');
            else
                presc_count <=
                    std_logic_vector(unsigned(presc_count)+1);
            end if;
        end if;
    end if;
end process;
```

Sample code with Timer

```
NOP                ; program waits until r17=x01
LDI  r16,x01
IN   r17,x0        ; <----
EOR  r17,r16        ;      |
BRNE -3            ; -----
OUT  8,r16
EOR  r16,r16        ; clear r16
LDI  r18,x0F        ; value of timer_limit
OUT  10,r18         ; set timer_limit
IN   r17,2          ; read timer_state  <-----
OR   r17,r16        ; r16 is zero, this tests for zero      |
BRNE -3            ; -----
RJMP -1            ; HALT
```


Sample code with Timer. Initial Waveforms

 Simulation with `presc_count_limit = 4`, meaning 5 system clocks per terminal count



Sample code with Timer. Initial Waveforms

Simulation with `presc_count_limit = 4`

 

- ▶ Instruction #8 (`OUT 10,r18`) sets `timer_limit=x0F` at $t = 21 \mu s$, its effect being seen at $t = 22 \mu s$
- ▶ `timer_state` becomes 1 at $t = 22 \mu s$ and reaches 0 at $t = 97 \mu s$. This means an interval of 85 (5×15) μs
- ▶ loop exits after the next read of `timer_state` at $t = 100 \mu s$