

# Digital Systems - 1

Pere Palà - Alexis López

iTIC <http://itic.cat>

February 2016

# Boolean functions

▶  $f(A, B, C) = A \cdot B + \bar{A} \cdot \bar{C}$

```
library ieee;
use ieee.std_logic_1164.all;

entity boolean_function is
    port( A, B, C : in  std_logic;
          f       : out std_logic);
end boolean_function;

architecture my_arch of boolean_function is
begin
    f <= (A and B) or ((not A) and (not C));
end;
```

- ▶ Precedence rules: Highest priority first

```
not
and
or
nand
nor
xor
xnor
```

# Traffic light controller

- ▶ Define a bus: one-hot encoding (red, yellow, green)

```
entity light_controller is
  port( lights_in  : in  std_logic_vector (3 downto 1);
        enable    : in  std_logic;
        lights_out : out std_logic_vector (3 downto 1));
end entity light_controller;


architecture and_enable of light_controller is
begin
  lights_out(1) <= lights_in(1) and enable;
  lights_out(2) <= lights_in(2) and enable;
  lights_out(3) <= lights_in(3) and enable;
end architecture and_enable;
```

- ▶ Alternative

```
architecture conditional_enable of light_controller is
begin
  lights_out <= lights_in when enable = '1' else
                "000";
end architecture conditional_enable;
```
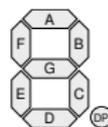
# 7 segment decoder

- ▶ Input: BCD coded
- ▶ Output: 7 segment



```
entity BCDdecoder is
  port( BCD_in      : in  std_logic_vector (3 downto 0);
        segments_out : out std_logic_vector (6 downto 0));
end entity BCDdecoder;

architecture my_arch of BCDdecoder is
begin
  segments_out <= "1111110" when BCD_in = "0000" else
                 "0110000" when BCD_in = "0001" else
                 "1101101" when BCD_in = "0010" else
                 "1111001" when BCD_in = "0011" else
                 "0110011" when BCD_in = "0100" else
                 "1011011" when BCD_in = "0101" else
                 "1011111" when BCD_in = "0110" else
                 "1110000" when BCD_in = "0111" else
                 "1111111" when BCD_in = "1000" else
                 "1110011" when BCD_in = "1001" else
                 "-----";
end architecture my_arch;
```

## 7 segment decoder /2

- ▶ Less typing: with ... select ...

```
entity BCDdecoder is
  port( BCD_in      : in  std_logic_vector (3 downto 0);
        segments_out : out std_logic_vector (6 downto 0));
end entity BCDdecoder;

architecture my_arch of BCDdecoder is
begin
  with BCD_in select
    segments_out <= "1111110" when "0000",
                   "0110000" when "0001",
                   "1101101" when "0010",
                   "1111001" when "0011",
                   "0110011" when "0100",
                   "1011011" when "0101",
                   "1011111" when "0110",
                   "1110000" when "0111",
                   "1111111" when "1000",
                   "1110011" when "1001",
                   "-----" when others;
end architecture my_arch;
```

## 7 segment decoder /3

### ► Adding a blanking input

```
entity BCDdecoder is
  port( BCD_in      : in  std_logic_vector (3 downto 0);
        blank      : in  std_logic_vector;
        segments_out : out std_logic_vector (6 downto 0));
end entity BCDdecoder;

architecture my_arch of BCDdecoder is
  signal temp_segs : std_logic_vector (6 downto 0);
begin
  with BCD_in select
    temp_segs <= "1111110" when "0000",
                "0110000" when "0001",
                "1101101" when "0010",
                "1111001" when "0011",
    ...
                "1111111" when "1000",
                "1110011" when "1001",
                "-----" when others;

  segments_out <= "0000000" when blank = '1' else
                 temp_segs;
end architecture my_arch;
```