


Digital Systems - 3

Pere Palà - Alexis López

iTIC <http://itic.cat>

February 2016

D Flip-Flop

 

```
signal d, q    : std_logic;
...
my_dff: process (clk) is
begin
    if rising_edge(clk) then
        q <= d;
    end if;
end process my_dff;
```


Process statement

```
name1: process (a,b,c) is
begin
    sequential statement 1a;
    sequential statement 2a;
    ...
end process name1;

name2: process (c,d,e) is
begin
    sequential statement 1b;
    sequential statement 2b;
    ...
end process name1;
```


- ▶ Process `name1` is (only!) triggered when `a`, `b` or `c` changes. This is the sensitivity list.
- ▶ Inside a process, the statements are executed in order.
- ▶ Process `name1` is executed concurrently with process `name2`

D Flip-Flop on a bus with clock enable

 


```
signal d, q      : std_logic_vector (7 downto 0);
signal ce       : std_logic;
...
my_dff: process (clk) is
begin
    if rising_edge(clk) then
        if ce = '1' then
            q <= d;
        end if;
    end if;
end process my_dff;
```

D Flip-Flop with Asynchronous Reset

 

```
signal d, q    : std_logic_vector(7 downto 0);
signal reset   : std_logic;
...
my_dff: process (clk,reset) is
begin
    if reset = '1' then --reset overrides everything !
        q <= "00000000";
    elsif rising_edge(clk) then
        q <= d;
    end if;
end process my_dff;
```

D Flip-Flop with Synchronous Reset

 

```
signal d, q    : std_logic_vector (7 downto 0);
signal reset   : std_logic;
...
my_dff: process (clk) is
begin
    if rising_edge(clk) then
        if reset = '1' then
            q <= (others => '0');
        else
            q <= d;
        end if;
    end if;
end process my_dff;
```