

# Digital Systems - 6


Pere Palà - Alexis López

iTIC <http://itic.cat>

March 2016
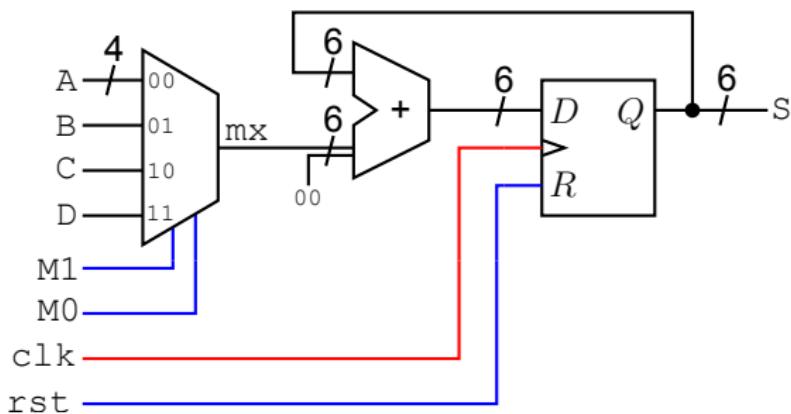
# Sequential Datapath and Control Section

- ▶ Objective: To add 4 numbers of 4 bits
- ▶ Restriction: Only one adder.
- ▶ Datapath
- ▶ Control Section




# Datapath

```
signal A,B,C,D,mx      : std_logic_vector(3 downto 0);
signal clk,rst         : std_logic;
signal M               : std_logic_vector(1 downto 0);
signal addA,addB,addOut,
      Din,Q,S       : std_logic_vector(5 downto 0);
begin
  with M select
    mx <= A when "00", B when "01",
              C when "10", D when "11", "----" when others;
  addA   <= Q;
  addB   <= "00" & mx;
  addOut <= std_logic_vector(unsigned(addA)+unsigned(addB));
  Din    <= addOut;
  process(clk)
  begin
    if rising_edge(clk) then
      if rst='1' then
        Q<="000000";
      else
        Q <= Din;
      end if;
    end if;
  end process;
  S<=Q;
end;
```


# Control Section
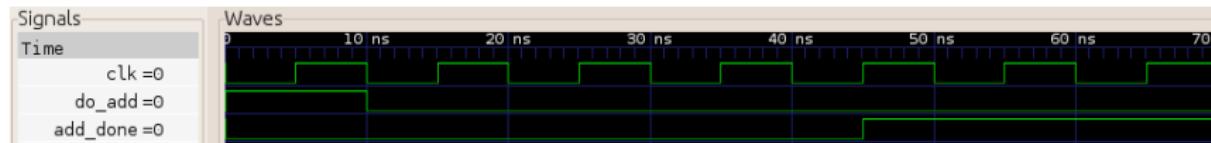
## Control Signals

- ▶ Trigger the process
- ▶ Indicate completion



## State Transition Diagram

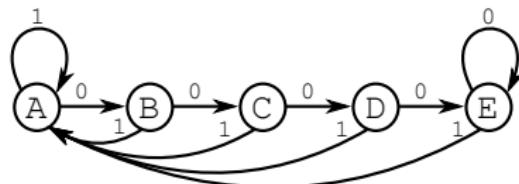

Depending on the signal `do_add`

# State Transitions

Present State	Next State	Actions
A	A, if do_add=1	M <= "00"
	B, if do_add=0	add_done <= '0'
B	A, if do_add=1	M <= "01"
	C, if do_add=0	add_done <= '0'
C	A, if do_add=1	M <= "10"
	D, if do_add=0	add_done <= '0'
D	A, if do_add=1	M <= "11"
	E, if do_add=0	add_done <= '0'
E	A, if do_add=1	M <= "--"
	E, if do_add=0	add_done <= '1'

# State Machine Coding


```
type t_state is (sA,sB,sC,sD,sE);
signal pr_state,nx_state : t_state;

process(clk)
begin
    if rising_edge(clk) then
        pr_state <= nx_state;
    end if;
end process;

rst<=do_add;

process(pr_state,do_add)
begin
    case pr_state is
        when sA => --actions corresponding to state A
            M      <= "00";      --1: Outputs. Caution!!!
            add_done <= '0';     --Do not forget any output!
            if do_add='1' then
                nx_state <= sA;    --2: Compute next state
            else
                nx_state <= sB;    --depending on present state
                and the input(s)
            end if;
        when sB => --actions corresponding to state B
        ...
    end case;
end process;
```

# Simulation Results

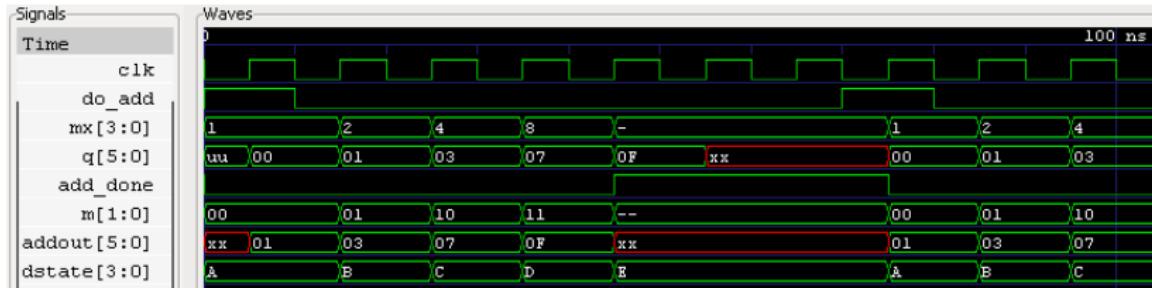

- ▶ Showing  $1+2+4+8 = \text{x}0F = 001111$
- ▶ `add_done` signals when the result is available.
- ▶ Has to be read on the next clock edge!
- ▶ Additional signal `dstate` created to debug the state.