

# Circuit Theory


## Final examination. June 23, 2022

Time limit: 2 hours. Revision day; July 4

Each equation, or group of equations, must be preceded by a brief explanation of what you want to do.
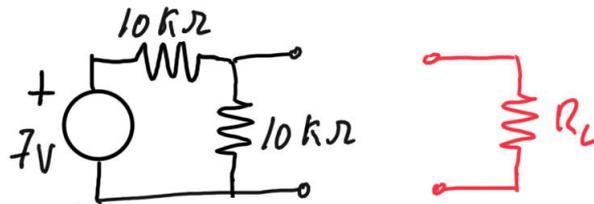
### 1 Problem: (15 %)


Consider the connection of the generator (on the left made of three elements) with the load (on the right).



- Compute the value of  $R_L$  in order to transfer the maximum power from the generator to the load. Use this value in the following questions.
- Compute the power transferred to the load.
- Compute the power at each one of the three elements of the generator.

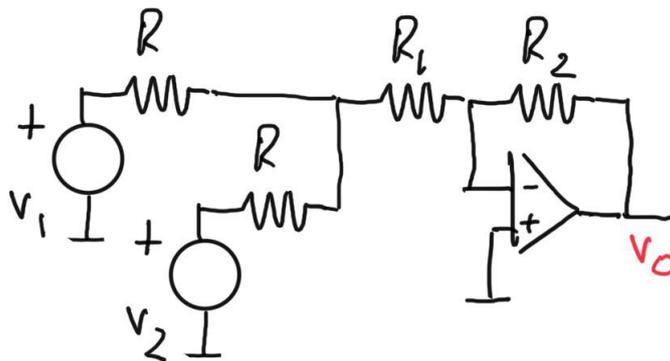
### 2 Problem (15 %)

- Determine  $v_o$ .
- Give values to the resistances, in order to have  $v_o = -(v_1 + v_2)$ .



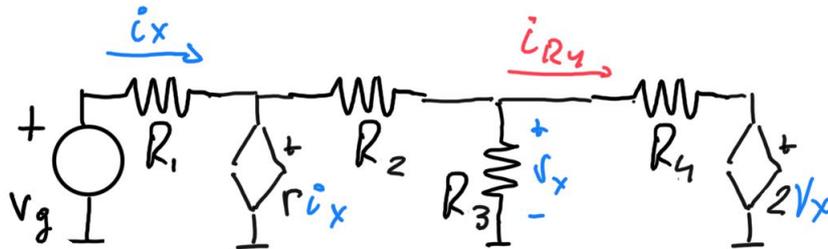
### 3 Problem: (15 %)

- First, Use the nodal analysis to determine the voltage  $v_x$ .
- Next, determine  $i_{R_4}$ .
- Finally compute  $i_{R_4}$  when  $v_g = 10\text{ V}$  and  $R_1 = R_2 = R_3 = R_4 = r = 1\text{ k}\Omega$ .


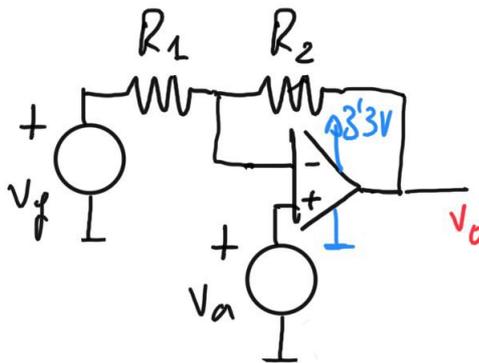
### 4 Problem: (15 %)


Use the following circuit as a *signal conditioner* to condition an audio signal  $v_g$  that takes values from  $-0.5\text{ V}$  to  $+0.5\text{ V}$ . The goal is that  $v_o = +3v_g + 1.65$  or  $v_o = -3v_g + 1.65$ . Note that the OA is powered at  $3.3\text{ V}$  and  $0\text{ V}$ .



- First, give values to  $R_1$ ,  $R_2$  and  $V_a$ . If  $v_g = 0.5 * \cos(2\pi 10t)$ , draw the output  $v_o$ .
- Next, consider the use of the power source of the OA (of  $3.3\text{ V}$ ) to avoid the use of  $v_a$ .
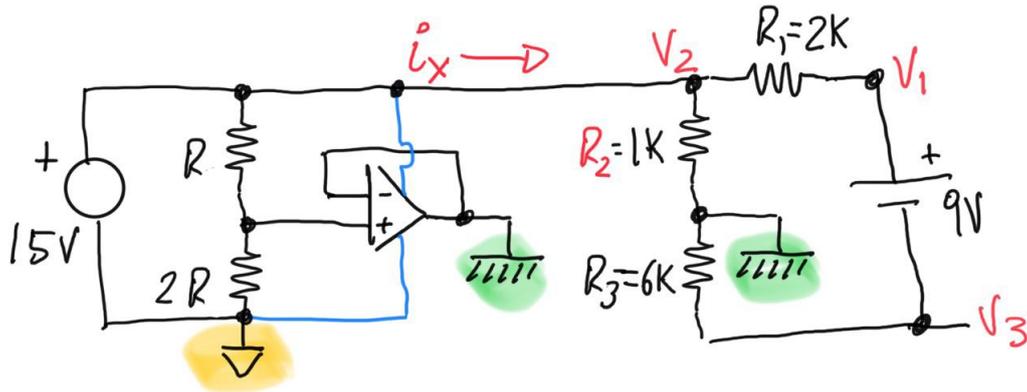
### 5 Problem: (20 %)

- Compute the voltage at  $v_1$ ,  $v_2$  and  $v_3$  with respect to the reference in yellow.
- Compute the voltage at  $v_1$ ,  $v_2$  and  $v_3$  with respect to the reference in green.
- Compute the currents through  $R_1$ ,  $R_2$  and  $R_3$ . Draw the direction in the circuit.
- Compute  $i_x$ .
- Give a value to  $R_2$  in order to have  $i_x = 0$ .



### 6 Problem: (20 %)

- Draw  $v_o(t)$ , between  $t = 0$  and  $t = 3$  ms, considering  $R_1 = 1.5$  k $\Omega$ ,  $R_2 = 3$  k $\Omega$ ,  $C_1 = 1.5$   $\mu$ F and  $C_2 = 3$   $\mu$ F. Compute  $v_o(t)$  at  $t = 0$ ,  $t = 1$  ms,  $t = 2$  ms and  $t = 3$  ms.
- Calculate the total energy stored by both capacitors at the instant when this energy is at its maximum.
- Compute when the LED will be turned ON and OFF.

