

Circuit Theory


Mid-semester examination. April 26, 2022

Time limit: 1 hour 45 minutes.


1 Short Questions (50%)

Each equation, or group of equations, must be preceded by a brief explanation of what you want to do.

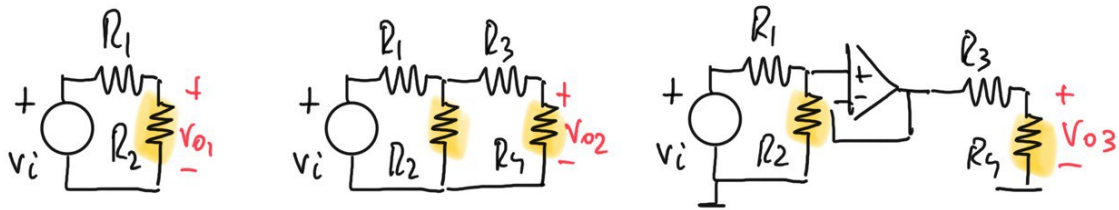
- a) Determine the voltage in red of the following circuits and the power consumed by the elements in yellow.



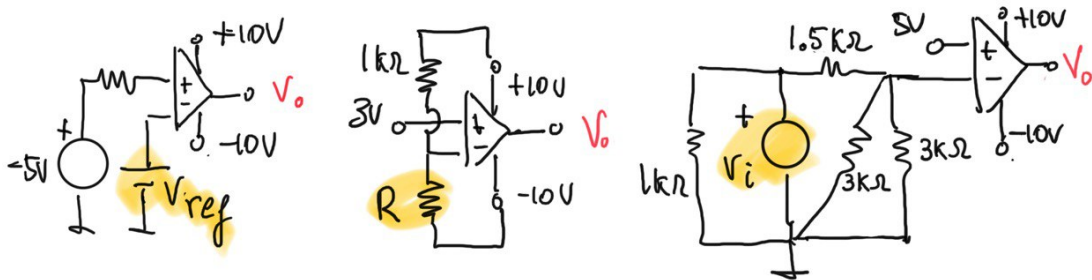- b) Compute the range of values of the elements in yellow that saturate the output of each comparator to a positive value.



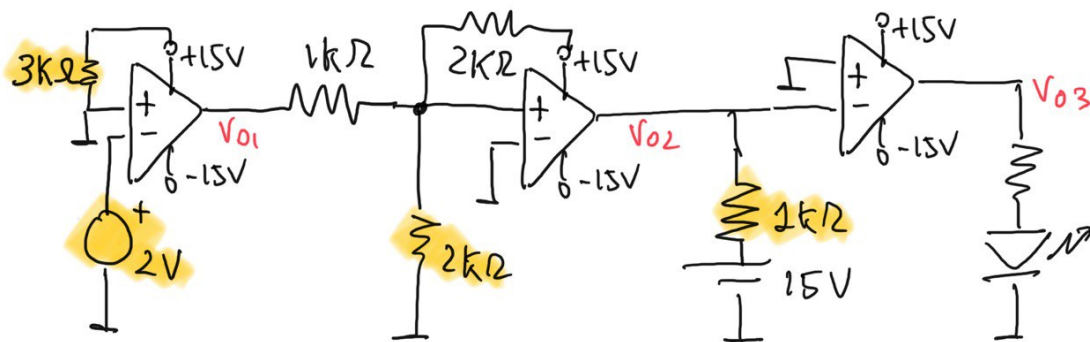
- c) Compute the power consumed by the elements in yellow. Comment on the results if the maximum power of the resistors is $1/4$ W. Will the LED be turned on? Compute the value of R_L if $V_{threshold} = 1.5$ V and the desired current is $i_{LED} = 15$ mA.



2 Problem: the Wheatstone bridge (20 %)

The following circuit shows a *Wheatstone bridge* in which R_4 is a *strain gauge*, a resistance whose value changes when it is deformed in a specific direction. To simplify the problem, we could say that $R_4 = R_0(1 + dx)$, where R_0 is the value of R_4 when there is no deformation, and dx is the deformation in micrometers. The resistance R_3 is adjusted to achieve $v_s = 0$ when there is no deformation, i.e $dx = 0$. When the resistance R_4 undergoes a deformation, $v_s \neq 0$. In the following, consider $v_i = 9\text{ V}$, $R_1 = 1\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$ and $R_0 = 4\text{ k}\Omega$.

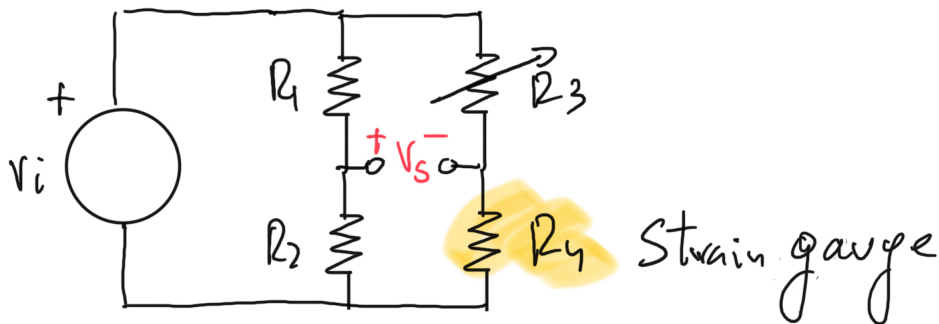- Comment on the number and type of equations needed to determine the voltage and current of all the elements in the circuit. Hint: number of KCLs and its relationship to the number of nodes...
- Compute v_s as a function of v_i , R_1 , R_2 , R_3 and R_4 .
- Adjust R_3 to get $v_s = 0$ when there is no deformation.
- Compute v_s when the deformation is $1\text{ }\mu\text{m}$, i.e $dx = 1$.



3 Problem: the inverting Schmitt trigger (30 %)

We want to design an inverting Schmitt trigger (the comparator with hysteresis that we have studied during the course) whose output v_o turns on a LED when the deformation of the previous strain gauge is greater than $1.5\text{ }\mu\text{m}$, and turns it off when it is lesser than $1\text{ }\mu\text{m}$. Use a rail-to-rail operational amplifier with a power supply of $\pm 9\text{ V}$.

- Compute the values of v_s of the previous circuit (the Wheatstone bridge) for the two values of dx that limit the hysteresis cycle.
- Draw the relationship v_o versus v_s .
- Design the comparator with hysteresis using two resistors and an extra voltage source.
- Design the comparator with hysteresis using no extra voltage source.
- Draw the complete design including the Wheatstone bridge and the LED.